

Designing Microphone Preamplifiers

By Gary K. Hebert
129th AES Convention
San Francisco CA, November 2010


THAT Corporation

The Tutorial Overview

Section 1
Support Circuitry

Section 2
The Amplifier

Simple Block Diagram

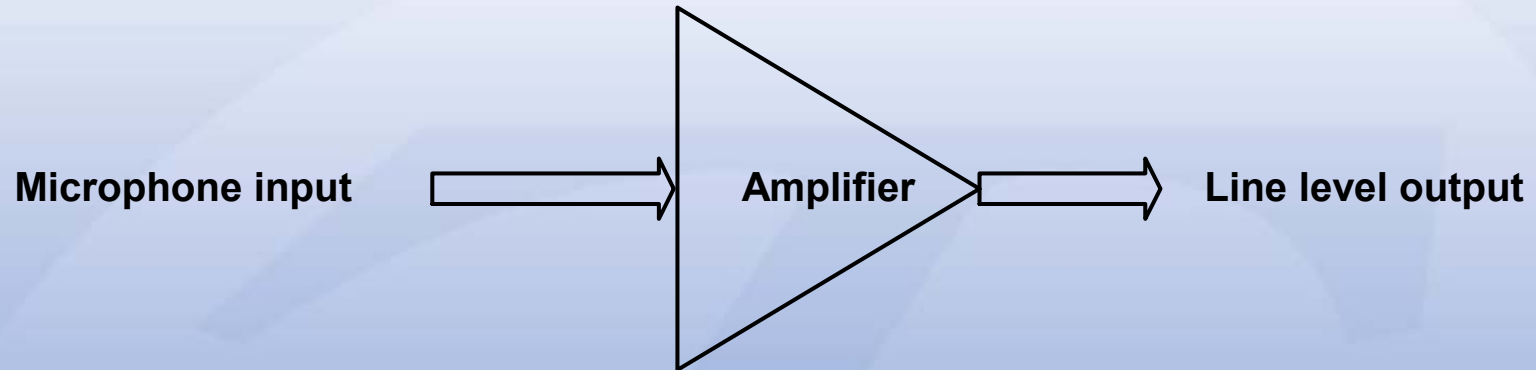

Microphone signal levels vary widely due to:

- Microphone sensitivity
- Source SPL
- Proximity to source

Line level outputs are somewhat more constrained:

- “Standard” maximum operating levels include 24, 18, 15 dBu
- A/D converter input levels are approximately 8 dBu or 2 Vrms differential

Typical Requirements

Gain

- Up to 40 dB covers the majority of close-mic'd applications
- Some situations require more than 70 dB
- Variability of input levels requires adjustable gain over a very wide range

Phantom Power

- Required for many microphones
- Standardized in IEC EN 61938
48 Volts +/- 4V at up to 10 mA per microphone
- On / off control

Input Pad

- Can allow higher input signal levels, at the expense of noise
- May be required depending on minimum gain and supply rails
- 20 dB is common

Resistant to common mode noise and RFI

Reliable

Preamplifier Technologies

Transformer-Coupled Vacuum Tube

- Robust
- Colorful
- Costly

Transformer-Coupled Solid State


- Also Robust
- Performance can be excellent
- Cost can be high

Transformerless Solid State

- More vulnerable
- Performance can be excellent
- Cost ranges from very low to high


Transformerless solid state designs are the focus today

Amplifier Input Bias Current

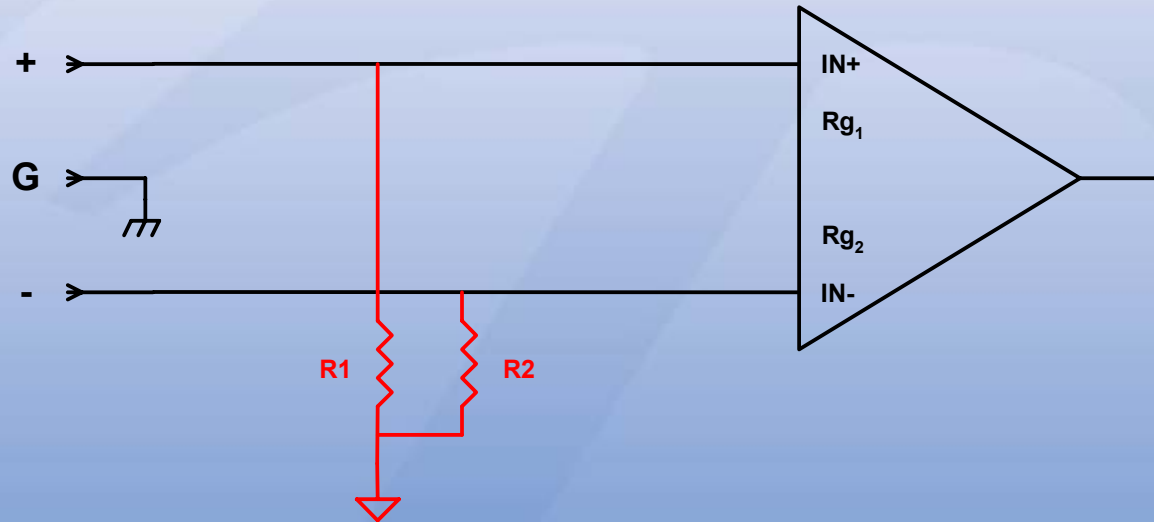

Must provide a DC current path to supply the amplifier input bias current

Gain Control

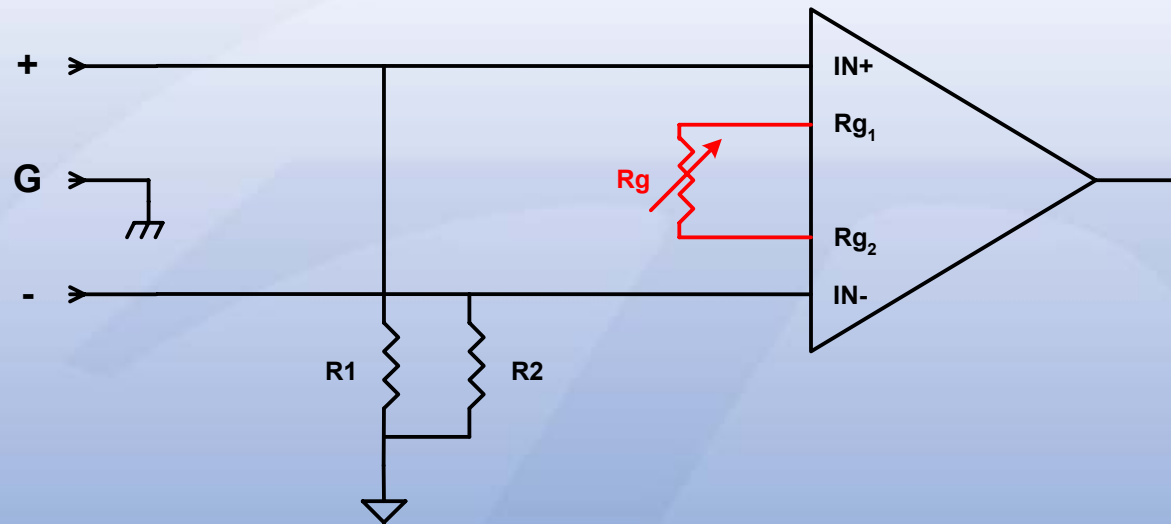

The amplifier is often designed to vary gain using a single variable resistor (R_g)


Manually controlled options

- Potentiometer with continuous control over a defined range
- Switched resistor network with a fixed number of steps and gain settings

Digitally controlled options


- Digitally switched resistor network with a predetermined number of steps
- Switches are either relays or silicon devices
- Both discrete and integrated circuit solutions are available

Phantom Power

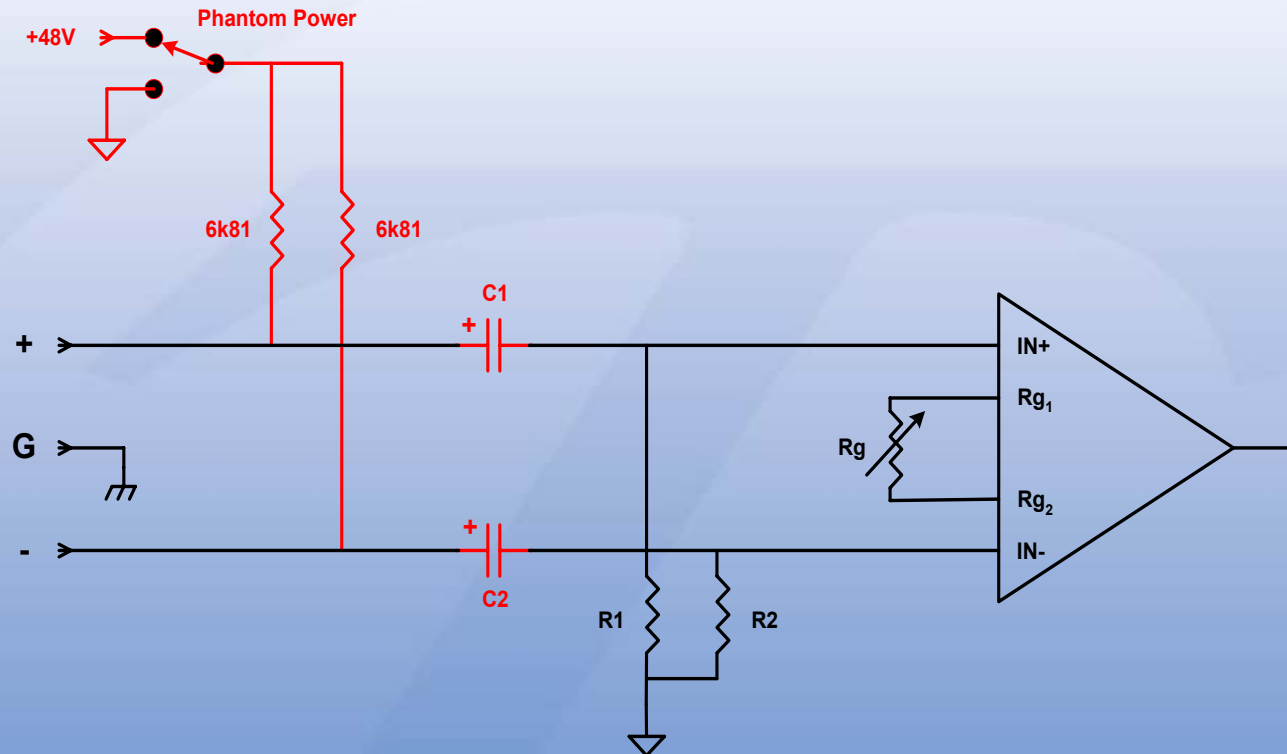


- C1 and C2 required to block the 48 V from the amplifier inputs
- 6.81k series resistors are specified in the standards for 48V phantom power
- On/Off is available via a
 - Simple mechanical switch in manual applications
 - Relay or silicon switch in digitally controlled systems

Input Pad

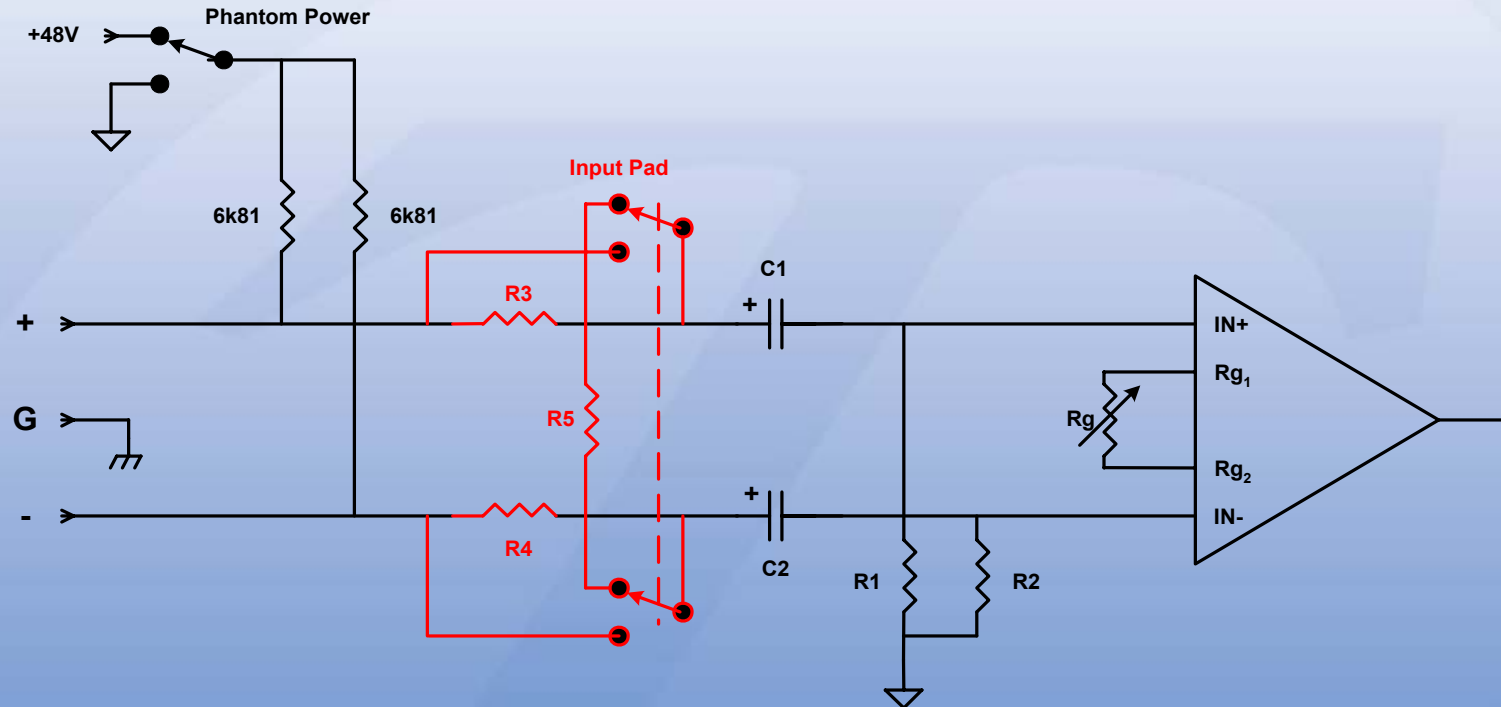

- Input pad is simply a signal attenuator prior to the amplifier
- This is a differential-only pad, it does not attenuate common-mode signals


“Complete” Microphone Preamp

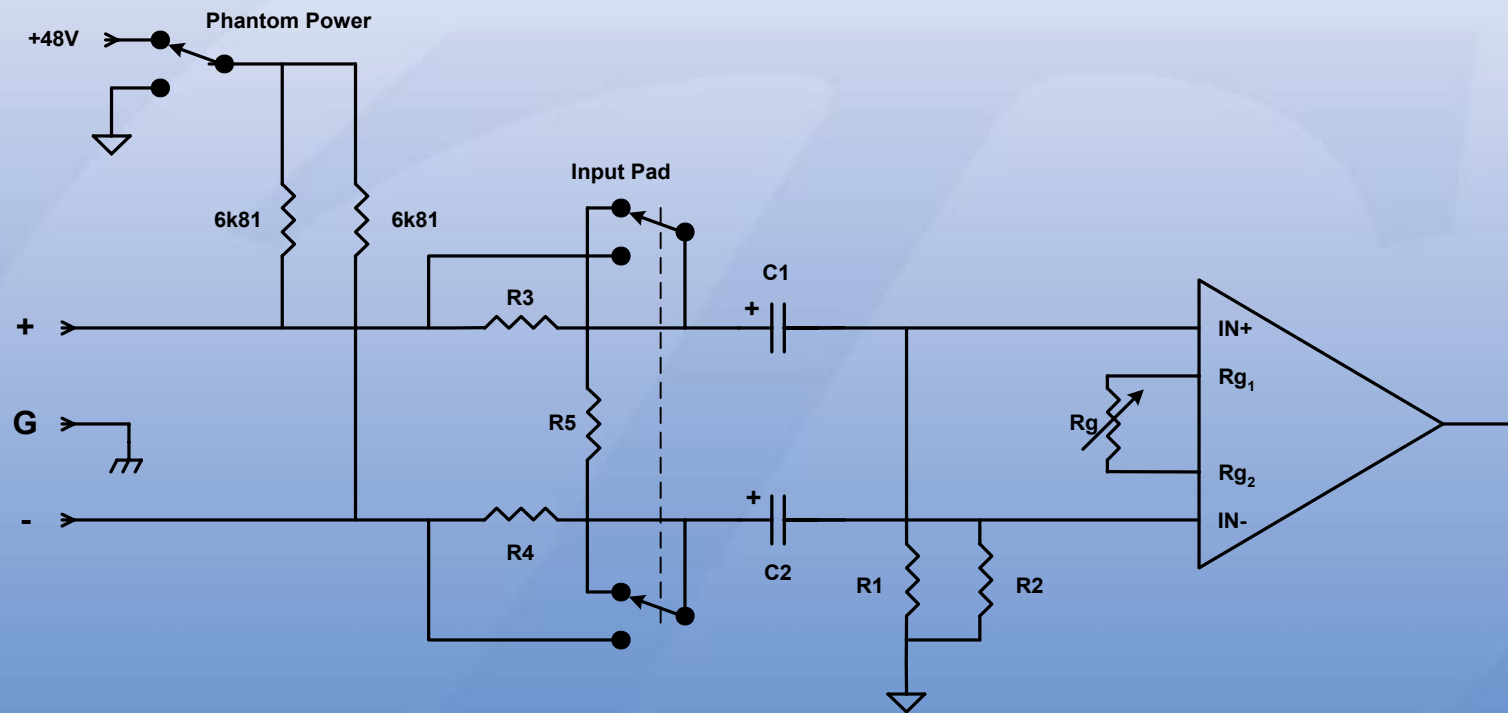

*It would be nice to say “that’s all there is”
but.....*


there are gremlins in the details!!

DC Offset Changes

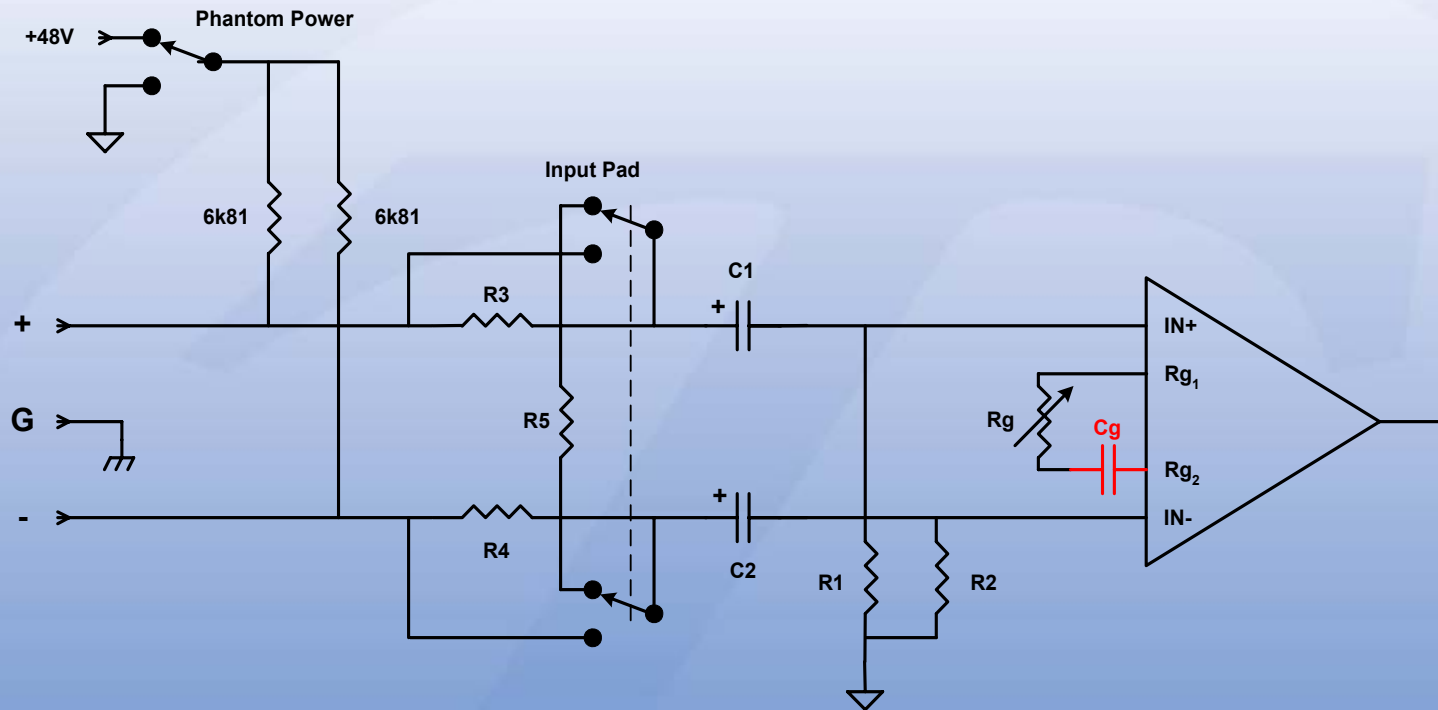


- Changes in gain can result in the DC offset changes at the output of the amplifier
- 2 solutions are available
 - Adding a capacitor (C_g) sets the DC gain to a fixed value and avoids these offset changes
 - A servo-amplifier can also be effective, but we don't have time to discuss them today

Trade-offs with C_g

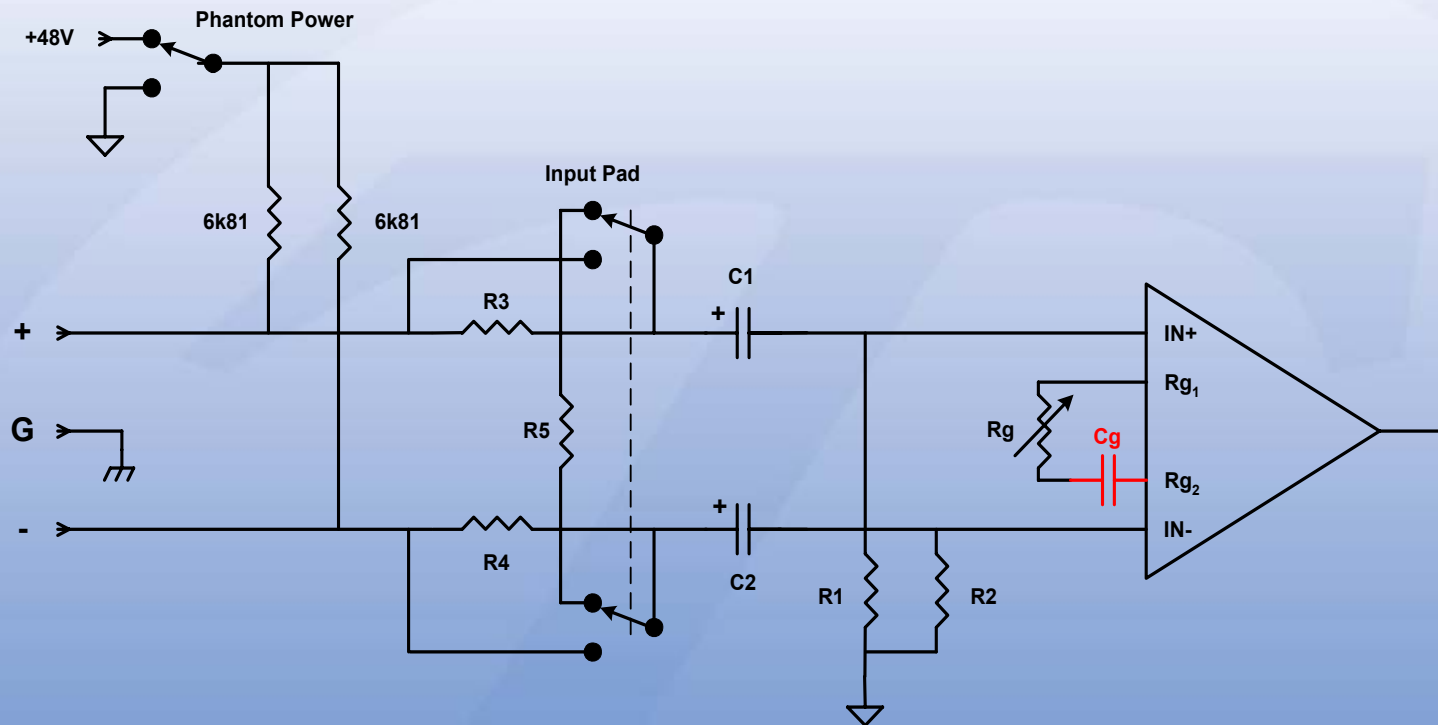


- R_g and C_g create a high-pass filter in the signal path
- R_g can vary from <5 to $>10k$ ohms
- C_g must have a very large capacitance to avoid low frequency audio attenuation
 - Worst at highest gain

Resistor Value Selection

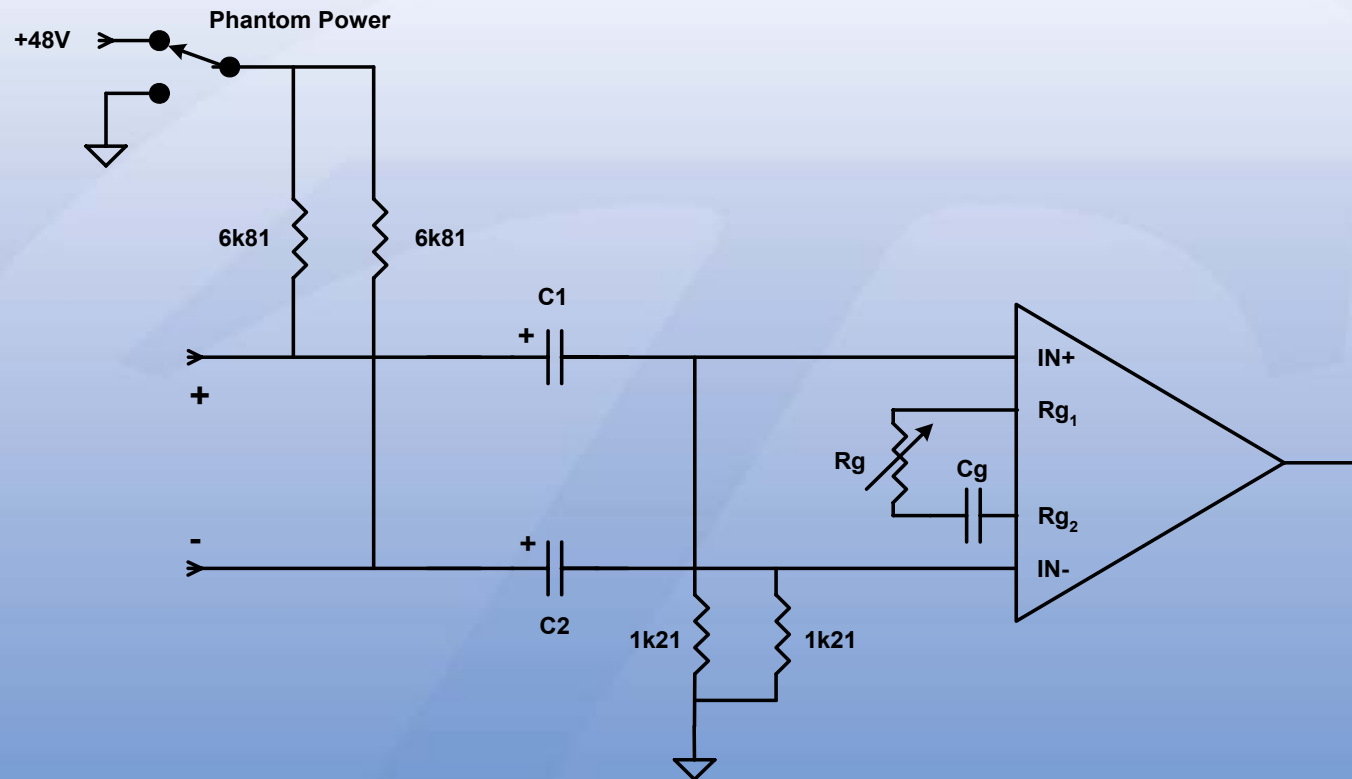


- Microphone are commonly specified for 2 to 3 kohm loads
- Differential input impedance is $(R1 \parallel 6.81k) + (R2 \parallel 6.81k)$
- Therefore, suitable values for R1 & R2 are between 1172 and 1924 ohms

Capacitor Value Selection

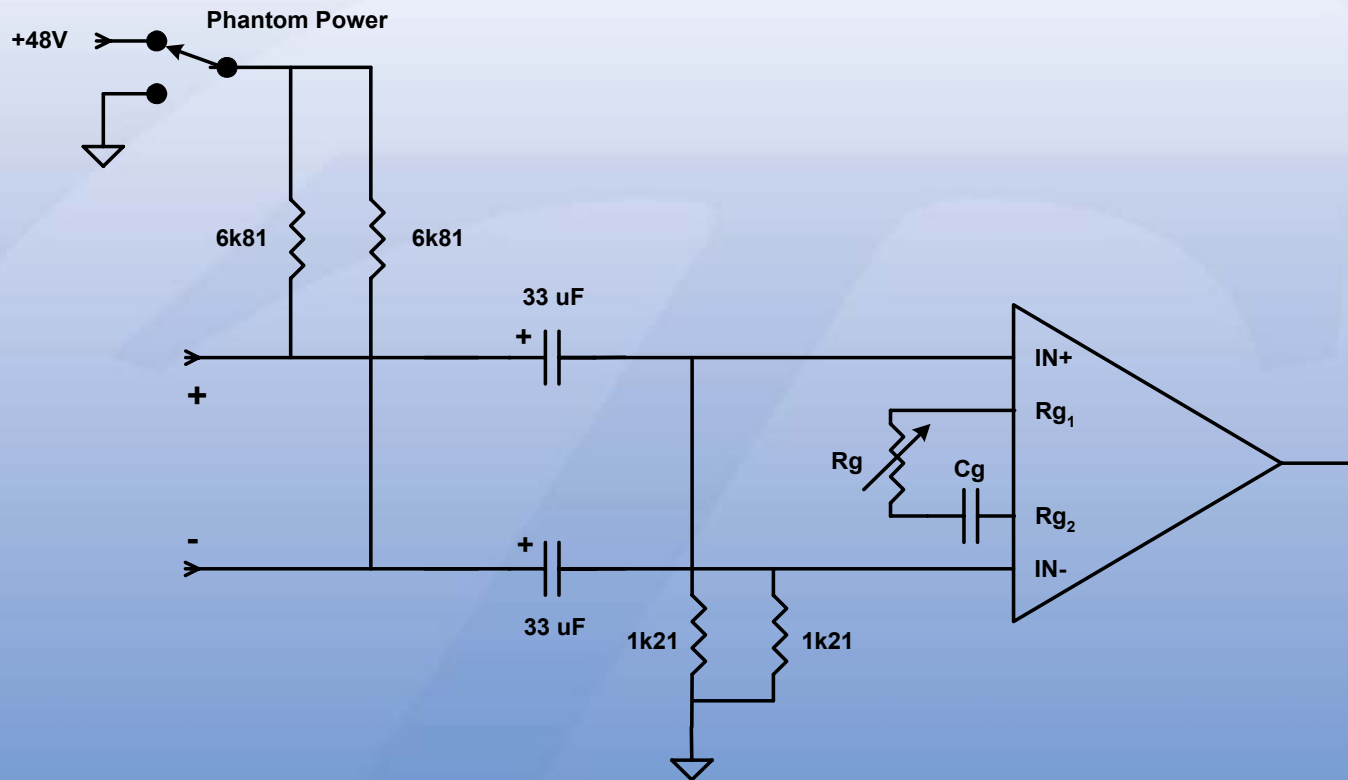


- High-pass filter corner frequency is set by the blocking capacitor and bias resistor and is equal to $1 / (2 \times \pi \times R \times C)$
- For a 5 Hz corner frequency, the minimum values for C1 & C2 are 26 uF
- The next largest standard value is 33 uF
- Results in a nominal corner frequency of about 4 Hz

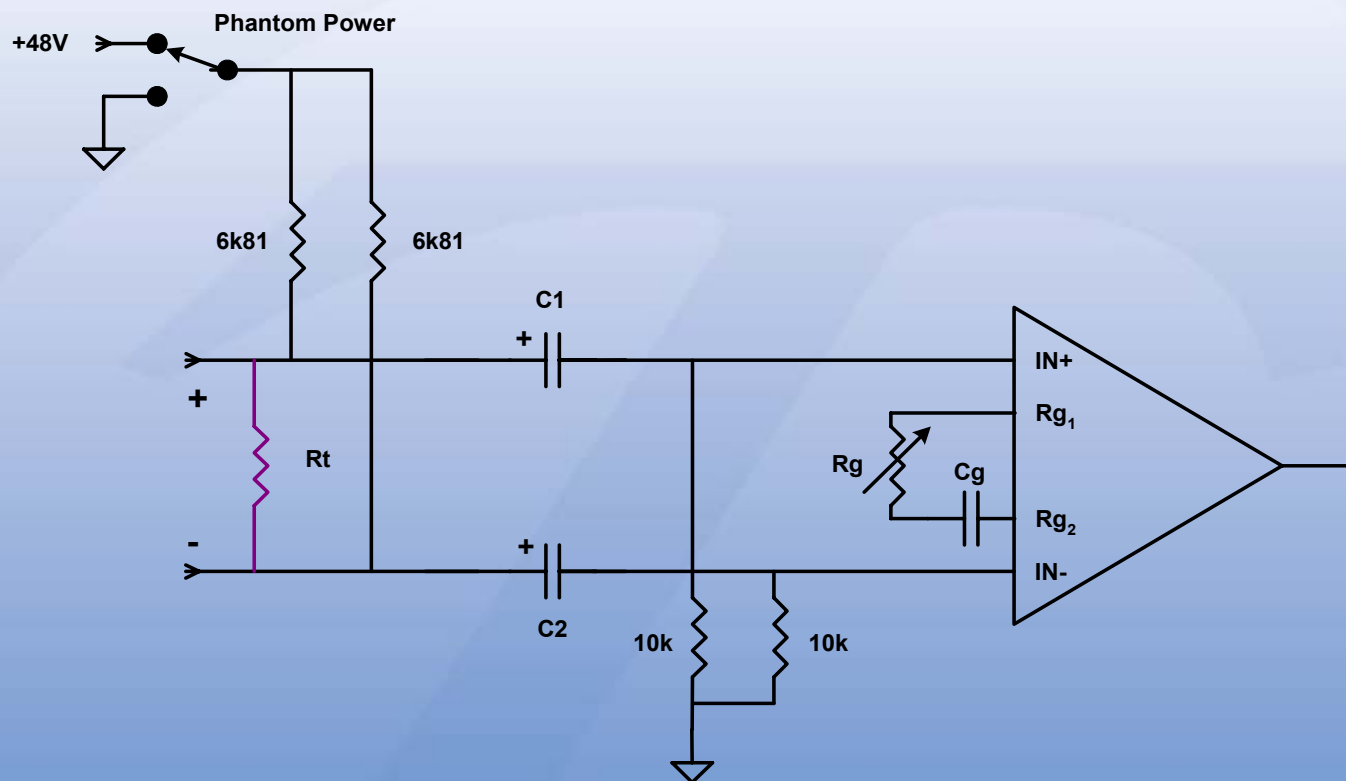Alternative Resistor-Capacitor Value Selection




- C_1 and C_2 can be made smaller if bias resistors are made larger
- R_{in} is defined by R_t
- However, C_1 and C_2 convert $1/f$ noise to $1/f^2$ noise
- 10k resistors contribute thermal noise and current noise $\cdot R$

Common Mode Rejection (CMRR)

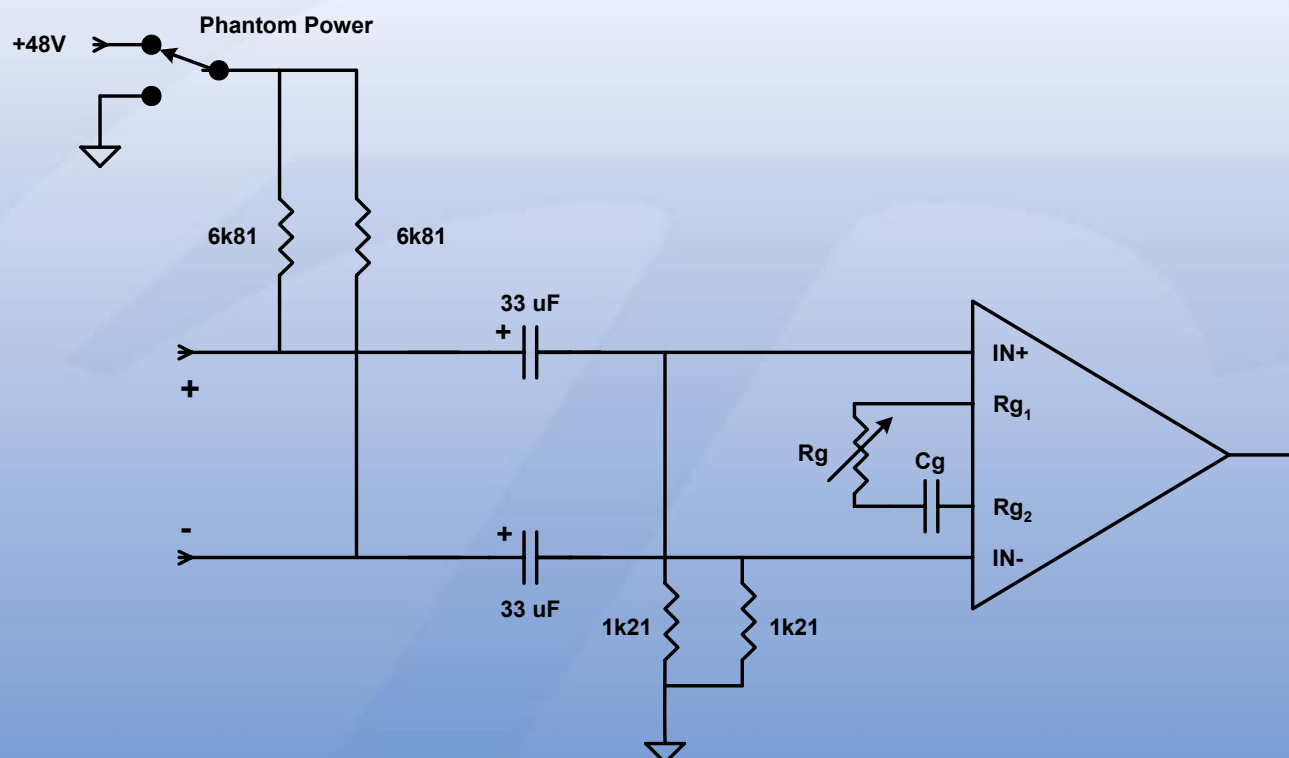


- Common-mode to differential conversion results from mismatches in:
 - 6.81 k resistors
 - 1.21 k resistors
- Low frequency CMRR affected by capacitor mismatch

U-Pad Attenuator

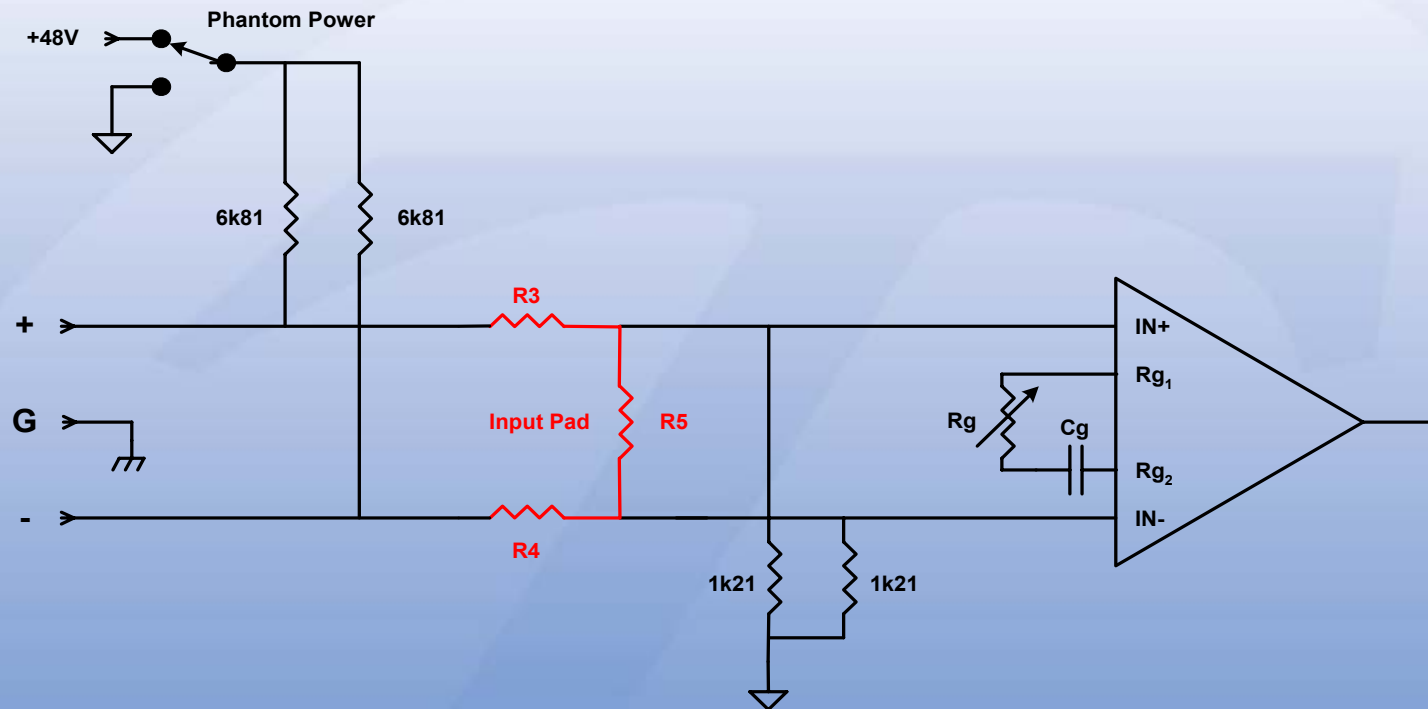


- Z_{IN} with and without pad can be closely matched
- Can be designed for any attenuation
 - 20dB is typical
- Noise performance is degraded
- Better noise, less headroom with less attenuation

Example -20 dB Input Pad

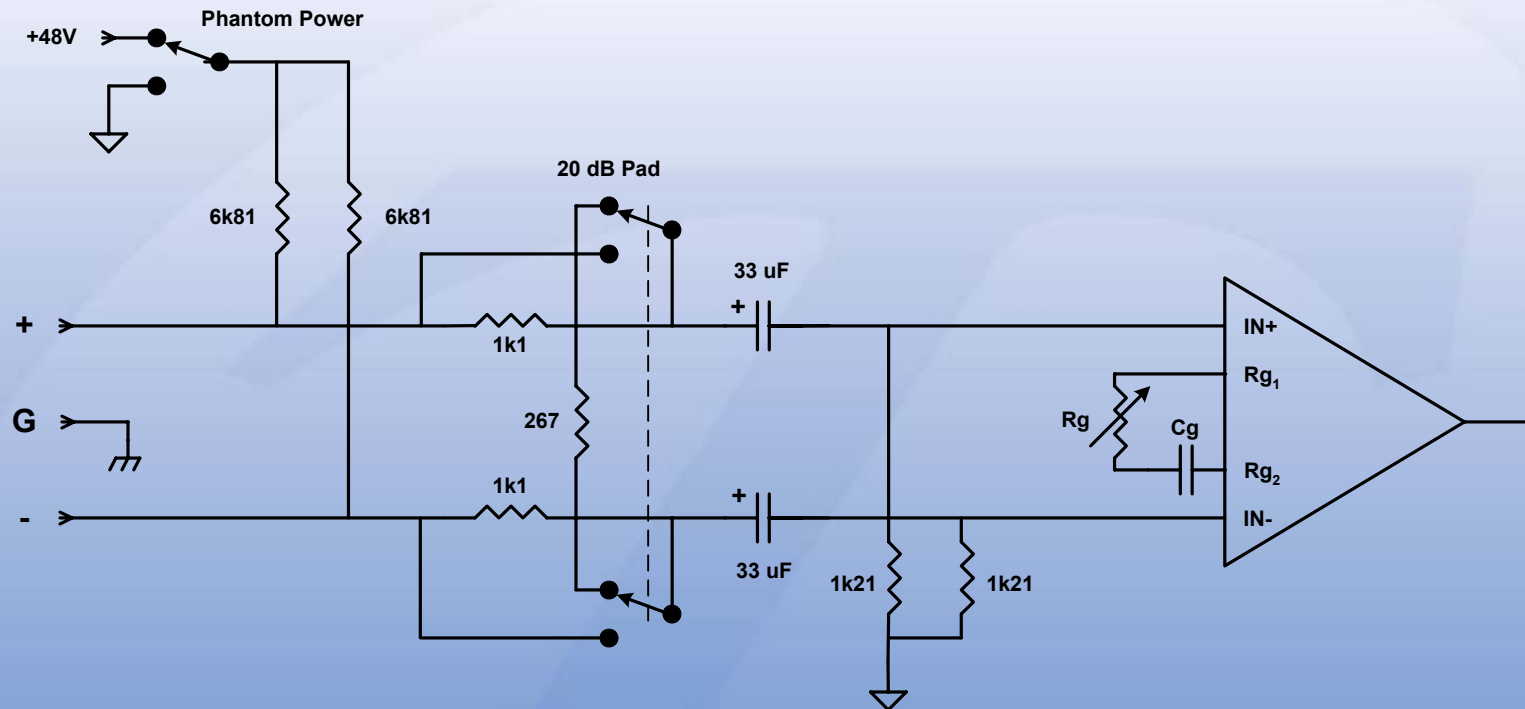

- Z_{IN} with and without pad is approximately 2k
- 20 dB Attenuation
- Pad output impedance is approximately 240 ohms
- See THAT Design Note DN-140 for details and alternatives

RFI Protection

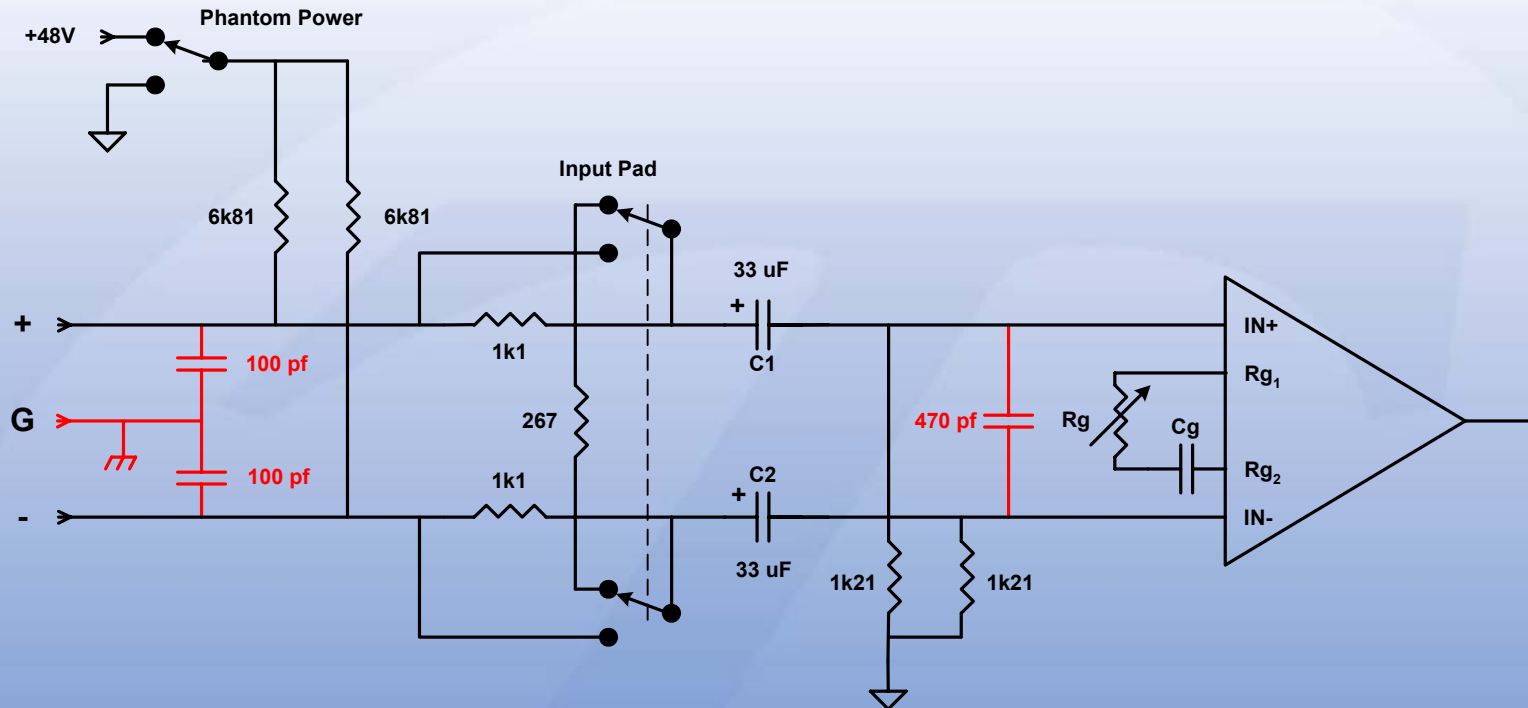

RFI protection is required in any practical design


100 pf caps at the input connector attenuate differential and common-mode RFI

470 pf cap at amplifier input pins reduces differential high frequencies from both internal and external sources

Phantom Power Faults


- **Shorting input pins to ground with phantom turned on**
 - 33uF coupling caps C1 & C2 start charged to 48V
 - Positive end of C1, C2 connect to ground
 - Negative end of C1, C2 driven to -48V!
- **The shorting sequence can vary**
 - “Single-ended”: One input to ground
 - “Common-mode”: both inputs to ground simultaneously
 - “Differential”: One input to ground, then the other
 - Differential is worst
- **Big currents flow as C1, C2 discharge**
 - Currents over 3 *amperes* flow in the capacitors

Phantom Fault Protection

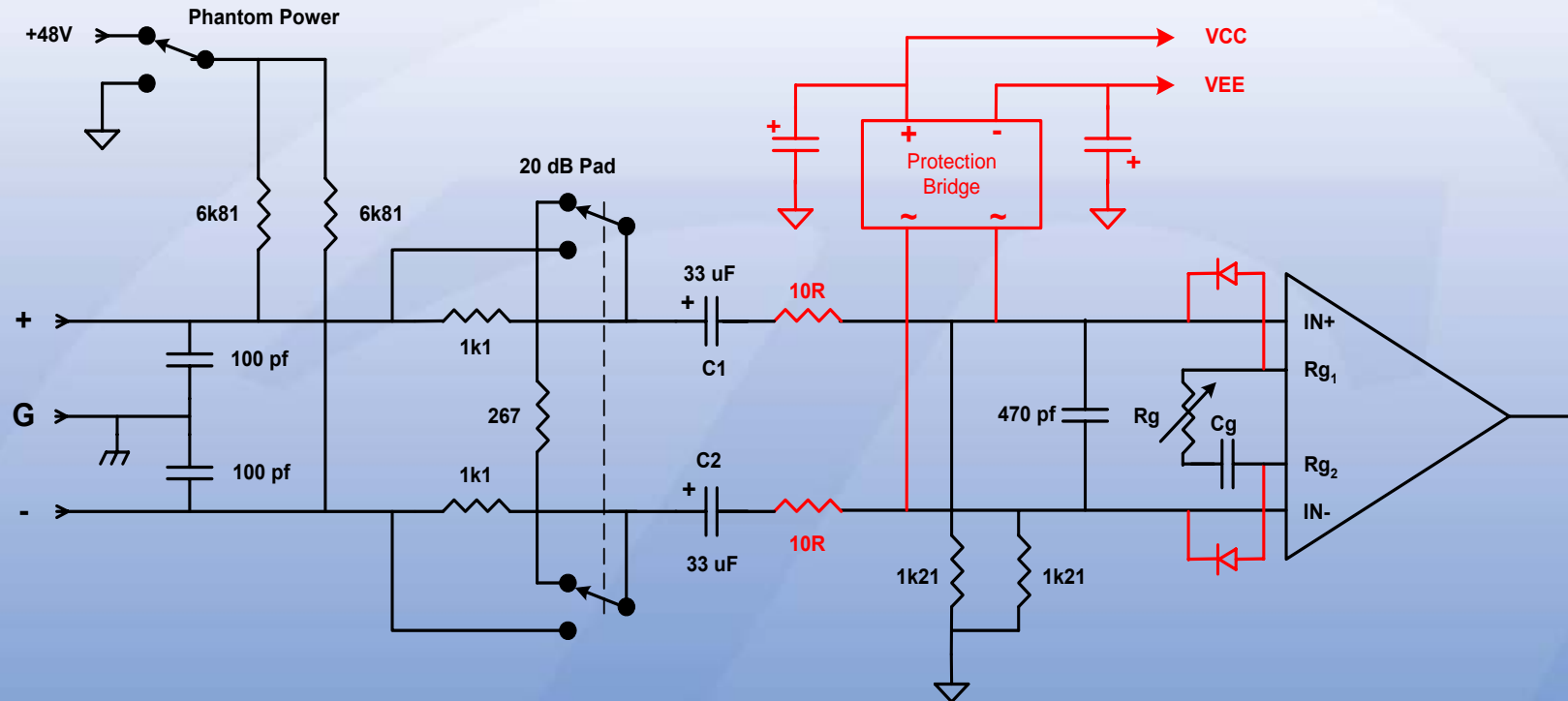

- Limit the current with small value resistors
- Direct fault currents away from the amplifier inputs
 - Input diodes provide a conduction path which bypasses the amplifier
 - This current varies with gain setting
- Diode bridge directs fault current to rails
 - Consider impact on supply rails
 - Minimize supply transient with capacitance

Complete Microphone Preamp

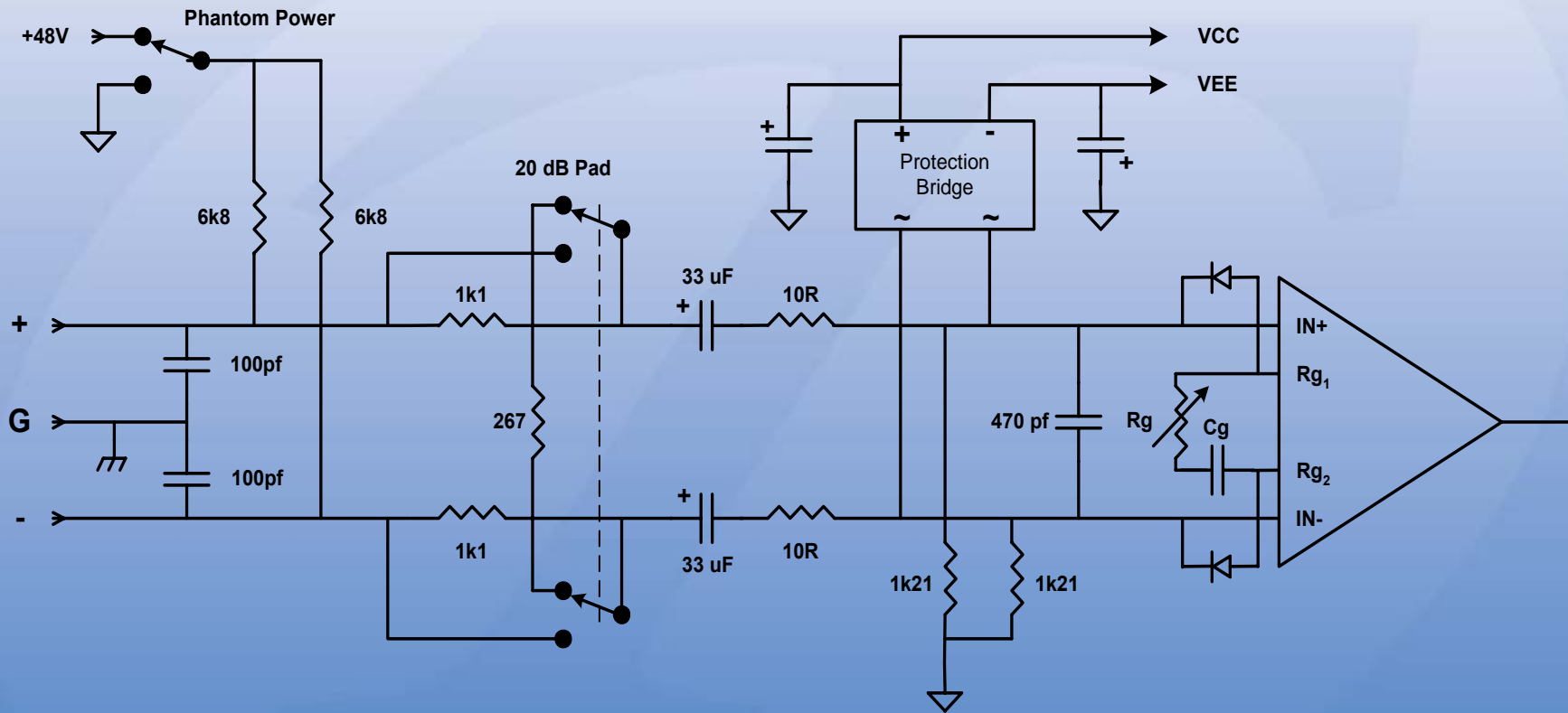

References and Additional Information

- THAT Corp *“THAT 1510/1512”* data sheet
- THAT Corp *“THAT 1570 & 5171”* data sheets,
- THAT Corp *“Design Note 140”*
- THAT Corp *“Design Note 138”*
- THAT Corp *“Analog Secrets Your Mother Never Told You”*
- THAT Corp *“More Analog Secrets Your Mother Never Told You”*
- *“The 48 Volt Phantom Menace Returns”* Audio Engineering Society Preprint from the 127th AES Convention, Oct 2009
- *“The 48 Volt Phantom Menace”* Audio Engineering Society Preprint from the 110th AES Convention, May 2001

All THAT Corp references are available at thatcorp.com


Amplifier Topologies

What's inside the triangle?


Scope

- We will concentrate on topologies that allow a wide range of gain with a single control.
- The goal is to balance the requirements for low distortion and low noise at both ends of the gain range.

Simple Mic Preamp Schematic

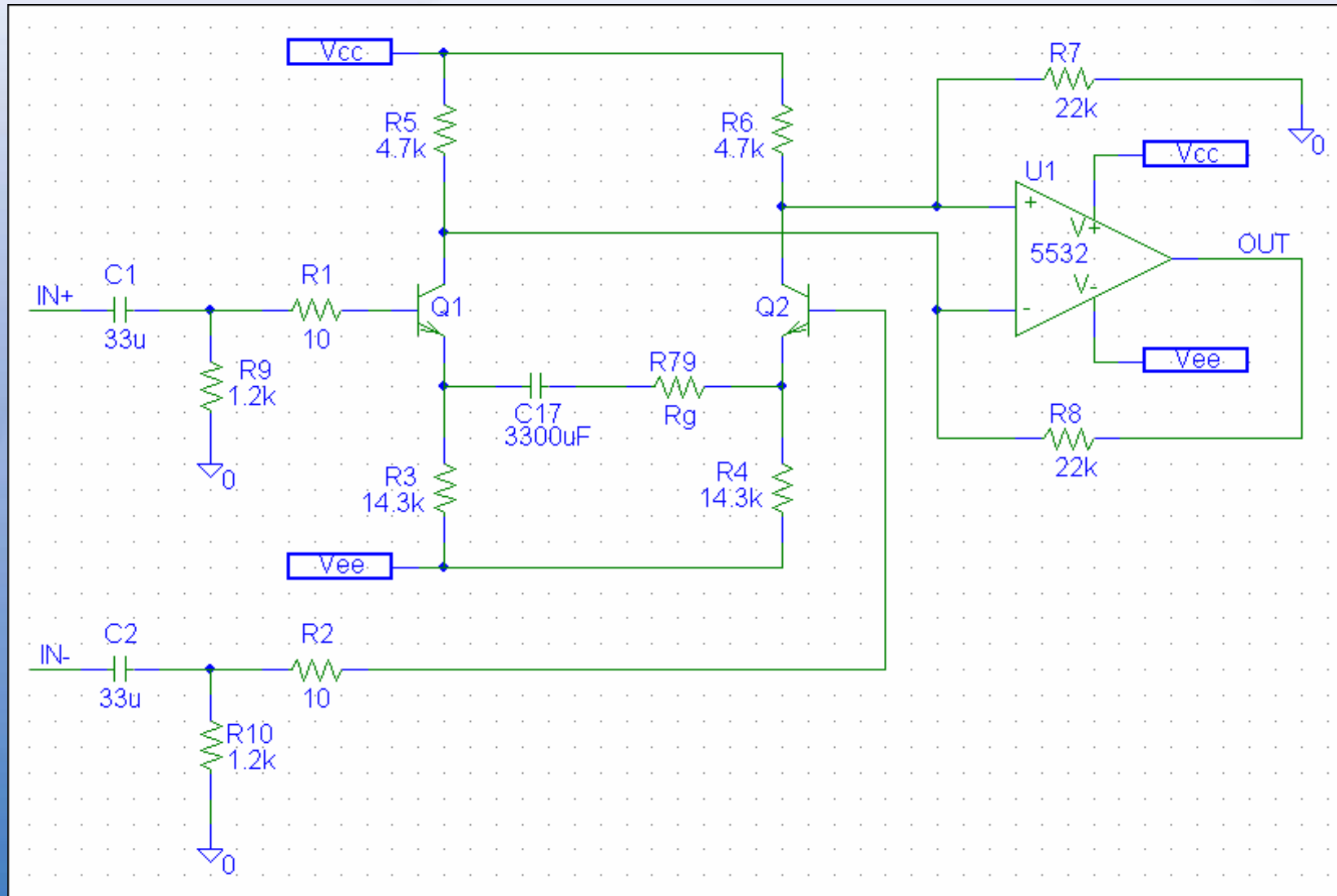


Simple Mic Preamp

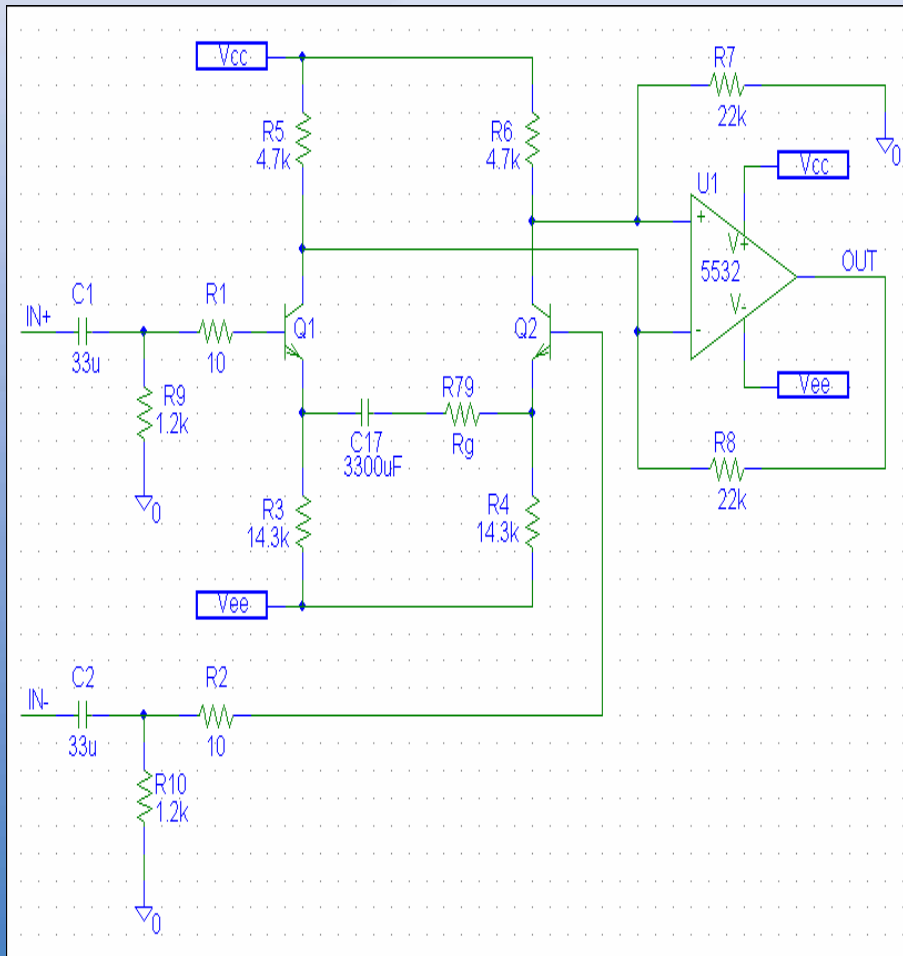


- $I_c = 1 \text{ mA}$ per input transistor, set by $(|V_{EE}| - V_{BE})/14.3\text{k}$
- Diff Gain = $22\text{k}/(r_e + R_g/2 || 14.3\text{k})$
- where $r_e = 1/g_m = KT/ql_C = 26 \text{ ohms}$
- But – “ r_e ” is current dependent!
- Minimum gain = $22\text{k}/14.3\text{k} = 3.7 \text{ dB}$

Simple Mic Pre THD Performance

THD vs. Gain, 1 kHz, +20 dBu Out

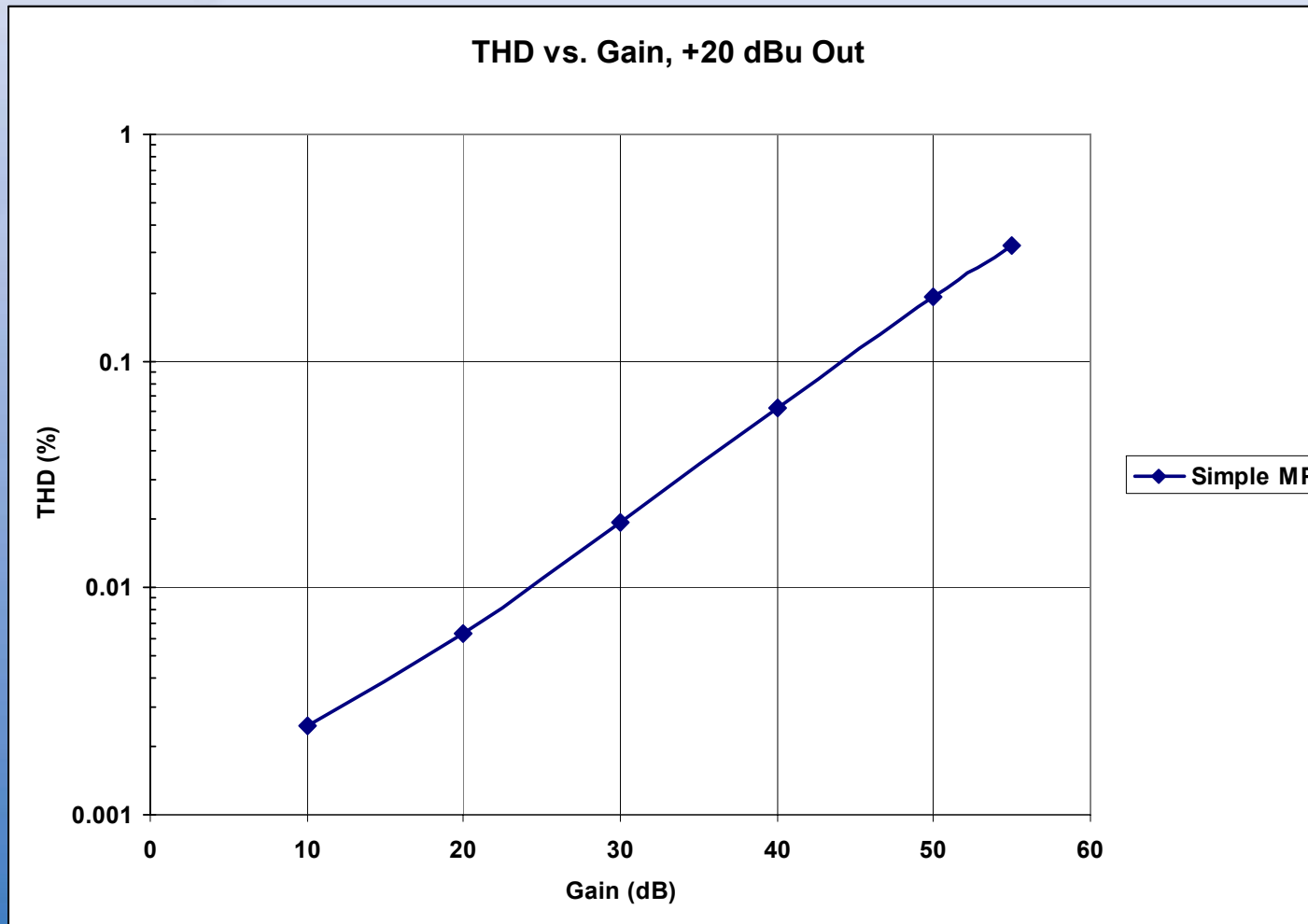


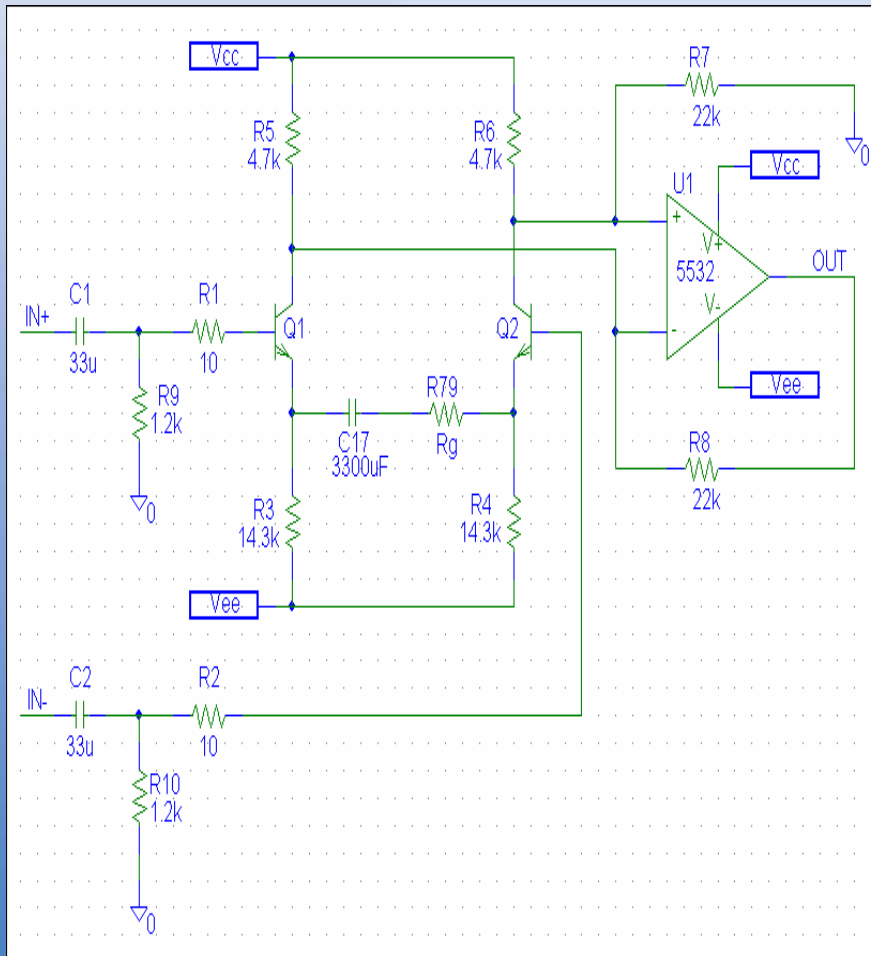High-Gain Noise Sources of Simple Mic Preamp



- Input noise at high gains dominated by:
- $Q_1, Q_2 I_C$ Shot Noise (RTI) = $\frac{2\sqrt{qI_C}}{g_m} = \sqrt{4kTr_e}$
- $Q_1, Q_2 r_b$ Thermal Noise = $\sqrt{8kTr_b}$
- R_1, R_2, R_g Thermal Noise = $\sqrt{4kT(R_1 + R_2 + R_g)}$

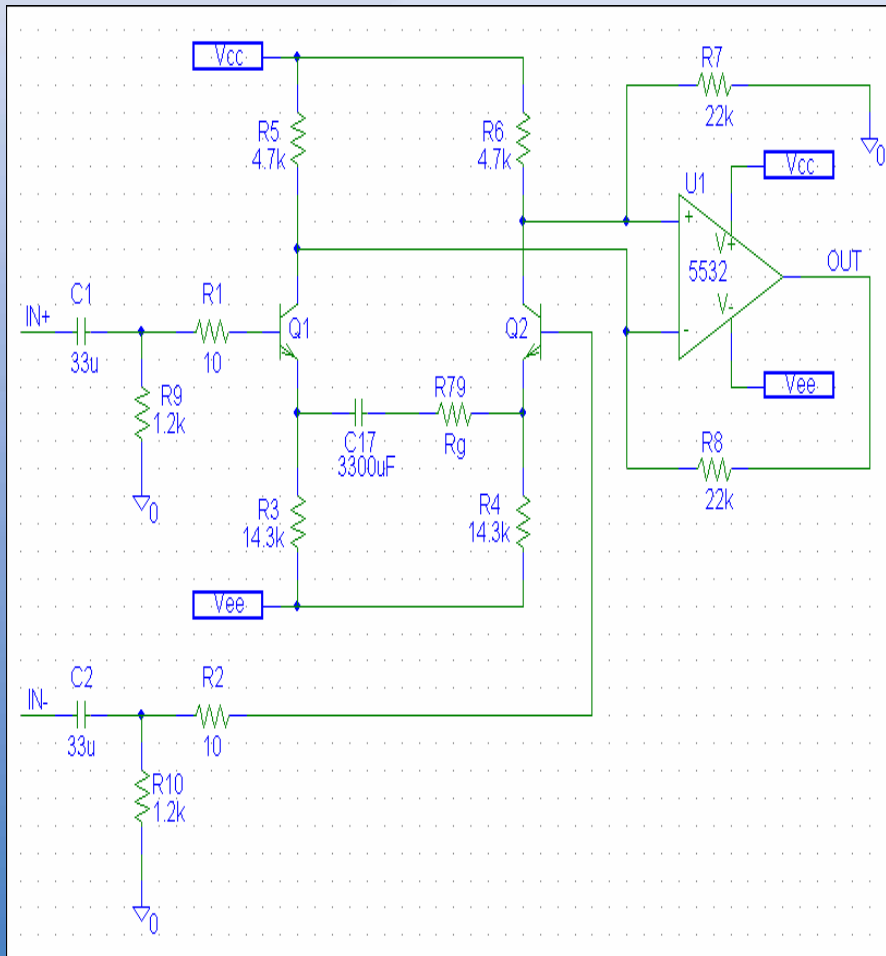
Low-Gain Noise Sources of Simple Mic Preamp




- Input noise at low gains dominated by:
- Thermal Noise of R_5 and R_6
- Thermal Noise of:

$$R_g \parallel (R_3 + R_4)$$
- $Q_1, Q_2 I_B$ shot noise across $\frac{R_g \parallel (R_3 + R_4)}{2}$
- EIN of U1

Noise Performance of Simple Mic Preamp

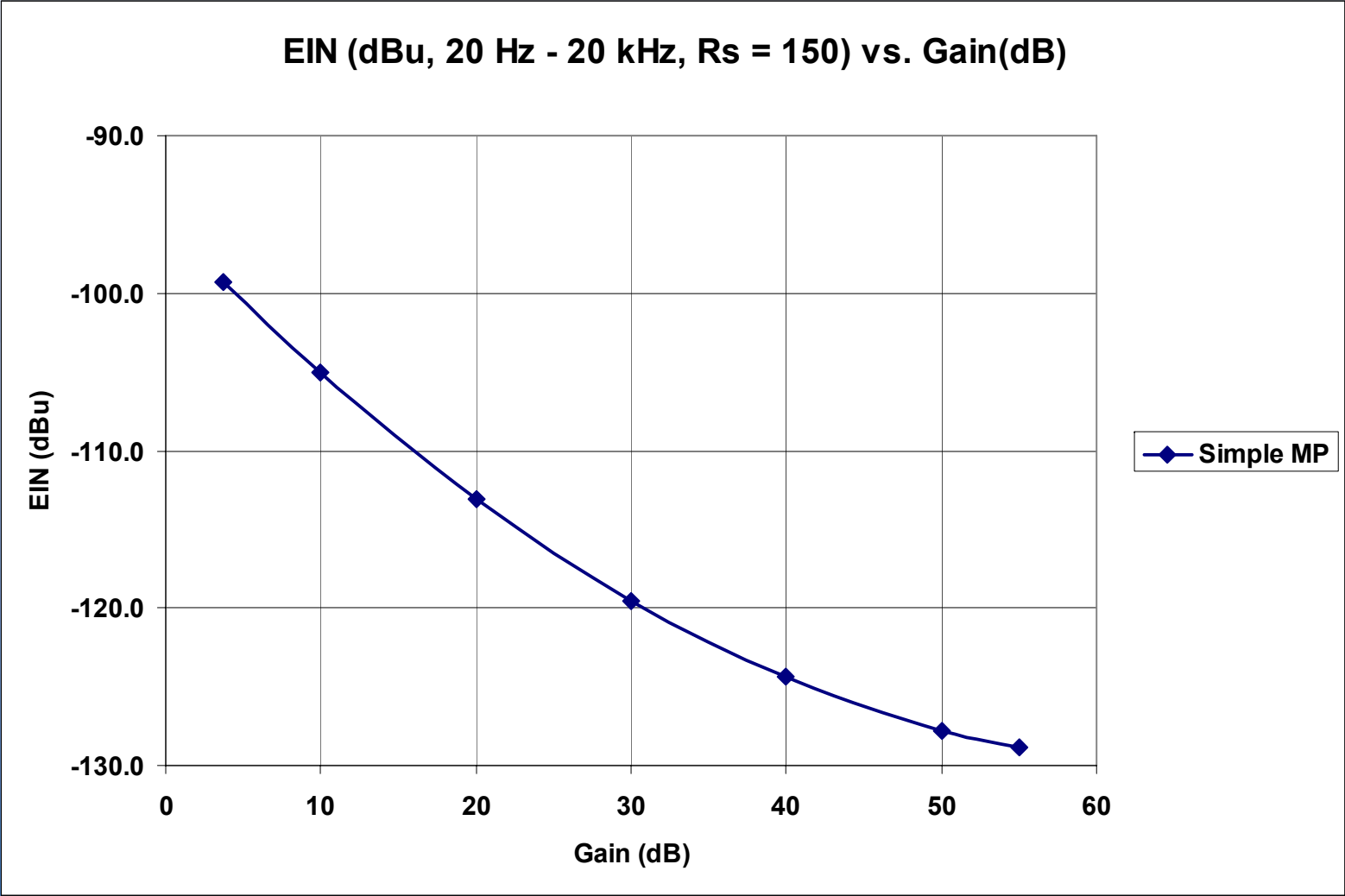

CMRR Performance of Simple Mic Preamp

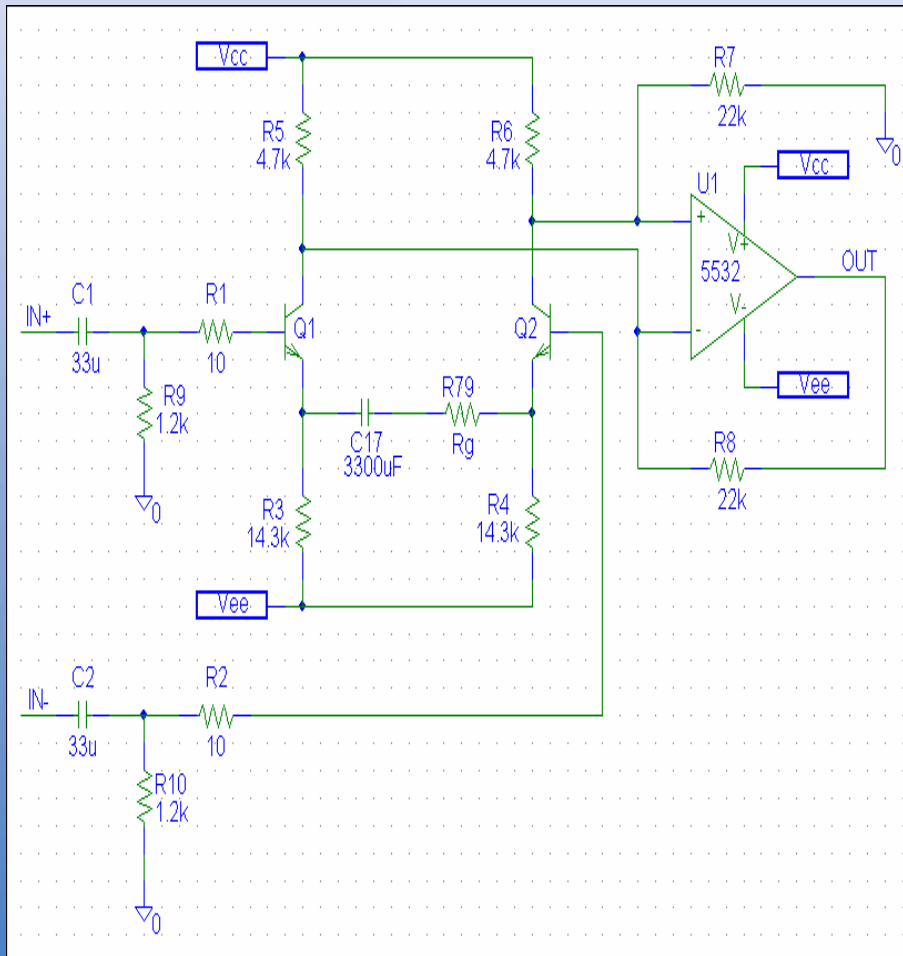


- CM to differential conversion can occur due to mismatches in:
- R_3 and R_4
- R_5 and R_6
- R_7 and R_8
- R_9 and R_{10}
- Q_1 and Q_2


Simple Mic Preamp

- 2 Transistors and 1 Opamp
- Very Low Cost
- Marginal Performance

Complementary Feedback Pair Mic Preamp

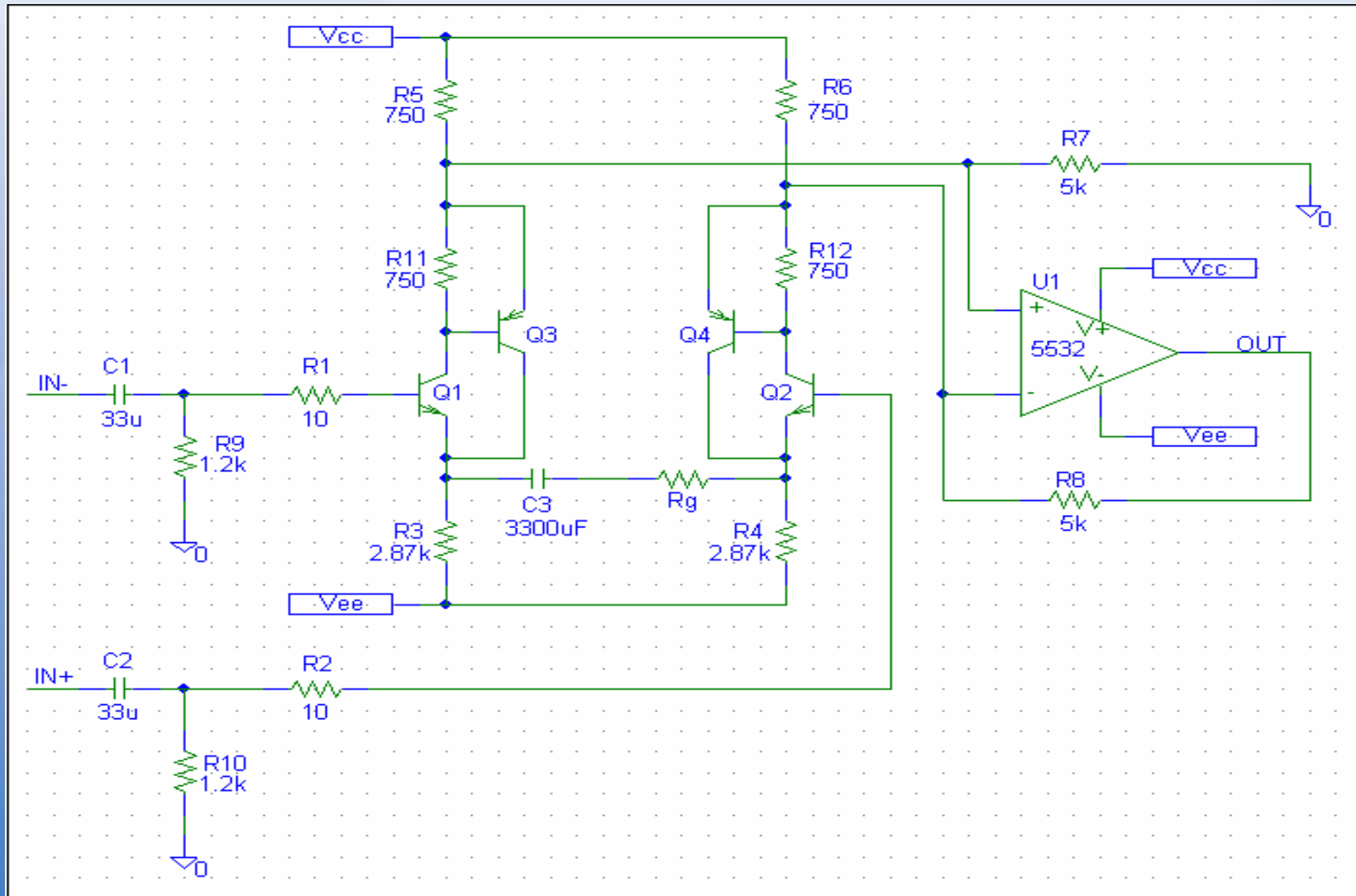


CFP Mic Preamp

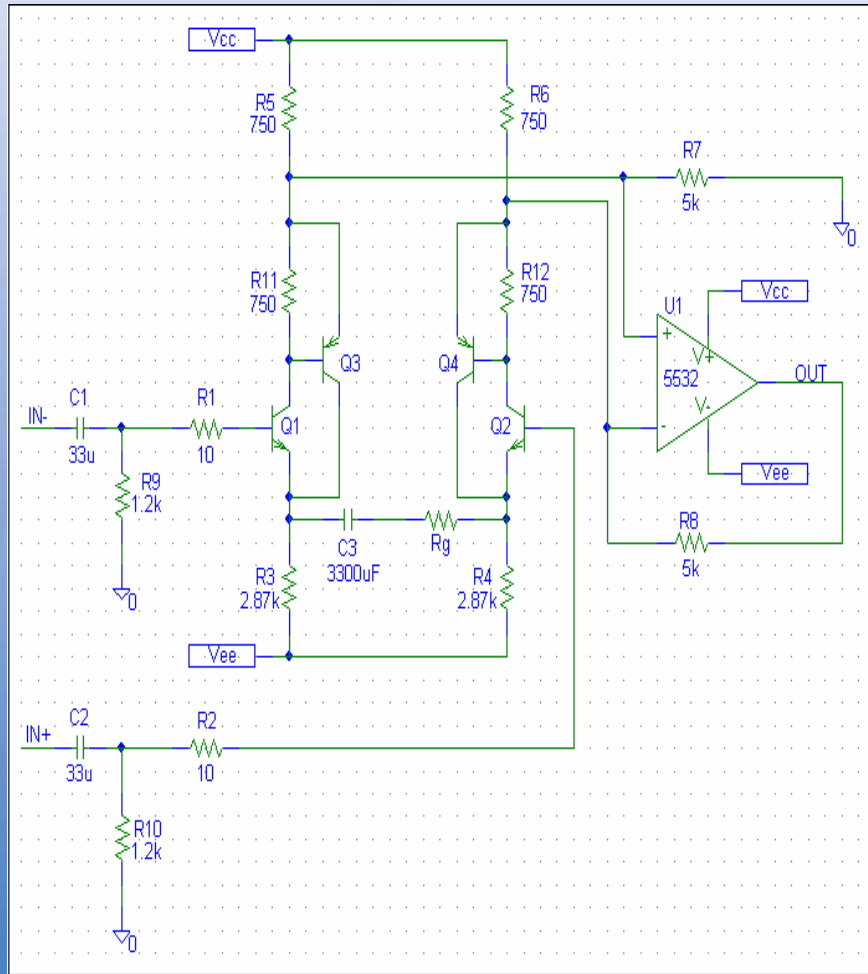

- Input devices are each a compound transistor (Complementary Feedback Pair)
- NPN Input I_c set by $V_{be}/750$ ohms (1 mA each)
- NPN I_c + PNP I_c set by $(|V_{ee}| - V_{be})/2k87$ (5 mA per side)


CFP Mic Preamp

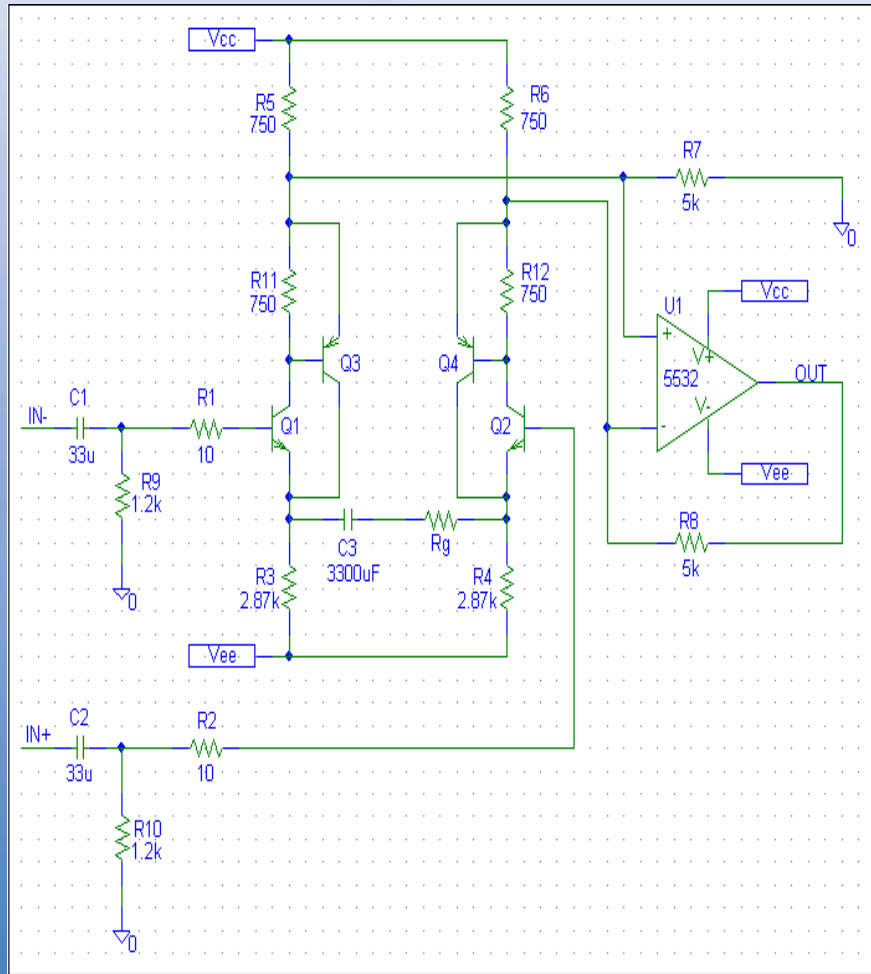


- Output impedance at NPN emitters is now:
$$r_o = \frac{1}{g_m(1+\beta_{PNP} \cdot \frac{R_{11}}{r_{\pi PNP} + R_{11}})}$$
- Still current dependent, but much lower
- Gain = $5k / (r_e / 74 + R_g / 2 || 2.87k)$
- Minimum Gain = $5k / 2.87k = 4.8 \text{ dB}$

THD Performance of CFP Mic Preamp

THD vs. Gain, 1 kHz, +20 dBu Out

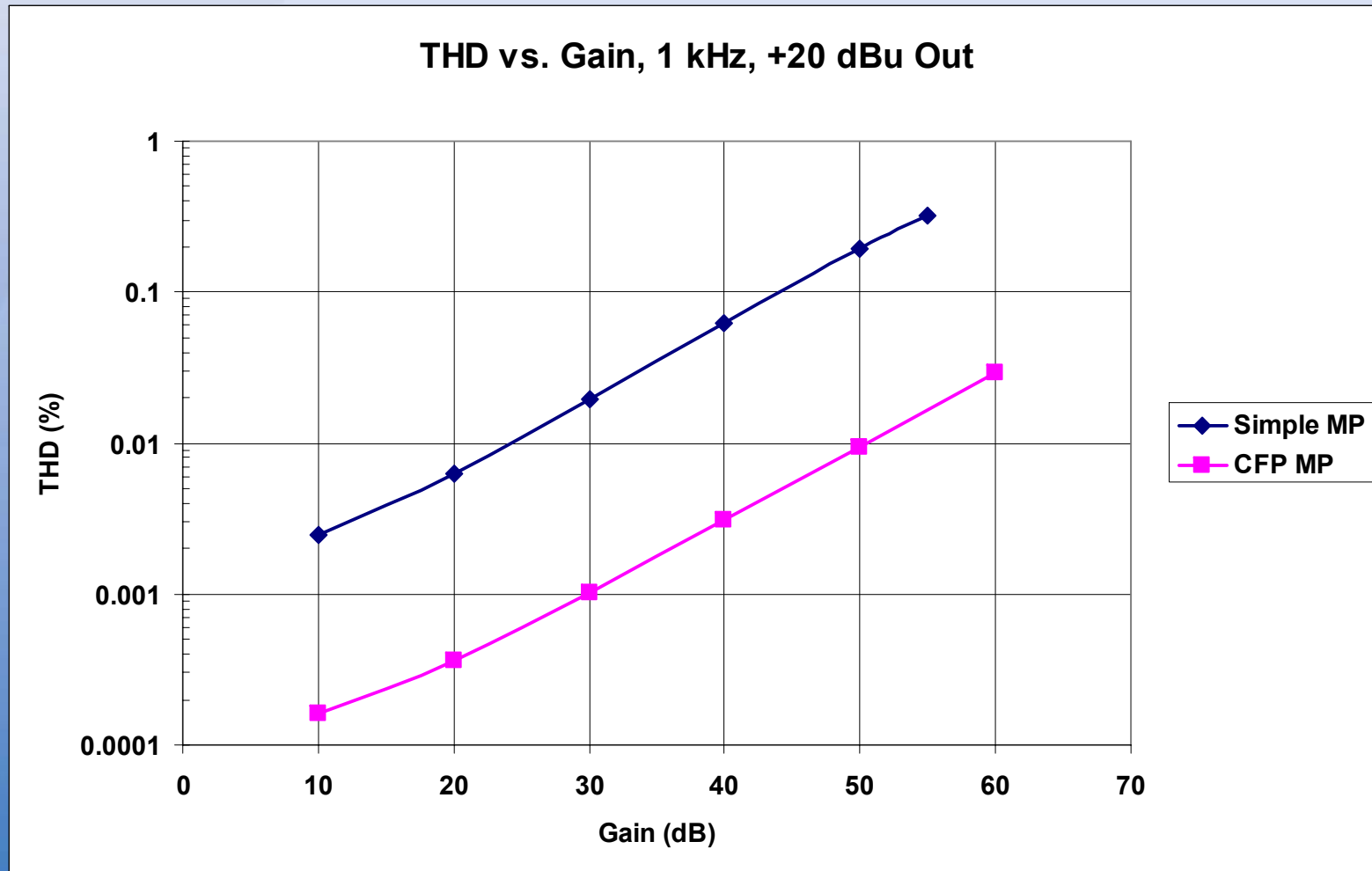


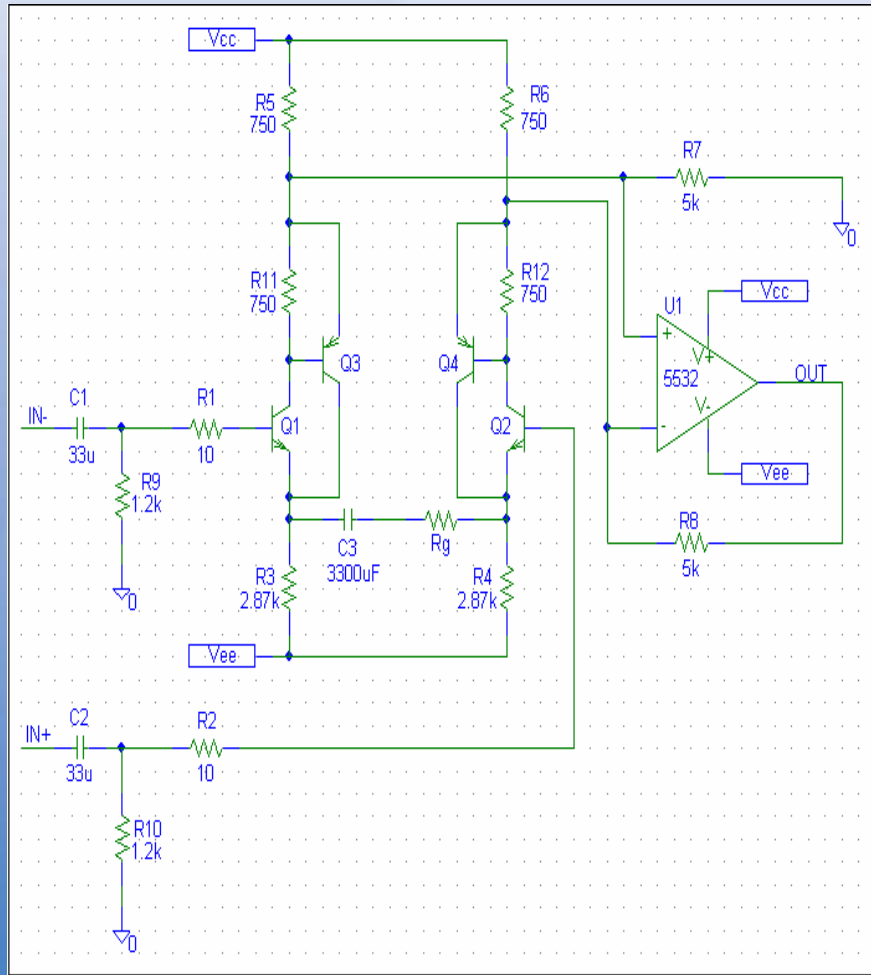High-Gain Noise Sources of CFP Mic Preamp




- Input noise at high gains dominated by:
- $Q_1, Q_2 I_C$ Shot Noise
(RTI) = $\frac{2\sqrt{qI_C}}{g_m} = \sqrt{4kTr_e}$
- $Q_1, Q_2 r_b$ Thermal Noise = $\sqrt{8kTr_b}$
- R_1, R_2, R_g Thermal Noise = $\sqrt{4kT(R_1 + R_2 + R_g)}$

Low-Gain Noise Sources of CFP Mic Preamp

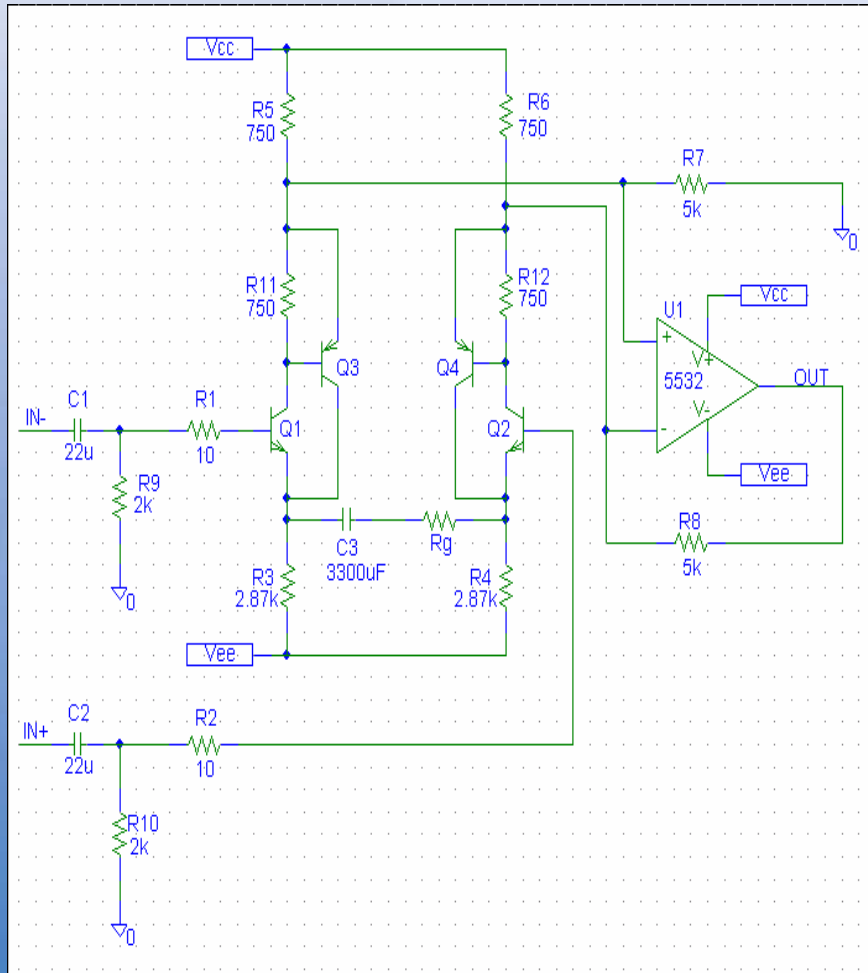


- Input noise at low gains dominated by:
- Thermal Noise of R_5 and R_6
- EIN of U1
- Thermal Noise of $R_g \parallel (R_3 + R_4)$
- $Q_1, Q_2 I_B$ shot noise across $\frac{R_g \parallel (R_3 + R_4)}{2}$

Noise Performance of CFP Mic Preamp

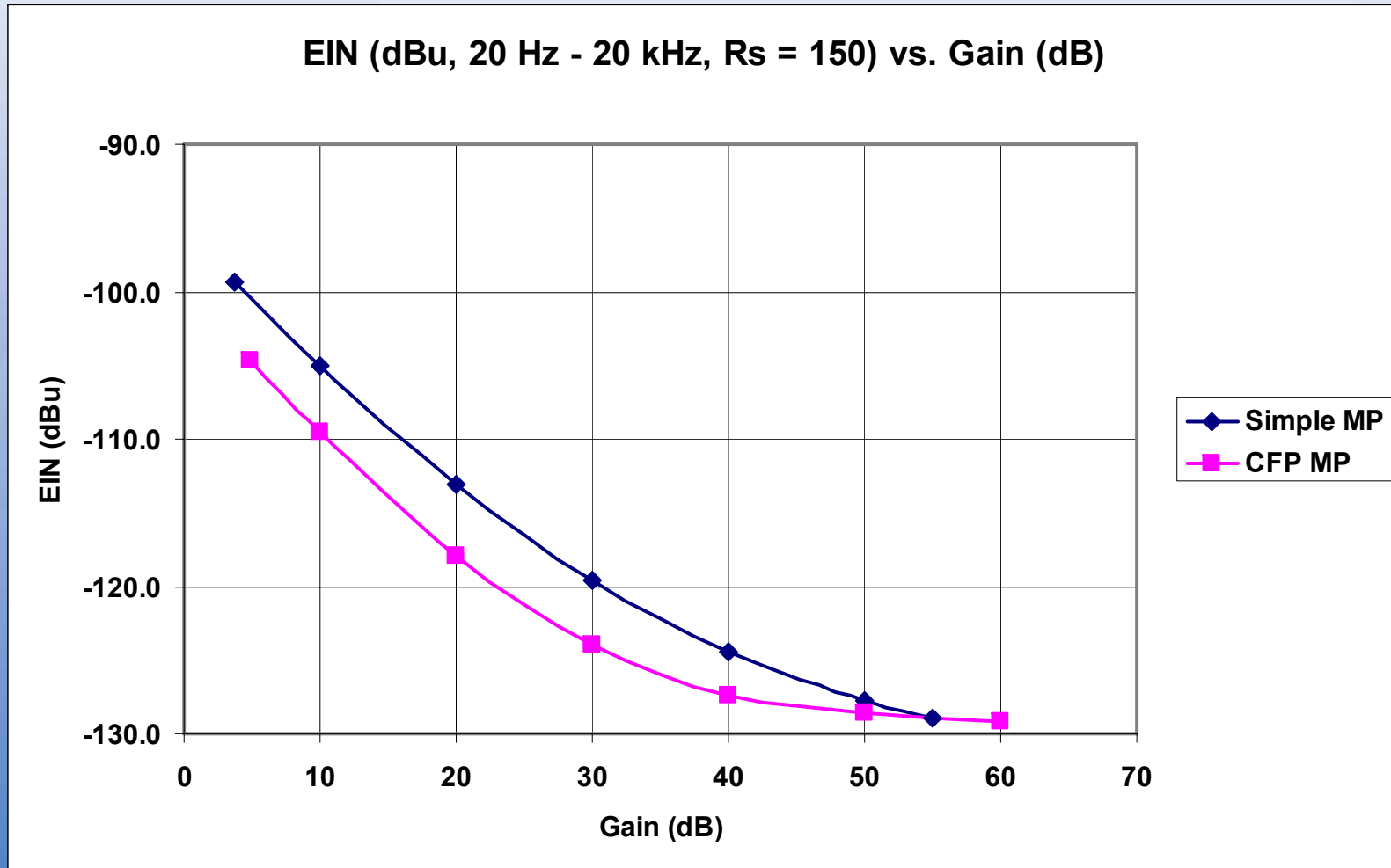

CMRR Performance of CFP Mic Preamp

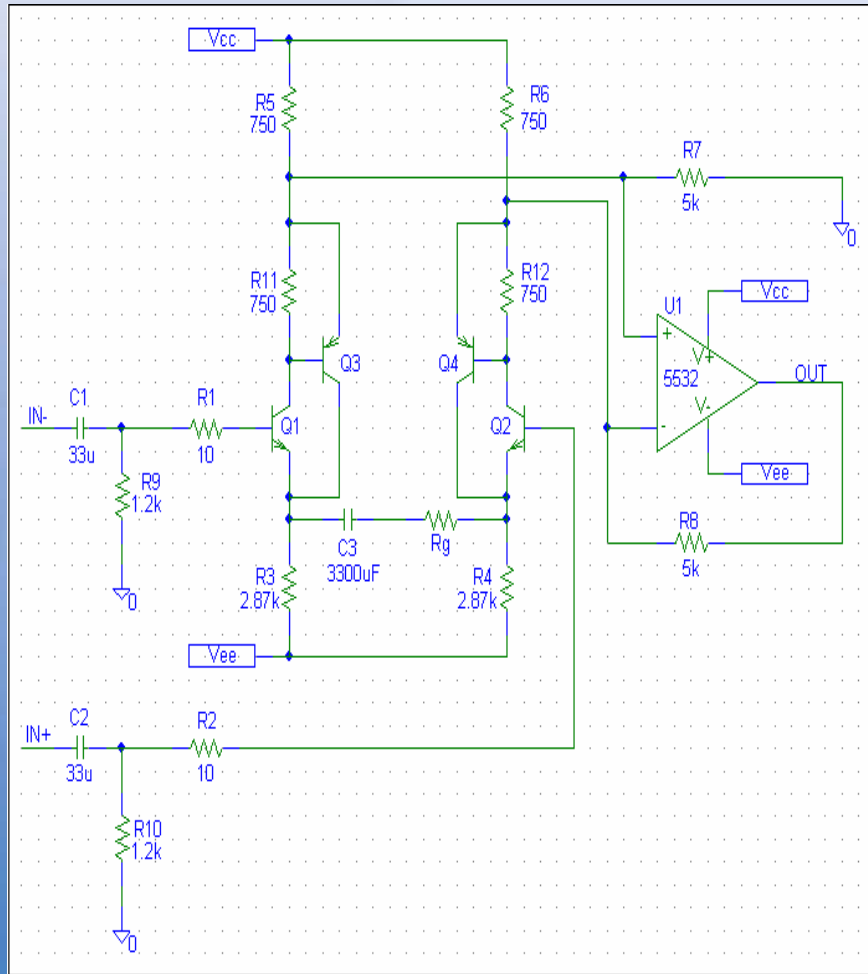

- CM to Diff conversion can occur due to mismatches in:
- R_3 and R_4
- R_5 and R_6
- R_7 and R_8
- R_9 and R_{10}
- R_{11} and R_{12}


CFP Mic Preamp

- Performance is improved over Simple Mic Preamp
- Distortion performance still not terrific at high gains
- Power consumption is high to get that performance
- Cost is modest


Current Feedback Instrumentation Amp

- Topology used in most integrated mic preamp ICs including ADI - SSM2019, TI - INA103, INA163, INA217, THAT – 1510, 1512, 1570 and possibly others
- Scott Wurcer – AD524 IEEE Paper 12/82
- Graeme Cohen AES Paper – “Double Balanced Microphone Amplifier” 9/84

Basic CFIA Mic Preamp Schematic

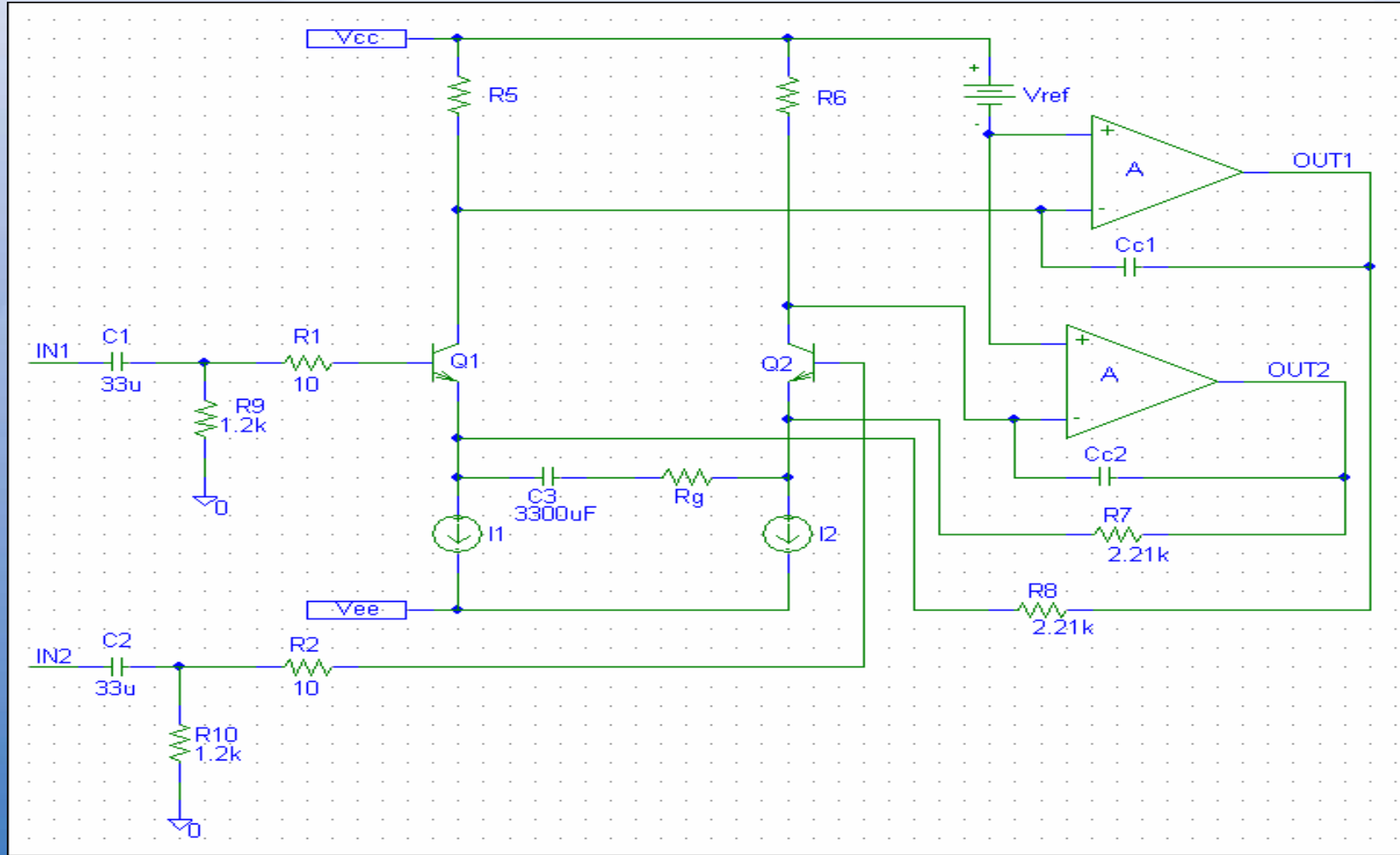


Basic CFIA Mic Preamp

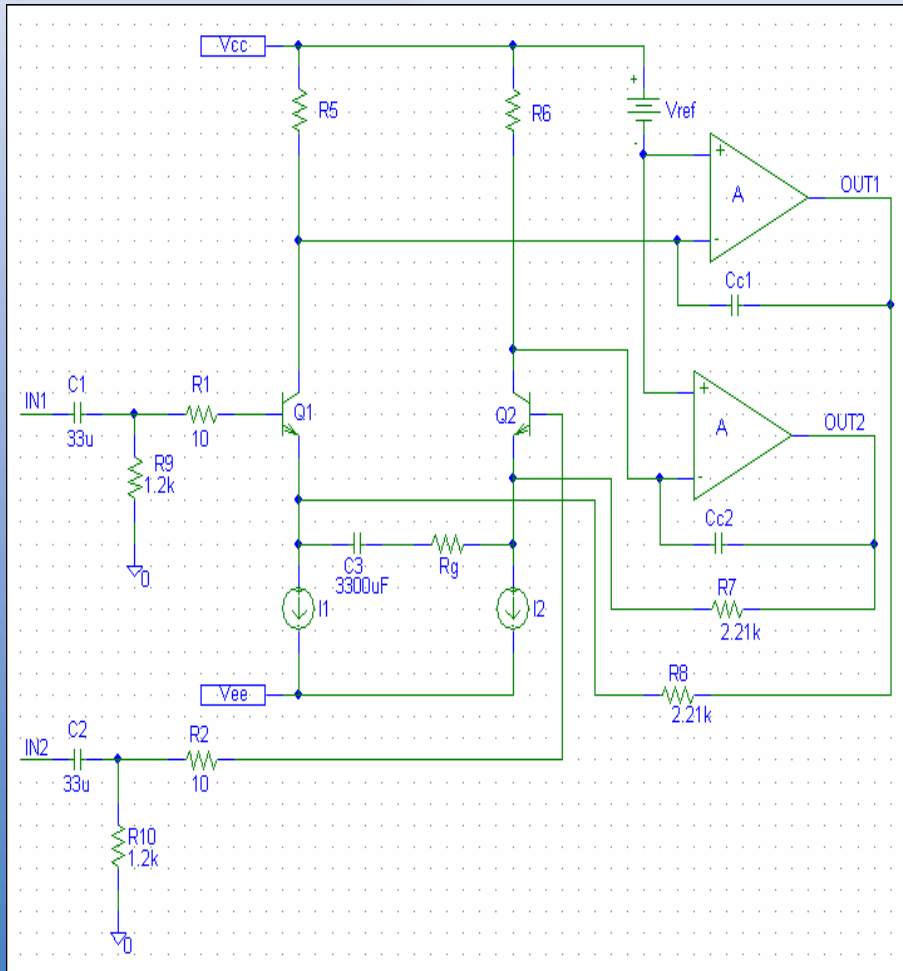


- Input Transistor $I_c = V_{ref}/R_5$
- Current Sources I_1 and I_2 are for “bias current cancellation” only
- Gain = $1 + (2R_7/R_g)$
- Min. gain = 0 dB

What's "Current Feedback"?

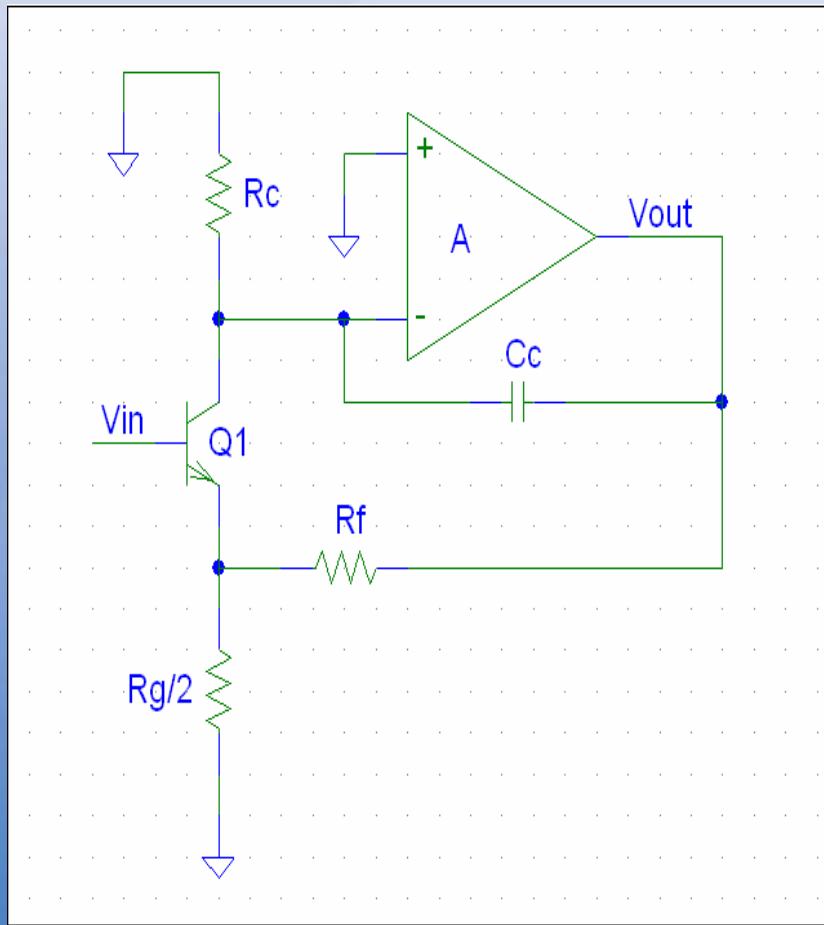

- Closed loop bandwidth stays substantially constant with closed loop gain until r_e becomes a significant factor
- C_c charging current is not limited

“Half Circuit” of CFIA

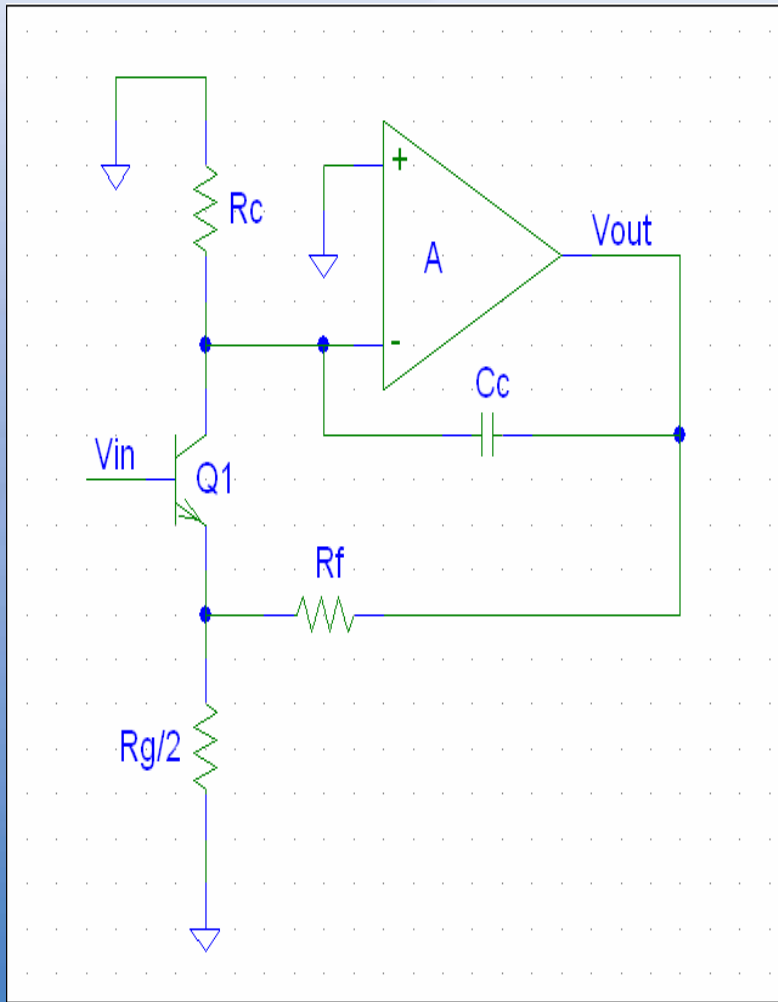

$$\frac{V_{out}}{V_{in}} = \frac{R_C \cdot A}{1 + \frac{[r_e + (R_F \parallel R_G/2)](R_C C_M S + 1)}{R_C \cdot A} \cdot \frac{R_G}{2R_F + R_G}} = \frac{A}{1 + A\beta}$$


Where $C_M = C_C(A+1)$, $r_e = 1/g_m$

For $r_e \ll (R_F \parallel R_G/2)$:

$$\frac{V_{out}}{V_{in}} = \frac{R_C \cdot A}{1 + \frac{(R_F \parallel R_G/2)(R_C C_M S + 1)}{R_F(R_C C_M S + 1)}} = \frac{A}{1 + A\beta}$$


Note that the loop transmission $A\beta$ is independent of the closed loop gain if r_e is much less than the feedback network impedance

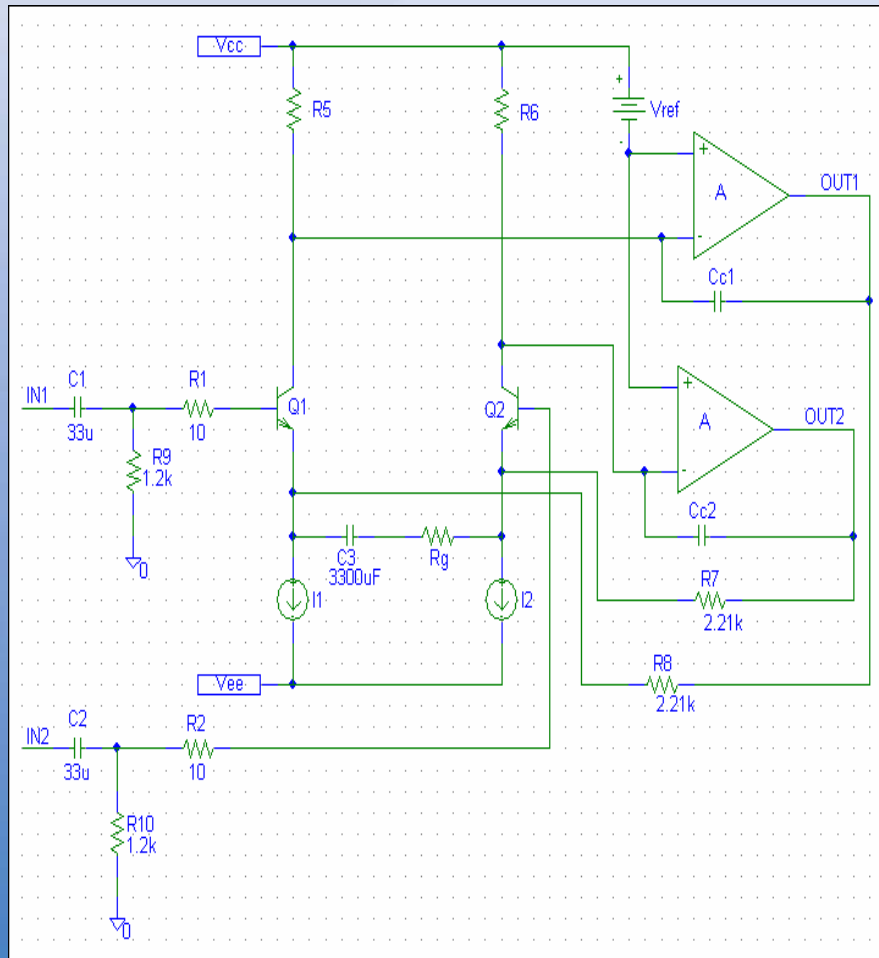High-Gain Noise Sources of CFIA Mic Preamp




- Input noise at high gains dominated by:
- $Q_1, Q_2 I_C$ Shot Noise
(RTI) = $\frac{2\sqrt{qI_C}}{g_m} = \sqrt{4kTr_e}$
- $Q_1, Q_2 r_b$ Thermal Noise = $\sqrt{8kTr_b}$
- R_1, R_2, R_g Thermal Noise = $\sqrt{4kT(R_1 + R_2 + R_g)}$

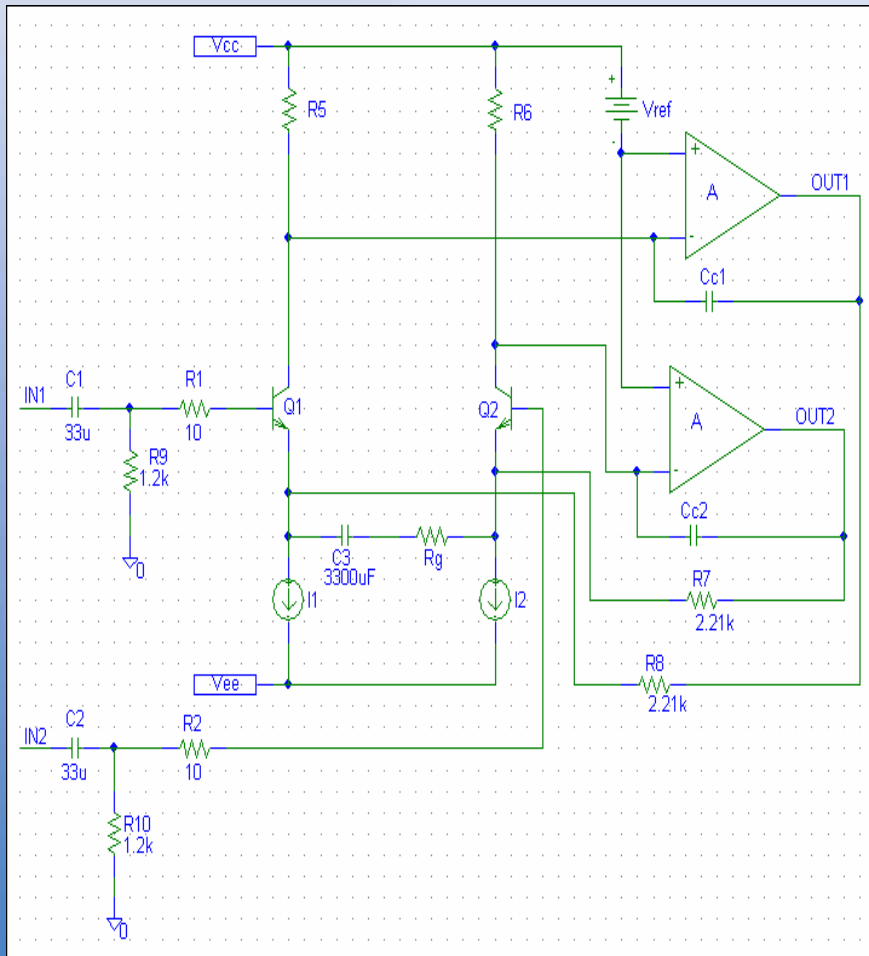Low-Gain Noise Sources of CFIA Mic Preamp




- Input noise at low gains dominated by:
- Thermal Noise of R_5, R_6
- Noise of I_1, I_2
- Thermal Noise of $R_g \parallel (R_7 + R_8)$
- $Q_1, Q_2 I_B$ shot noise across $\frac{R_g \parallel (R_7 + R_8)}{2}$
- EIN of U1, U2

CMRR Performance of CFIA Mic Preamp

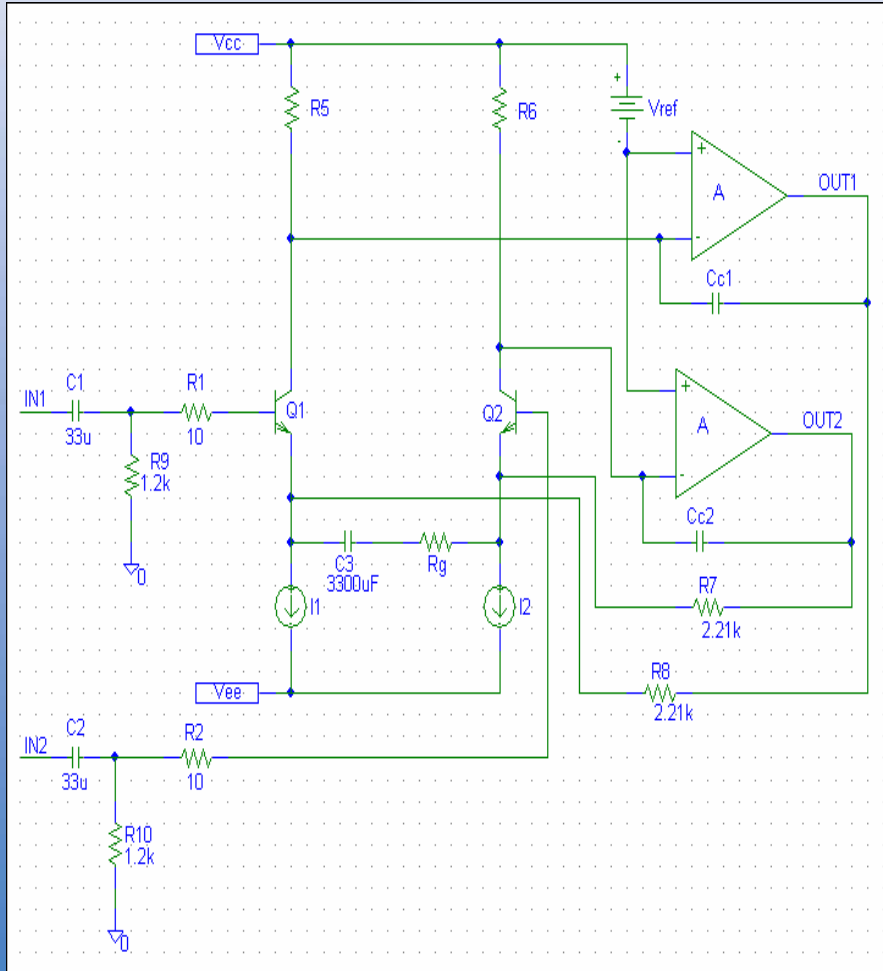


- Unity CM Gain to OUT1 – OUT2
- CMRR = Differential Gain
- CM to Diff conversion can occur due to mismatches in transistors

Refinements to the CFIA

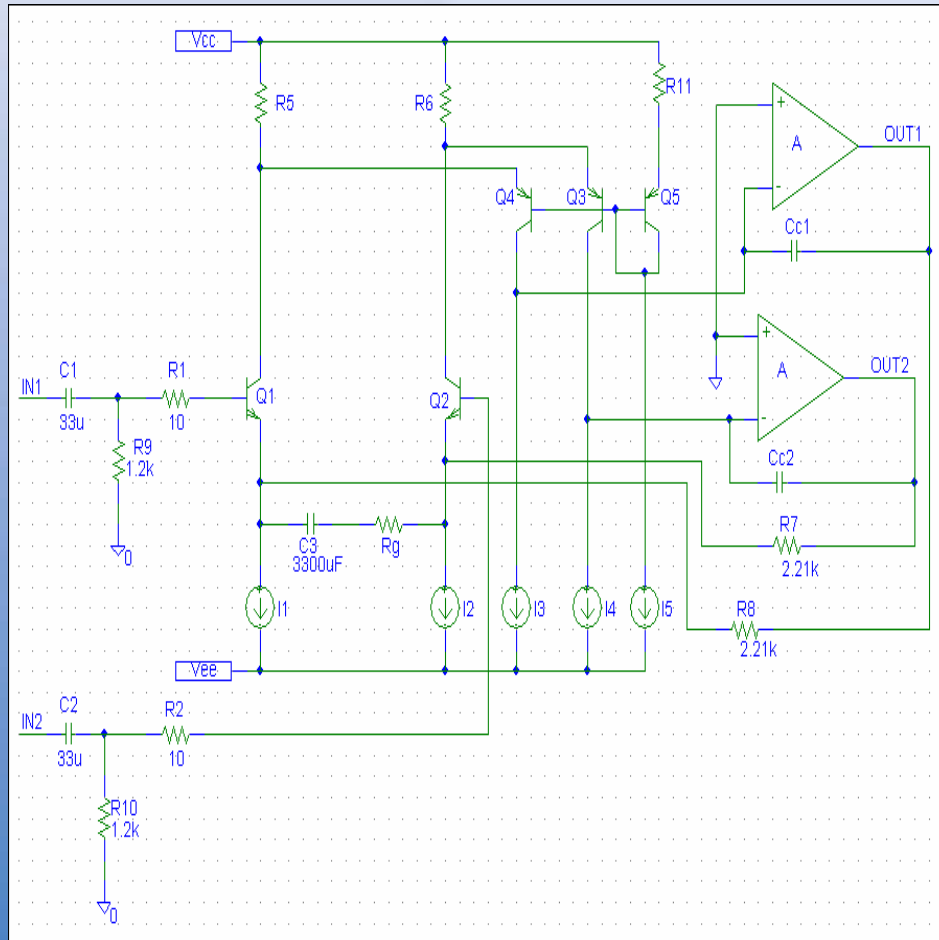


- Early effect and Ccb mismatch in the current source transistors can also contribute to THD at low gains
- Cascoding helps here at the expense of some input CM range
- A Folded Cascode can minimize the noise contribution of the integrator stages and R_5 and R_6 while minimizing the impact on input CM range
- At this level of complexity an IC makes sense and the good device matching helps performance

A Real Example THAT's 1570 CFIA

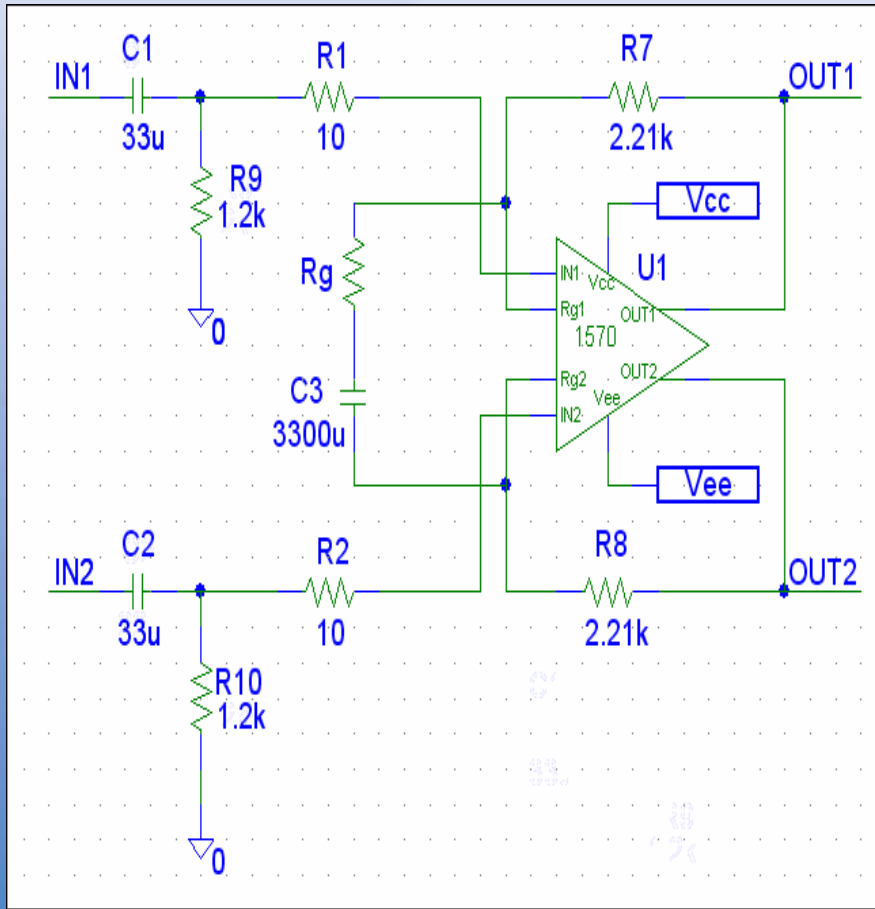


- An integrated circuit current-feedback instrumentation amplifier front end
- Utilizes the techniques described on the previous slide.
- Compensated for R_F values down to 2 kohm

1570 Bandwidth vs. Gain

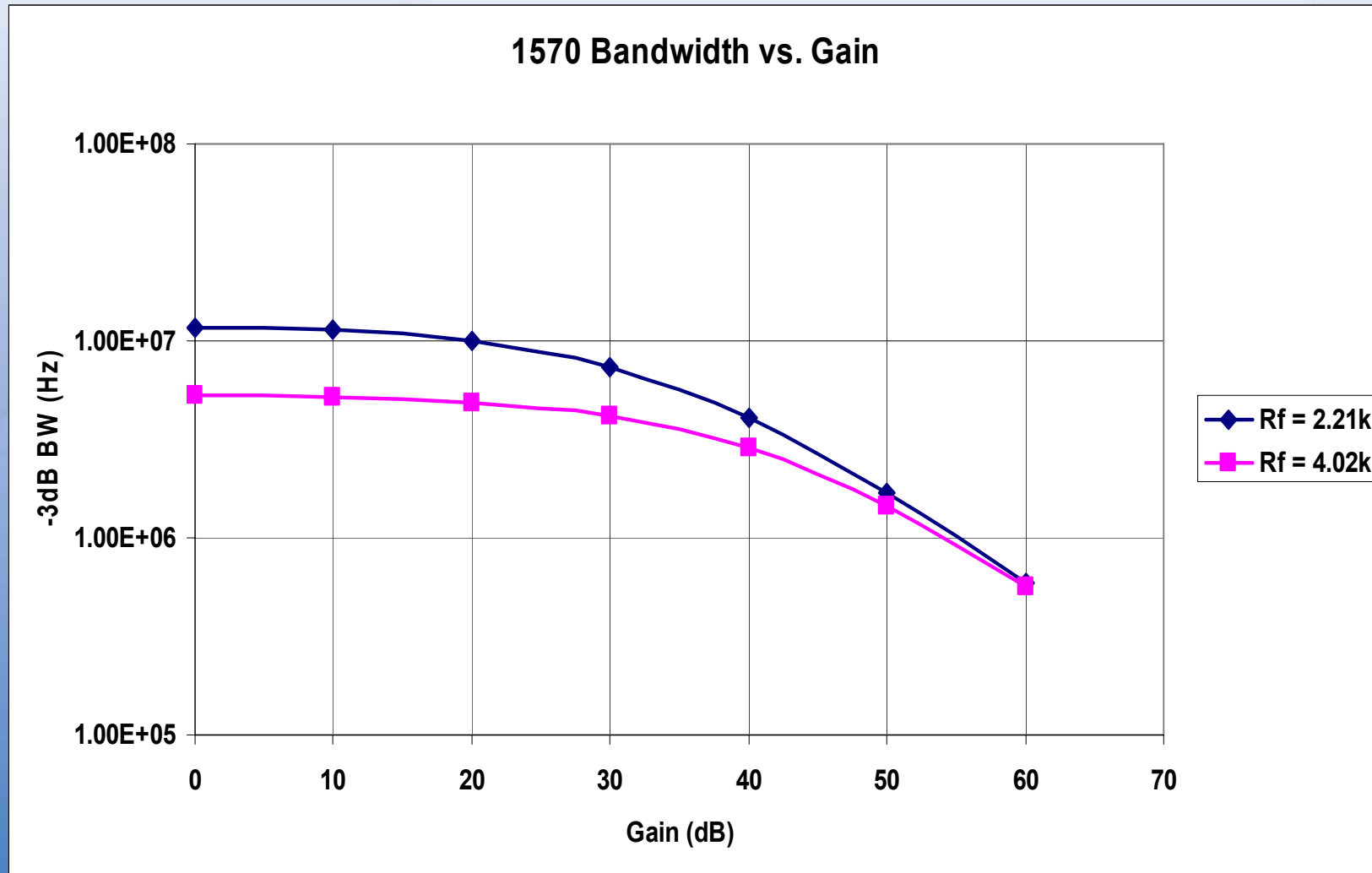


THD Performance of 1570 Mic Preamp


THD vs. Gain, +20 dBu Out, $R_f = 2.21k$

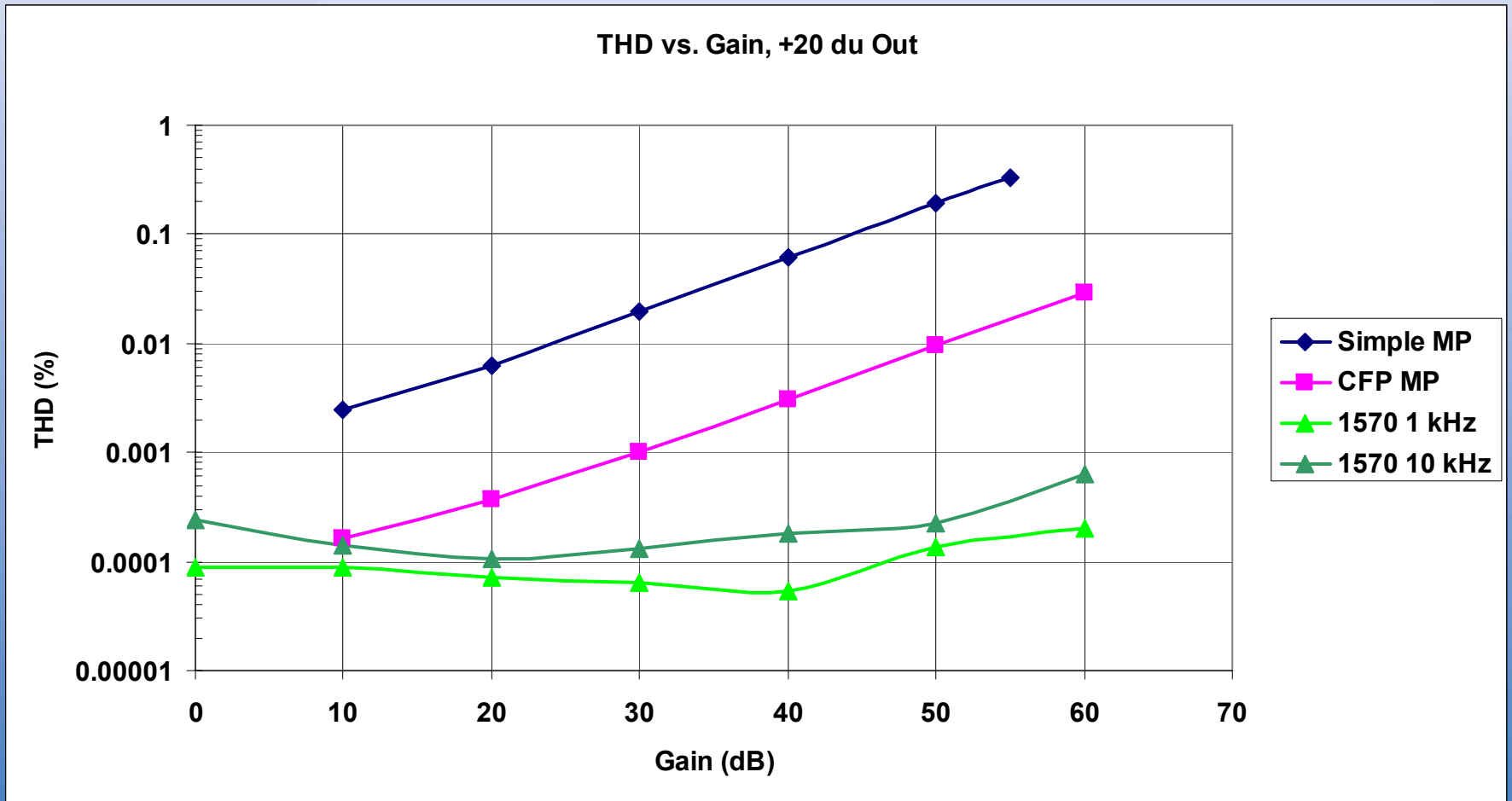

Noise Performance of 1570

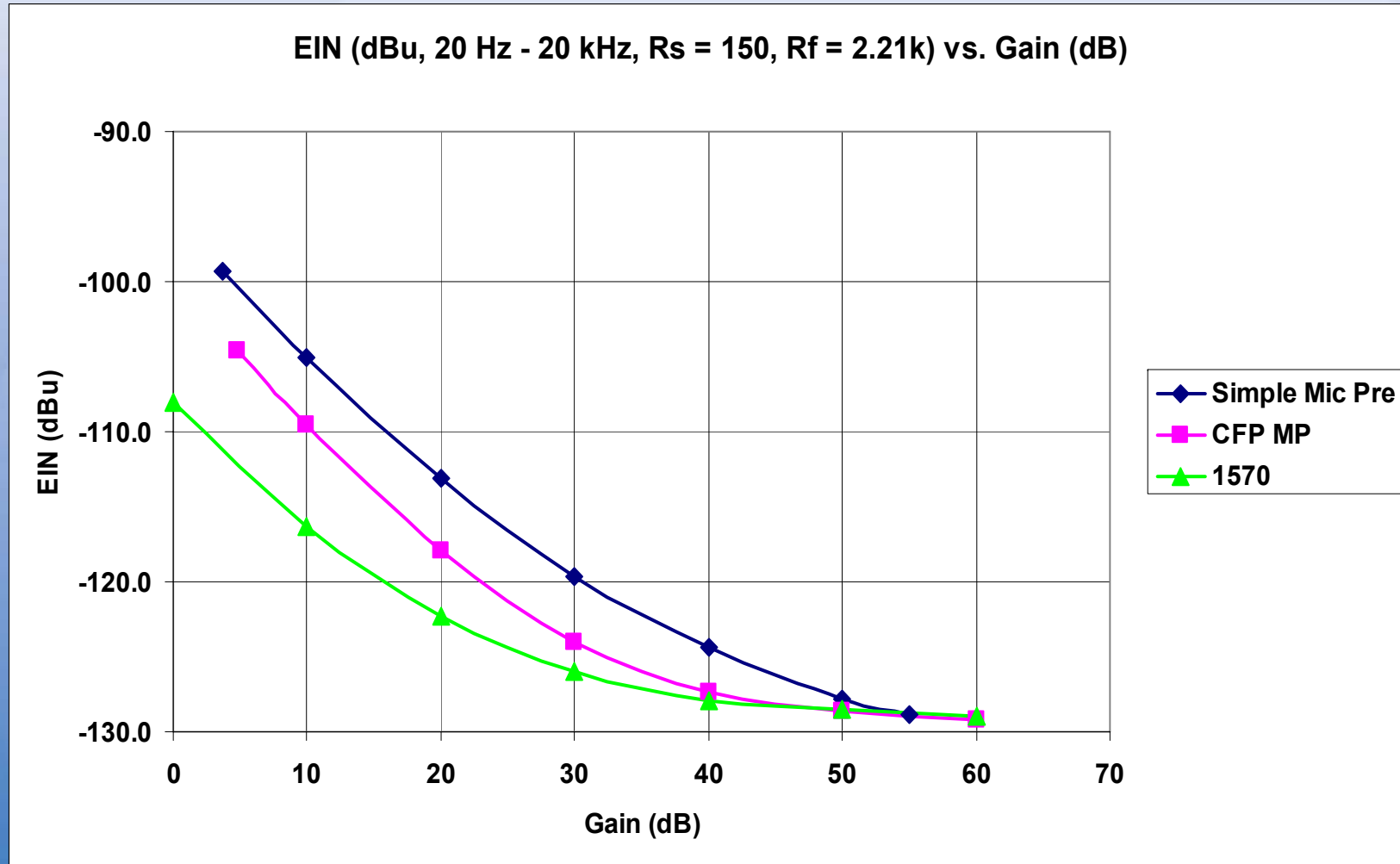


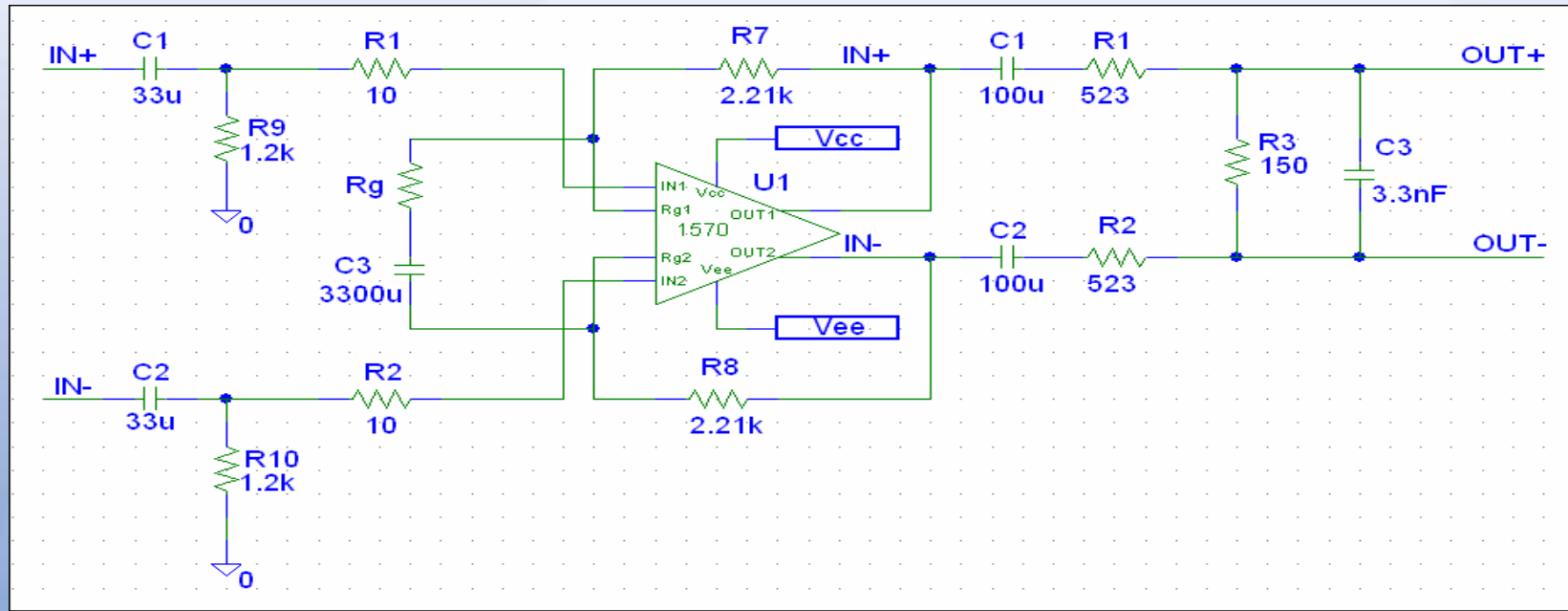Utilizing the Differential Output to Drive A/D Converters




- The cheap and simple way:
- Rely on the A/D converter for CMRR at low gains
- Converter CM input range might be an issue as the pad does not attenuate CM signals

Birt Circuit

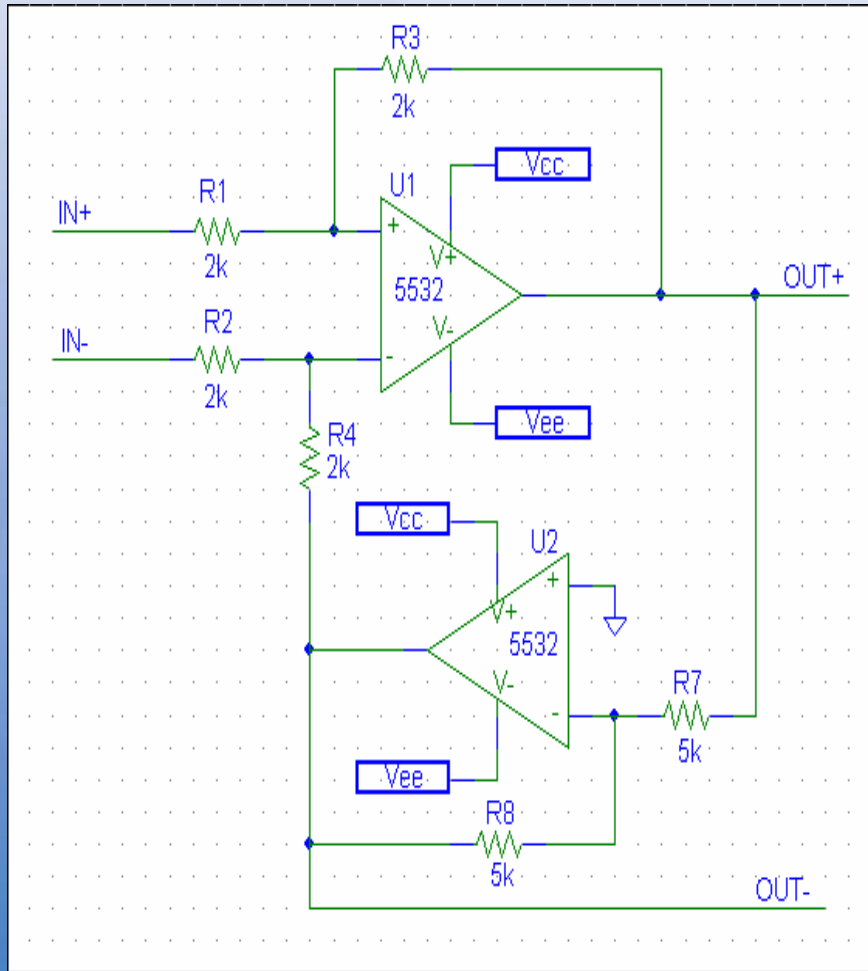


- David Birt, 1990
- Provides CMRR
- Gain = R_3/R_1
- Provides a convenient input for a CM DC reference voltage
- U2 input offset and noise appear as CM at $OUT+ - OUT-$

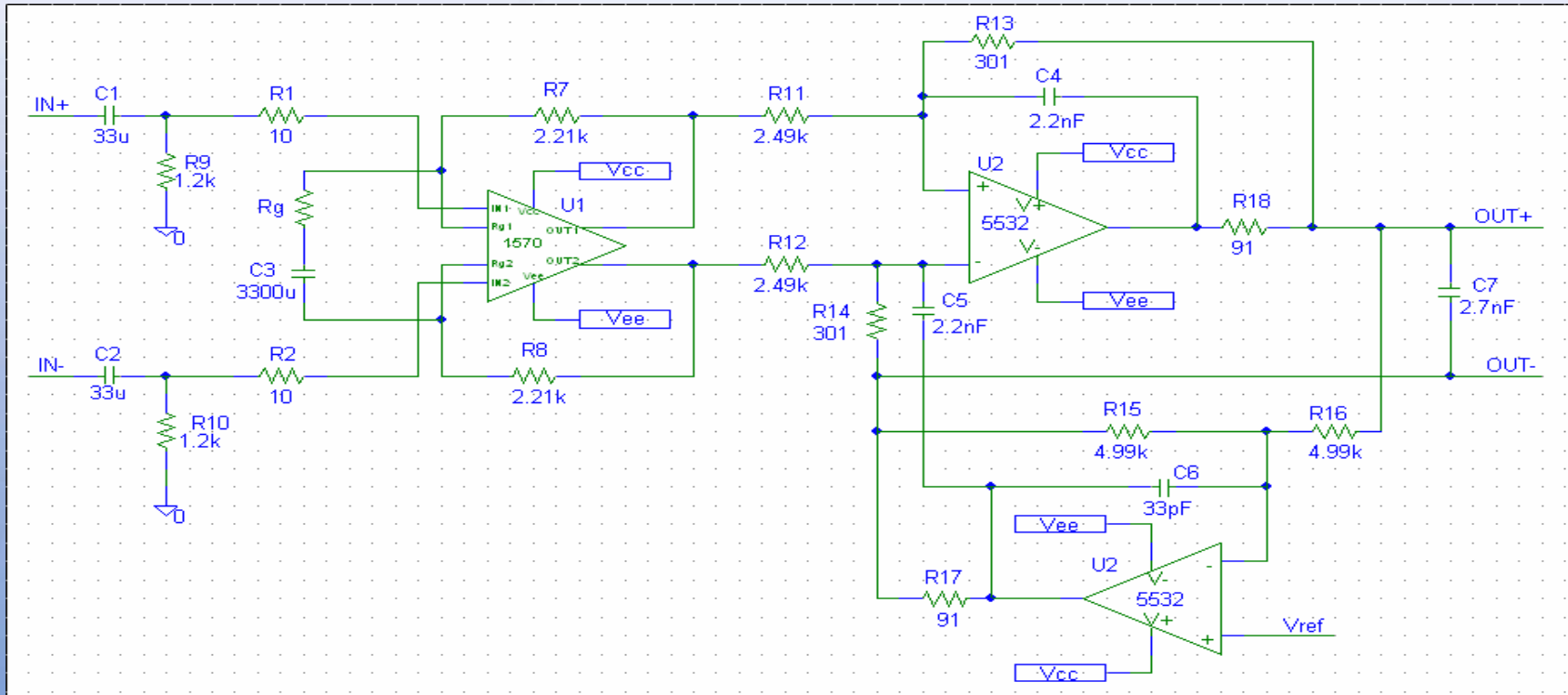Birt Circuit Applied to 1570 and A/D Drive




- The resistor ratios provide 18 dB of attenuation before the A/D
- The feedback networks enable capacitive load driving with low audio-band output impedance

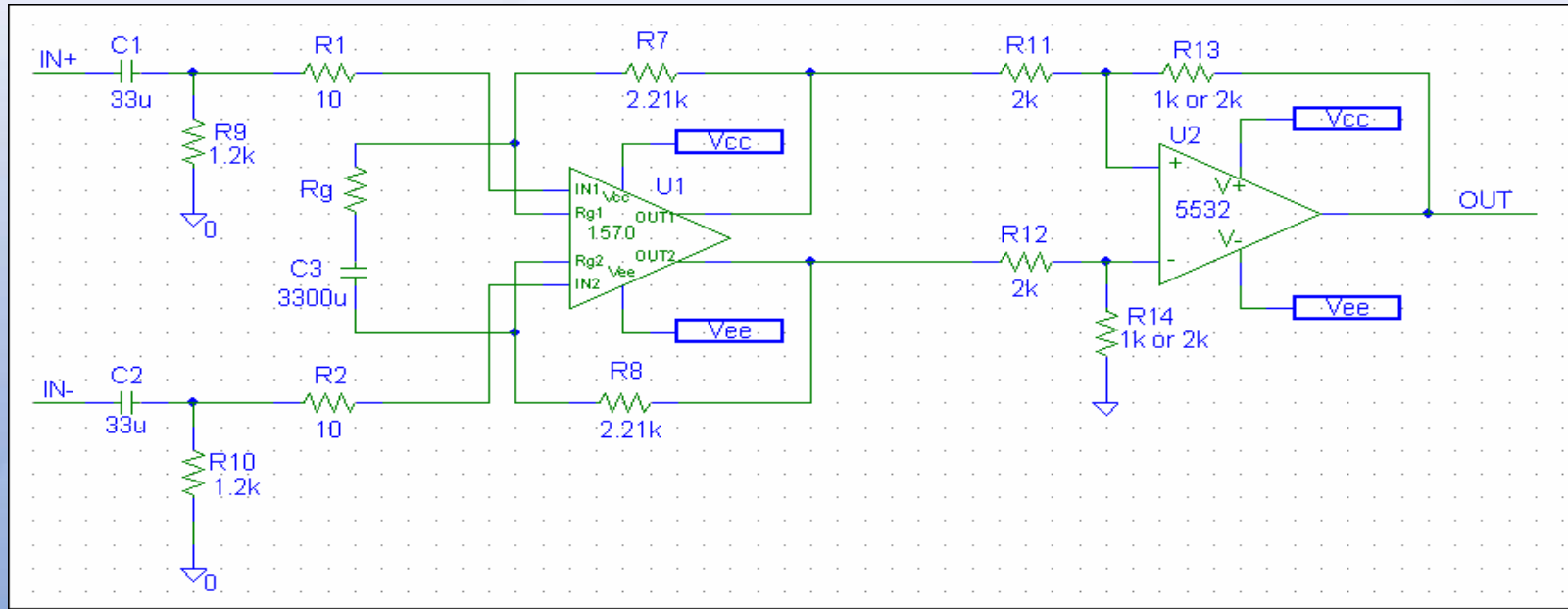Converting Differential Output to Single-Ended




- The traditional 4-resistor differential amplifier works fine
- At low gains, the noise of this stage can become important
- Resistor matching controls the CMRR

Differential to Single-Ended Conversion

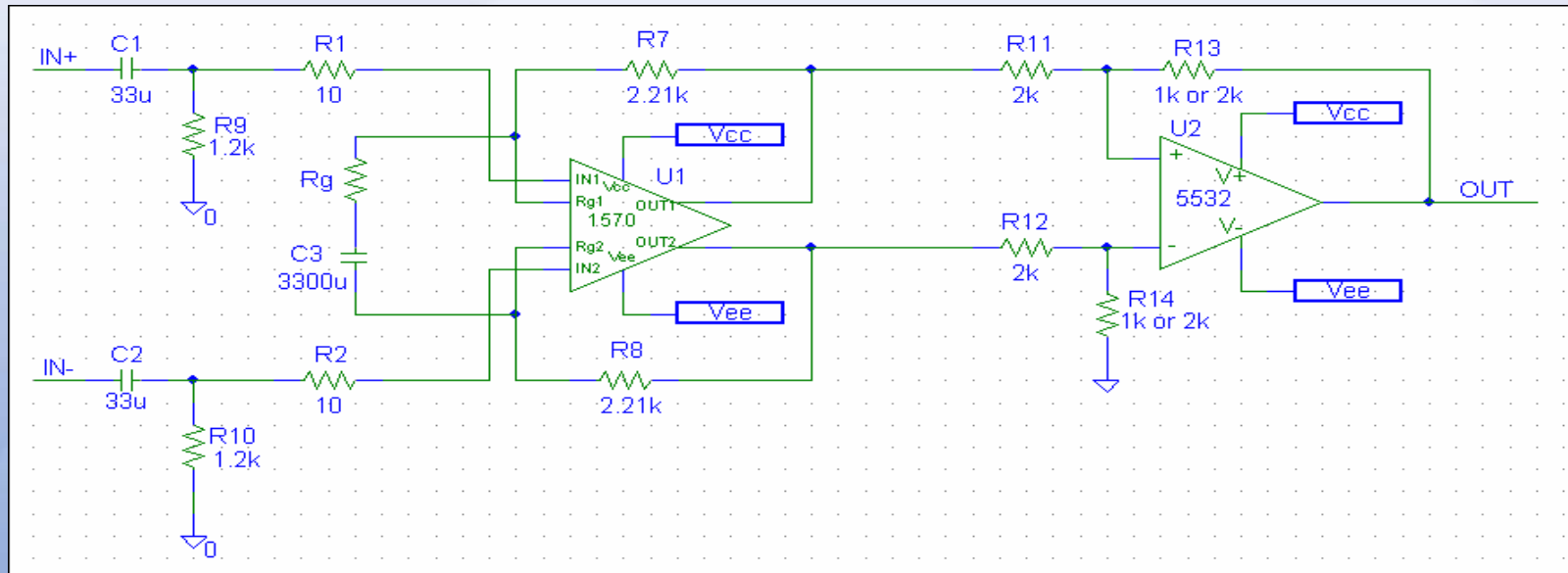

- What should the gain of the diff amp be?
- If $G=1$, we leave headroom on the table
- If $G=.5$, we take advantage of all of the swing capability of the differential output
- For the case of $G=.5$, the front end gain is always 6 db higher

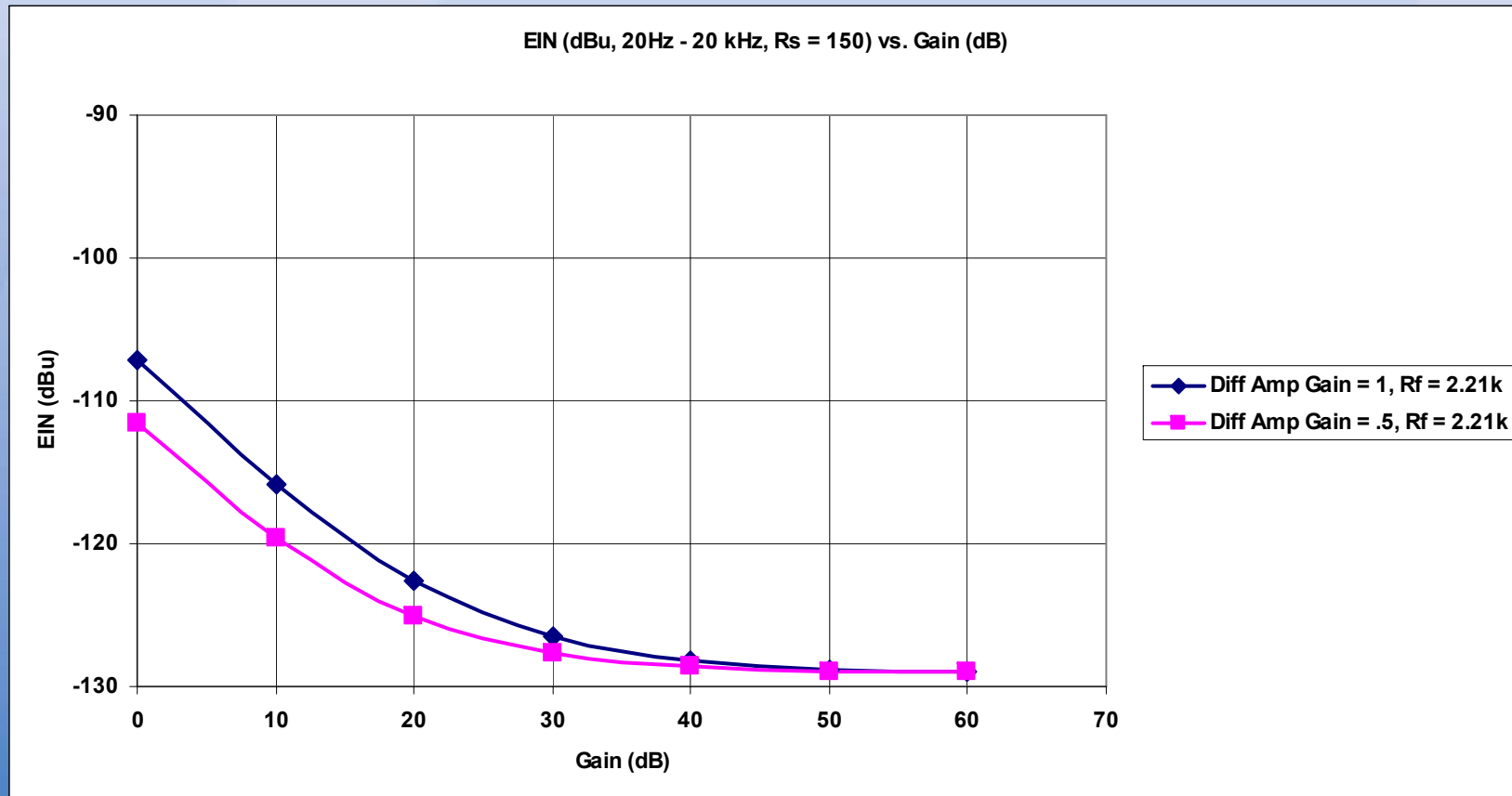1570 + Differential Amplifier Noise vs. Gain Performance



Conclusions

- Microphone preamplifiers with a wide gain range controlled by a single resistance involve tradeoffs between low-gain noise and high-gain distortion performance
- The current-feedback instrumentation amplifier is capable of good performance at both extremes
- An integrated approach can provide excellent performance in very small PCB area at moderate cost

Amplifier References

- David Birt, “Electronically Balanced Analogue-Line Interfaces,”
Proceedings of the Institute of Acoustics, Vol. 12, Part 8 (1990)**
- Graeme John Cohen, “Double Balanced Microphone Amplifier”, 1984
Audio Engineering Society Australian Regional Convention, Preprint
Number 2106, September 1984**
- Graeme John Cohen, “Microphone Amplifier History and Design”,
presented at the Audio Engineering Society Adelaide Section, August,
2006**
- Fred Floru, “An Improved Microphone Preamplifier Integrated Circuit”,
2001 Audio Engineering Society 16th UK Conference on Silicon For
Audio**
- Scott Wurcer, “A Programmable Instrumentation Amplifier for 12-Bit
Sources”, IEEE Journal of Solid-State Circuits, Volume SC-17, Number
6, December, 1982**

Acknowledgements

**Thanks to Steve Green for preparing the
“Support Circuitry” section.**

**Thanks to Greg Benulis, Rosalfonso Bortoni,
Fred Floru, Bob Moses, and Les Tyler for their
assistance in the preparation of this tutorial**

Questions ?

THAT Corporation