
Digital VLSI Architectures:

Pipelining & Parallel Processing

Mahdi Shabany

Sharif University of Technology




Architectural Techniques : Critical Path

❑ Critical path in any design is the longest path between

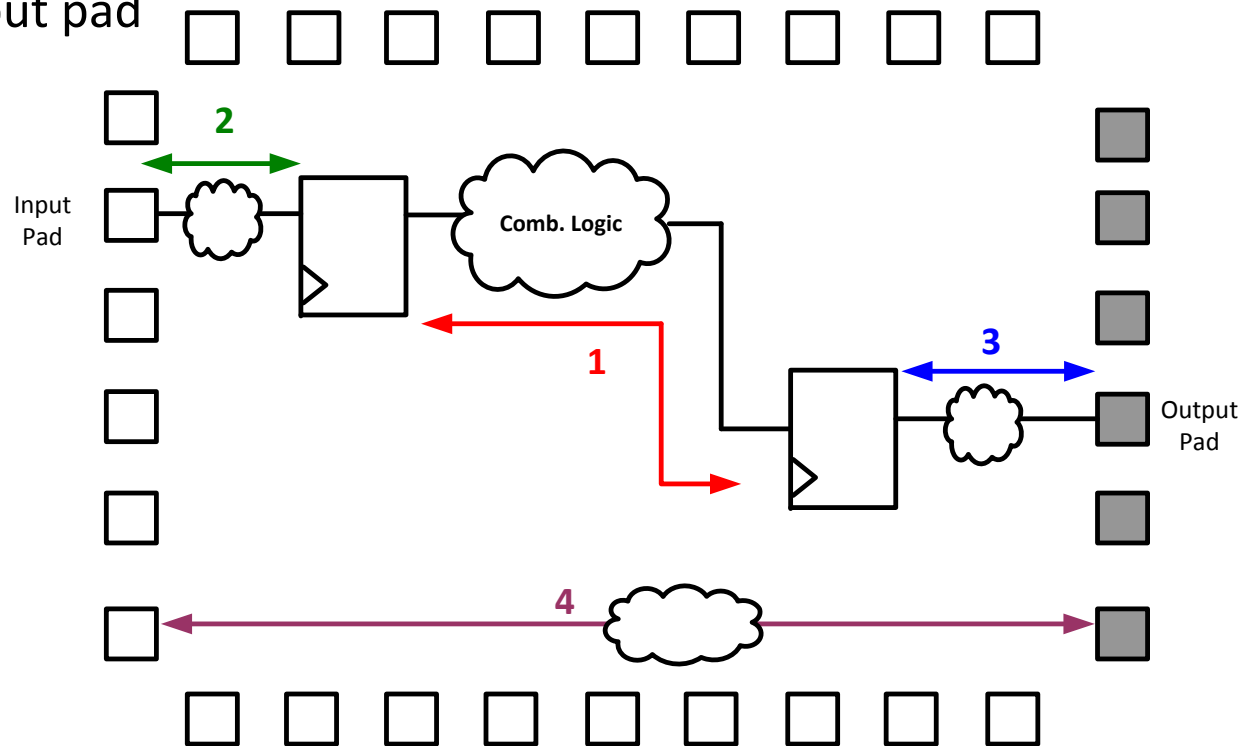1. Any two internal latches/flip-flops
2. An input pad and an internal latch
3. An internal latch and an output pad
4. An input pad and an output pad

Use FFs right after/before input/out pads to avoid the last three cases (off-chip and packaging delay)

The maximum delay between any two sequential elements in a design will determine the max clock speed



Digital Design Metrics

- Three primary physical characteristics of a digital design:
 - **Speed**
 - Throughput
 - Latency
 - Timing
 - **Area**
 - **Power**



Digital Design Metrics

□ Speed

➤ Throughput :

- The amount of data that is processed per clock cycle (bits per second)

➤ Latency

- The time between data input and processed data output (clock cycle)

➤ Timing

- The logic delays between sequential elements (clock period)
- When a design does not meet the timing it means the delay of the critical path is greater than the target clock period



Maximum Clock Frequency: Critical Path

□ Maximum Clock Frequency:

$$F_{\max} = \frac{1}{T_{\text{clk-q}} + T_{\text{logic}} + T_{\text{setup}} + T_{\text{routing}} - T_{\text{skew}}}$$


- $T_{\text{clk-q}}$: time from clock arrival until data arrives at Q
- T_{logic} : propagation delay through logic between flip-flops
- T_{routing} : routing delay between flip-flops
- T_{setup} : minimum time data must arrive at D before the next rising edge of clock
- T_{skew} : propagation delay of clock between the launch flip-flop and the capture flip-flop.



Pipelining (to Improve Throughput)

❑ Pipelining:

 - Comes from the idea of a water pipe: continue sending water without waiting the water in the pipe to be out
- Used to reduce the critical path of the design



❑ Advantageous:

- Reduction in the critical path
- Higher throughput (number of computed results in a give time)
- Increases the clock speed (or sampling speed)
- Reduces the power consumption at same speed



Architectural Techniques :Pipelining


□ Pipelining:

- Very similar to the assembly line in the auto industry
- The beauty of a pipelined design is that new data can begin processing before the prior data has finished, much like cars are processed on an assembly line.




Architectural Techniques : Pipelining

 - ❑ **Original System:** (Critical path = τ_1 Max operating freq: $f_1=1/\tau_1$)



- ❑ **Pipelined version:** (Critical path = τ_2 Max operating freq: $f_2=1/\tau_2$)

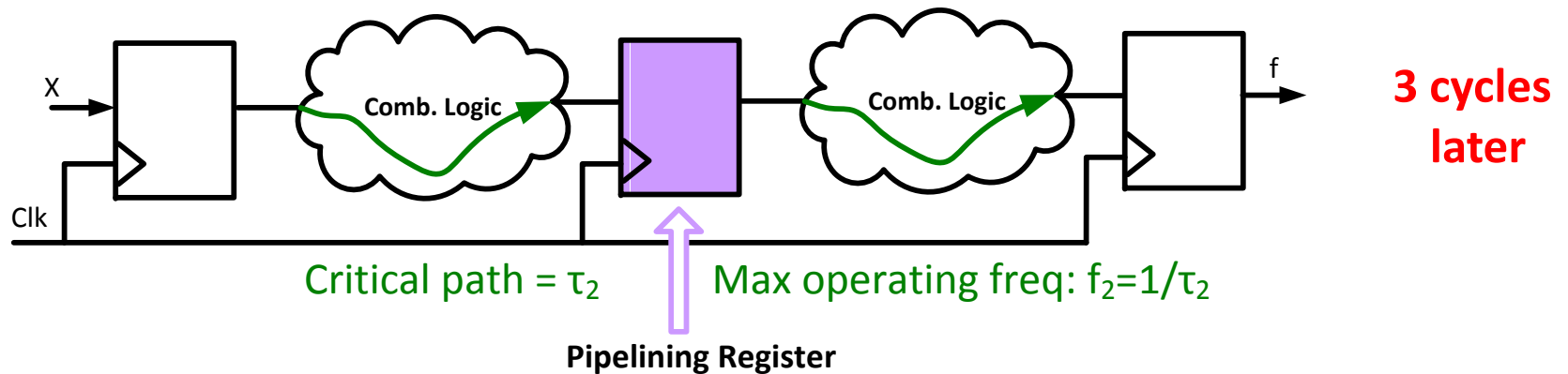
- ❑ Smaller Critical Path \longrightarrow higher throughput ($\tau_2 < \tau_1 \longrightarrow f_2 > f_1$)
- ❑ Longer latency



Architectural Techniques : Pipeline depth


□ Pipeline depth: 0 (No Pipeline)

➤ Critical path: 3 Adders

 

```
wire w1, w2;  
assign w1 = X + a;  
assign w2 = w1 + b;  
assign Y = w2 + c;
```


□ Latency : 0

 

Architectural Techniques : Pipeline depth


□ Pipeline depth: 1 (One Pipeline register Added)

➤ Critical path: 2 Adders

 

```
wire w1;  
reg w2;  
assign w1 = X + a;  
assign Y = w2 + c;  
  
always @(posedge Clk)  
w2 <= w1 + b;
```


□ Latency : 1

 

Architectural Techniques : Pipeline depth

□ Pipeline depth: 2 (One Pipeline register Added)


➤ Critical path: 1 Adder

 

```
reg w1, w2;  
assign Y = w2 + c;
```

```
always @(posedge Clk)  
begin  
    w1 <= X + a;  
    w2 <= w1 + b;  
end
```

□ Latency : 2

 


Architectural Techniques : Pipelining

□ Clock period and throughput as a function of pipeline depth:

➤ Clock period : $\tau_{\text{Clk}} \propto \frac{1}{n}$

➤ Throughput: $T \propto n$

 Adding register layers improves timing by dividing the critical path into two paths of smaller delay



Architectural Techniques : Pipelining

❑ General Rule:

- Pipelining latches can only be placed across **feed-forward cutsets** of the circuit.

❑ Cutset:

- A set of paths of a circuit such that if these paths are removed, the circuit becomes disjoint (i.e., two separate pieces)

❑ Feed-Forward Cutset:


- A cutset is called feed-forward cutset if the data move in the forward direction on all the paths of the cutset



Architectural Techniques : Pipelining


❖ Example:

 - FIR Filter
- Three feed-forward cutsets are shown



Architectural Techniques : Pipelining


Critical Path: $1M+2A$

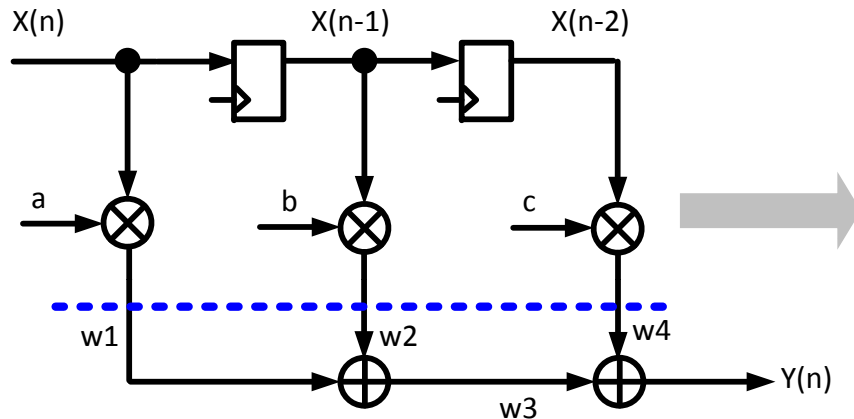

```

assign w1 = a*Xn;
assign w2 = b*Xn_1;
assign w3 = w1 + w2;
assign w4 = c*Xn_2;
assign Y = w3 + w4;
always @(posedge Clk)
begin
    Xn_1 <= Xn;
    Xn_2 <= Xn_1;
end
    
```

Critical Path: $2A$

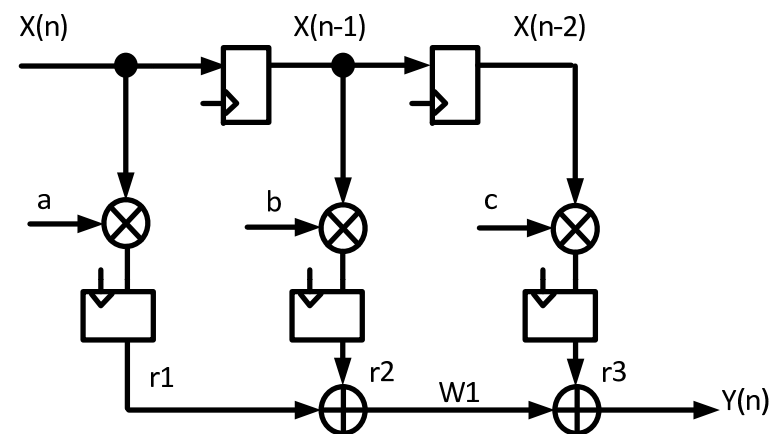


```

assign Y = r3 + w1;
assign w1 = r1 + r2;
always @(posedge Clk)
begin
    Xn_1 <= Xn;
    Xn_2 <= Xn_1;
    r1 <= a*Xn;
    r2 <= b*Xn_1;
    r3 <= c*Xn_2;
end
    
```




Architectural Techniques : Pipelining

 

Clock	Input	1	2	3	4	5	Output
0	$X(0)$	$aX(0)$	-	$aX(0)$	-	$aX(0)$	$Y(0)$
1	$X(1)$	$aX(1)$	$bX(0)$	$aX(1)+bX(0)$	-	$aX(1)+bX(0)$	$Y(1)$
2	$X(2)$	$aX(2)$	$bX(1)$	$aX(2)+bX(1)$	$cX(0)$	$aX(2)+bX(1)+cX(0)$	$Y(2)$
3	$X(3)$	$aX(3)$	$bX(2)$	$aX(3)+bX(2)$	$cX(1)$	$aX(3)+bX(2)+cX(1)$	$Y(3)$



Architectural Techniques : Pipelining

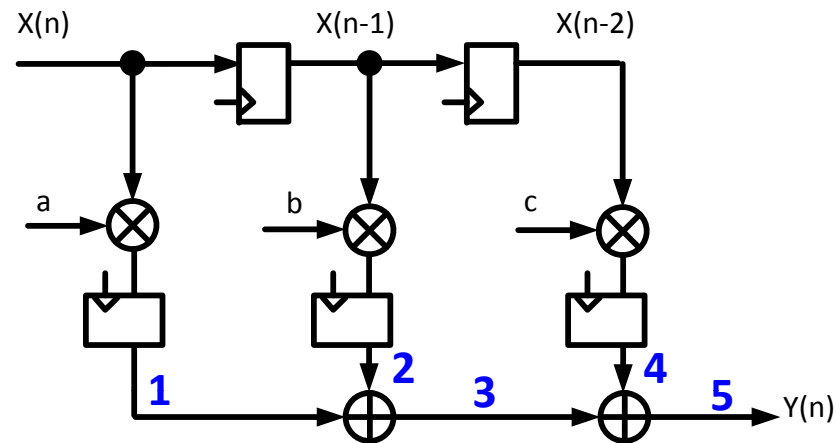


Clock	Input	1	2	3	4	5	Output
0	$X(0)$	-	-	-	-	-	-
1	$X(1)$	$aX(0)$	-	$aX(0)$	-	$aX(0)$	$Y(0)$
2	$X(2)$	$aX(1)$	$bX(0)$	$aX(1)+bX(0)$	-	$aX(1)+bX(0)$	$Y(1)$
3	$X(3)$	$aX(2)$	$bX(1)$	$aX(2)+bX(1)$	$cX(0)$	$aX(2)+bX(1)+cX(0)$	$Y(2)$



Architectural Techniques : Pipelining

Even more pipelining

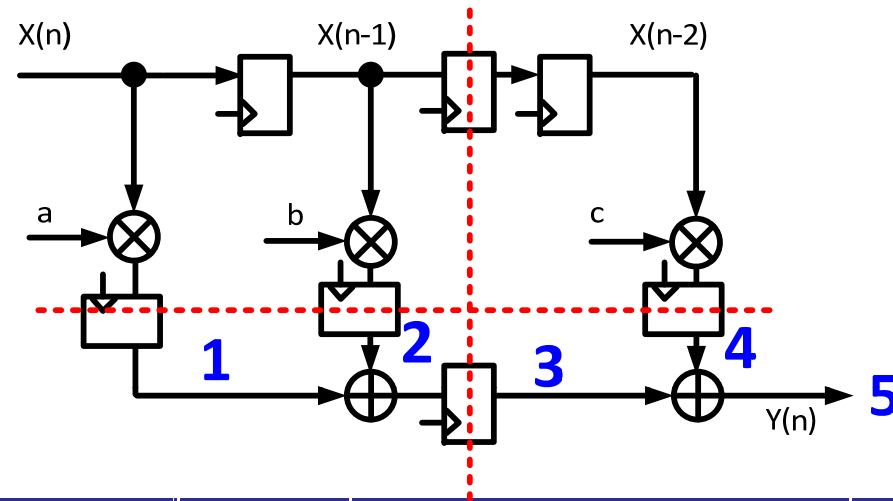


Clock	Input	1	2	3	4	5	Output
0	$X(0)$	-	-	-	-	-	-
1	$X(1)$	$aX(0)$	-	-	-	-	-
2	$X(2)$	$aX(1)$	$bX(0)$	$aX(0)$	-	$aX(0)$	$Y(0)$
3	$X(3)$	$aX(2)$	$bX(1)$	$aX(1)+bX(0)$	-	$aX(1)+bX(0)$	$Y(1)$
4	$X(3)$	$aX(2)$	$bX(1)$	$aX(2)+bX(1)$	$cX(0)$	$aX(2)+bX(1)+cX(0)$	$Y(2)$




Architectural Techniques : Fine-Grain Pipelining

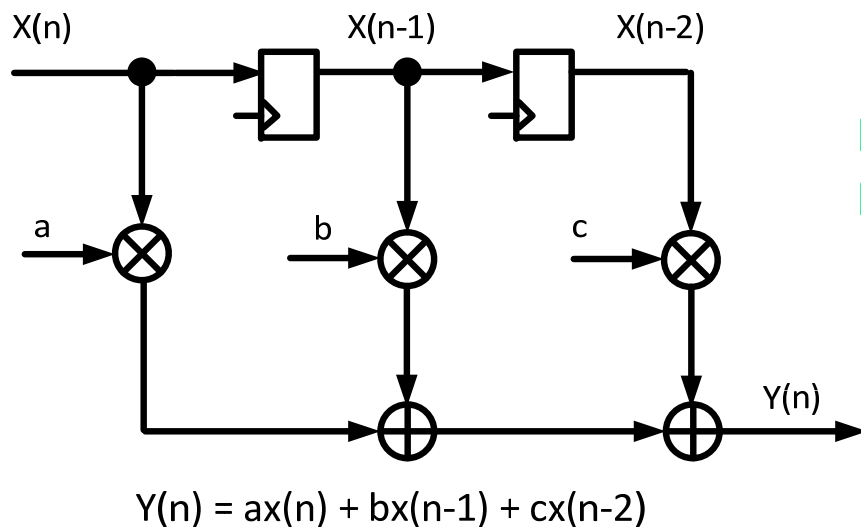- ❖ Pipelining at the operation level
 - Break the multiplier into two parts




Fine-Grain
Pipelining

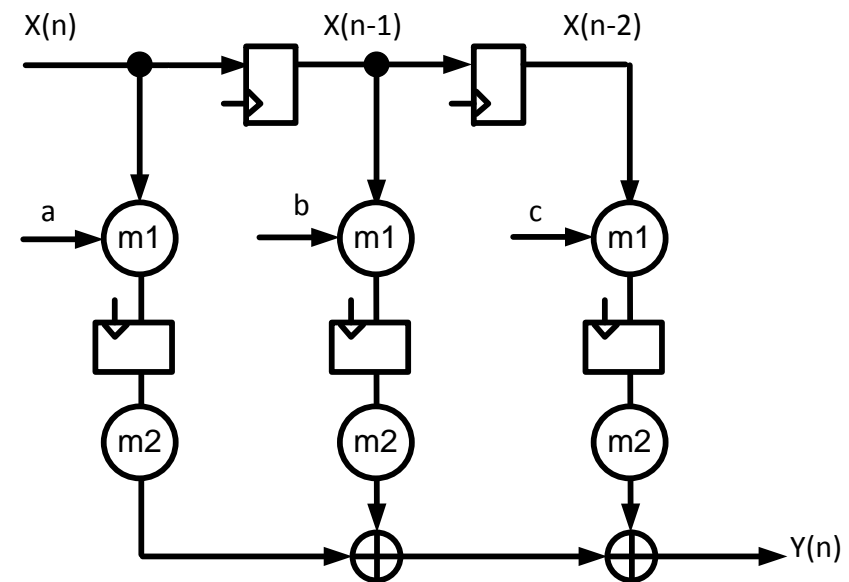

Unrolling the Loop Using Pipelining

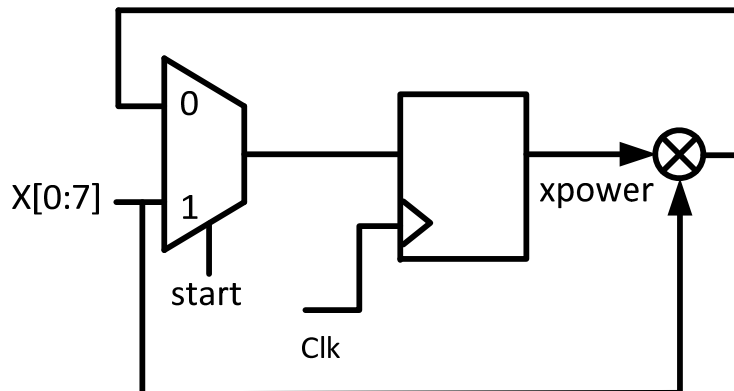- ❑ Calculation of X^3
 - Throughput = $8/3$, or 2.7 bits/clock
 - Latency = 3 clocks
 - Timing = One multiplier in the critical path
- ❑ Iterative implementation:
- ❑ No new computations can begin until the previous computation has completed



```
module power3(  
    output reg [7:0] X3,  
    output finished,  
    input [7:0] X,  
    input clk, start);  
    reg [7:0] ncount;  
    reg [7:0] Xpower, Xin;  
    assign finished = (ncount == 0);  
    always@(posedge clk)  
        if (start) begin  
            XPower <= X; Xin<=X;  
            ncount <= 2;  
            X3 <= XPower;  
        end  
        else if(!finished) begin  
            ncount <= ncount - 1;  
            XPower <= XPower * Xin;  
        End  
    endmodule
```




Unrolling the Loop Using Pipelining

❑ Calculation of X^3

- Throughput = 8/1, or 8 bits/clock (3X improvement)
- Latency = 3 clocks
- Timing = One multiplier in the critical path

❑ Penalty: More Area

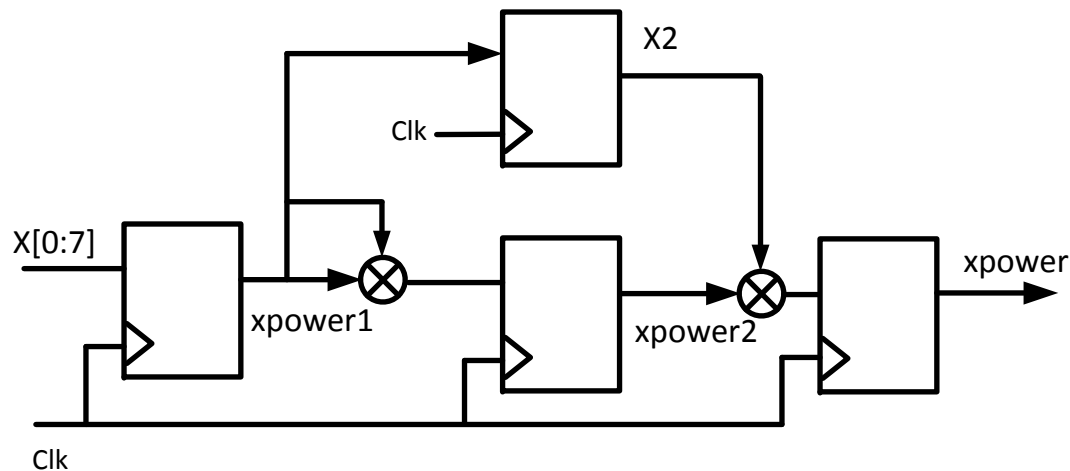Unrolling an algorithm with n iterative loops increases throughput by a factor of n



```
module power3(  
output reg [7:0] XPower,  
input clk,  
input [7:0] X);  
reg [7:0] XPower1, XPower2;  
reg [7:0] X2;  
always @(posedge clk) begin  
// Pipeline stage 1  
XPower1 <= X;  
// Pipeline stage 2  
XPower2 <= XPower1 * XPower1 ;  
X2 <= XPower1 ;  
// Pipeline stage 3  
XPower <= XPower2 * X2;  
end  
endmodule
```




Removing Pipeline Registers (to Improve Latency)

□ Calculation of X^3

- Throughput = 8 bits/clock (3X improvement)
- Latency = 0 clocks
- Timing = Two multipliers in the critical path

 Latency can be reduced by removing pipeline registers




```
module power3(  
    Output [7:0] XPower,  
    input [7:0] X);  
    reg [7:0] XPower1, XPower2;  
    reg [7:0] X1, X2;  
    always @*  
        XPower1 = X;  
    always @(*)  
    begin  
        X2 = XPower1;  
        XPower2 = XPower1*XPower1;  
    end  
  
    assign XPower = XPower2 * X2;  
  
endmodule
```




Architectural Techniques : Parallel Processing

 - ❑ In parallel processing the same hardware is duplicated to
 - Increases the throughput without changing the critical path
 - Increases the silicon area




Pipelining

Parallel Processing

 

Clock Freq: 2f
Throughput: 2M samples

 


Clock Freq: f
Throughput: 2M samples



Architectural Techniques : Parallel Processing

□ Parallel processing for a 3-tap FIR filter

 ➤ Both have the same critical path (M+2A)




Parallel Factor:3

$$y(3k) = ax(3k) + bx(3k - 1) + cx(3k - 2)$$

$$y(3k + 1) = ax(3k + 1) + bx(3k) + cx(3k - 1)$$
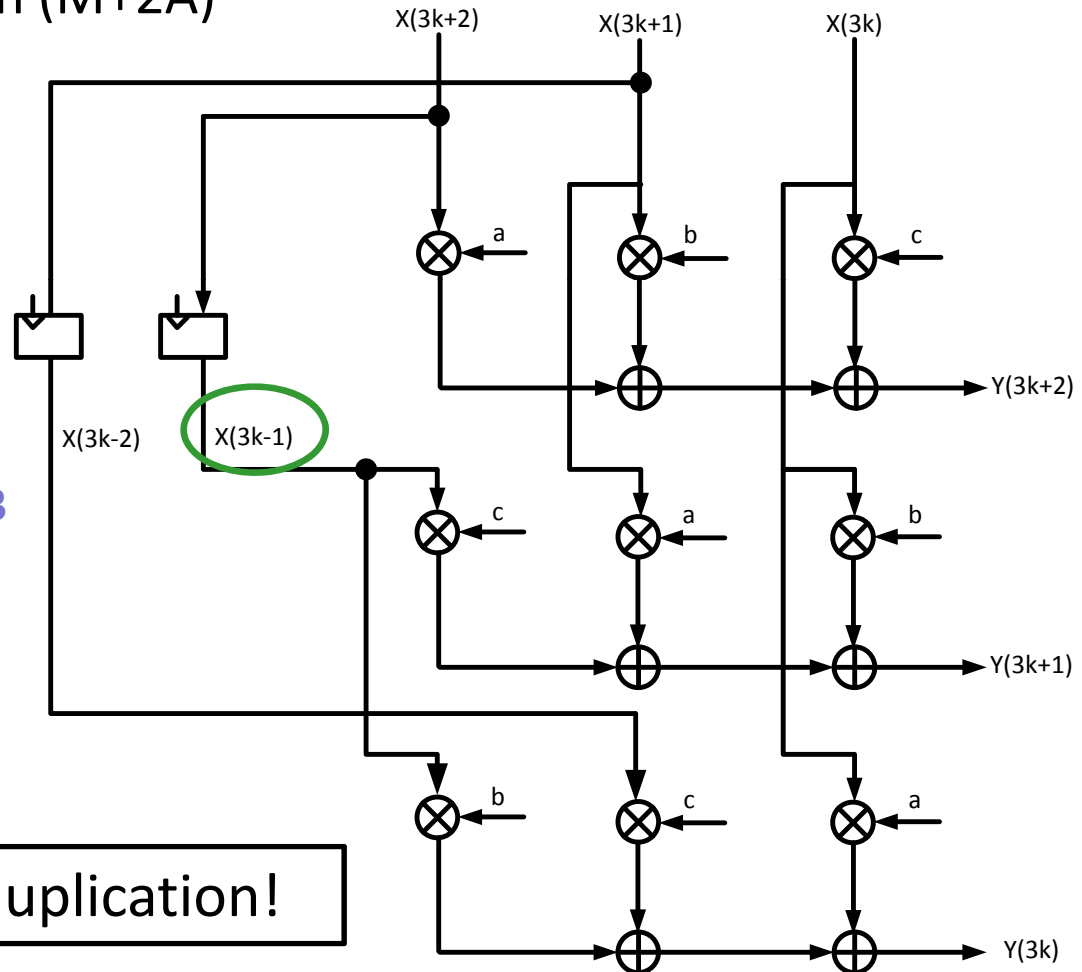
$$y(3k + 2) = ax(3k + 2) + bx(3k + 1) + cx(3k)$$




Not a simple duplication!



Sample Period vs. Clock Period


❑ Pipelined system: $T_{clk} = T_{sample}$

$$T_{sample} = T_{clk} = T_M$$

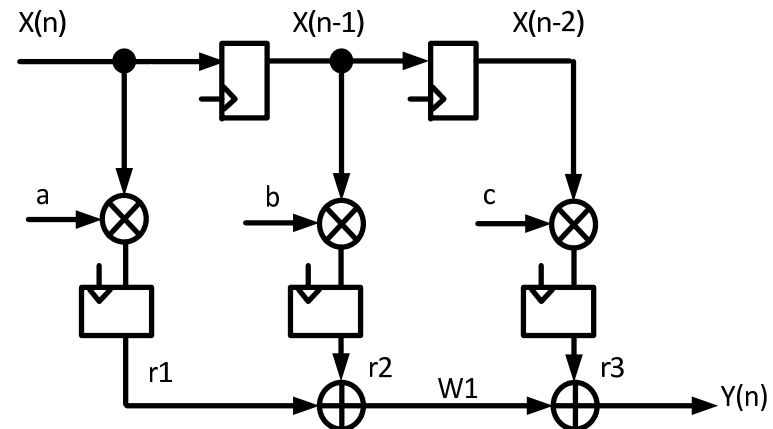

❑ Parallel System: $T_{clk} \neq T_{sample}$
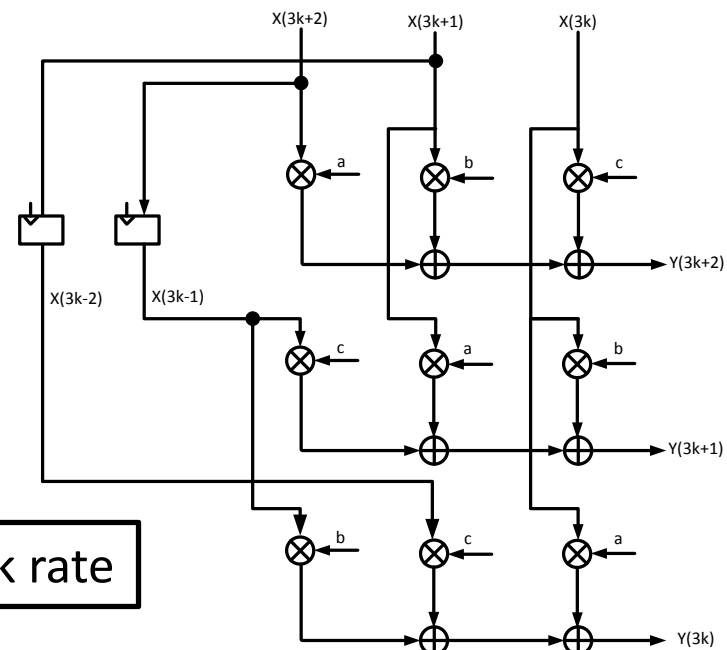
$$T_{sample} = \frac{1}{3} T_{clk} = \frac{1}{3} (T_M + 2T_A)$$




Higher Sample rate than the clock rate




Complete Parallel System with S/P and P/S

□ A Complete Parallel System:

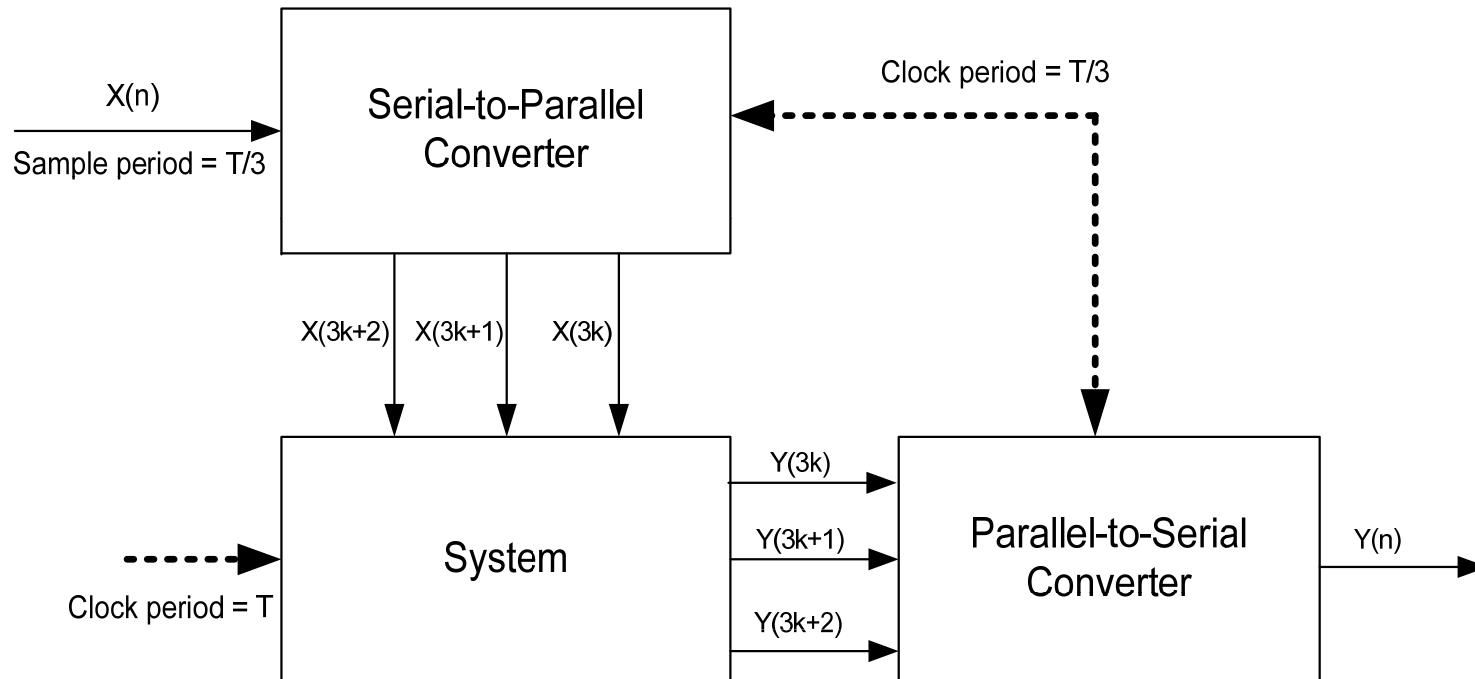


S/P and P/S Blocks

□ S/P Converter:

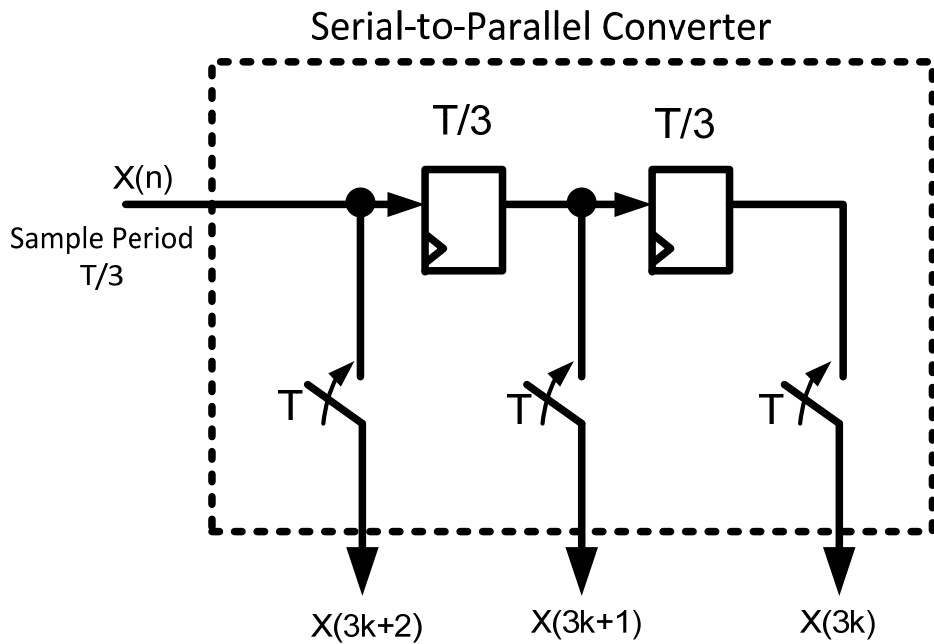

□ P/S Converter:

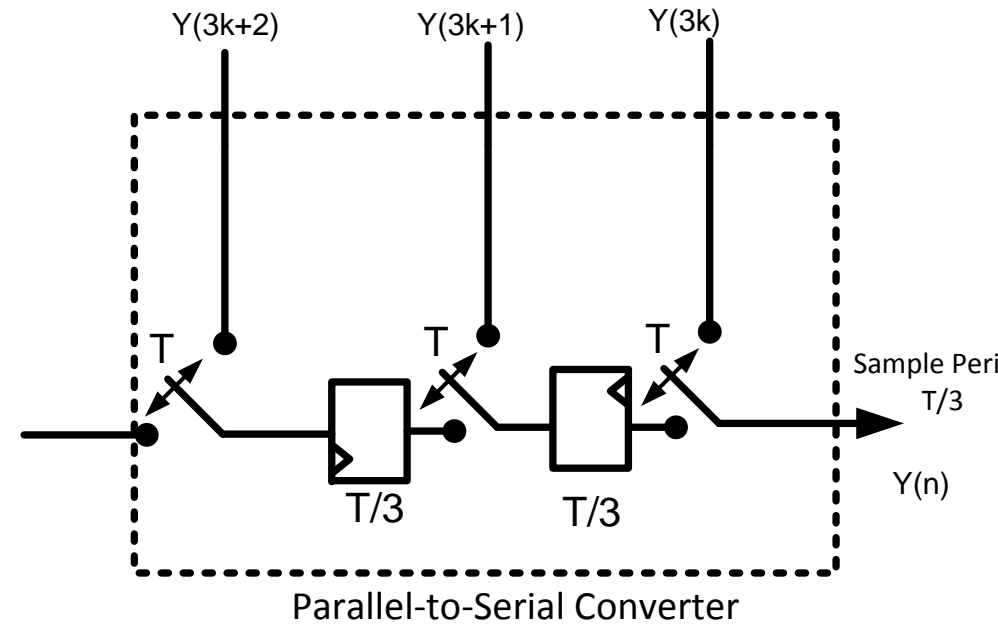

When Pipelining When Parallelism?

- ❑ Pipeline technique is used when the critical path is in the design (Number 1, 2, 3, 4)
- ❑ Parallelism is used when the critical path is bounded by the communication or I/O bound. (Number 5)
 - Pipelining does not help in this case!
 - a.k.a Communication Bounded

