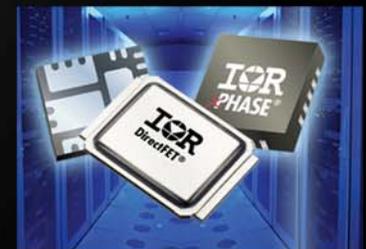


# EE 5741

## Design of Electronic Ballasts

Eric Persson  
Exec. Director, WW Field Applications Engineering  
April 17, 2009

International  
**IOR** Rectifier




# Agenda

---

- Gas-Discharge lamps
- ZVS Resonant Half-Bridge output stage
- Typical ballast designs
- PFC
- Protection features
- Summary


# Gas Discharge Lamp Basics

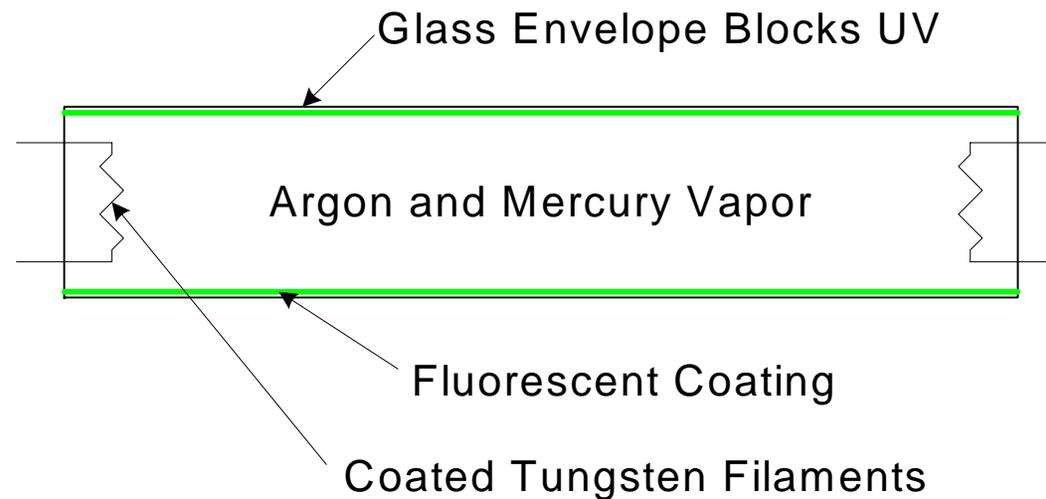

## “Low Pressure” Fluorescent Lamp

- Current flows through plasma between electrodes
  - Must be AC or mercury migrates to one end
- Plasma emits mostly UV radiation
- UV excites coating to fluoresce and produce visible light
- Heated electrodes improve lamp life and lower strike voltage

# High Intensity Discharge (HID) Lamps

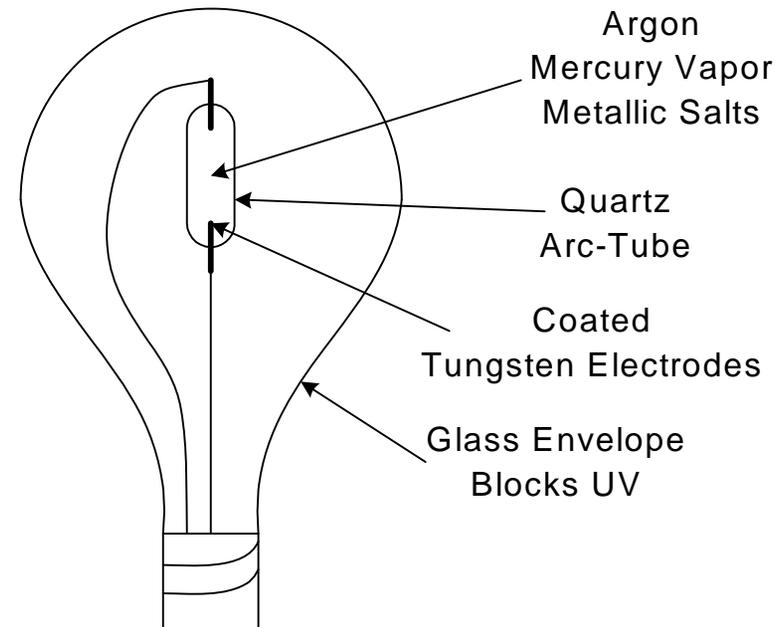

## Medium Pressure Lamp

- AC current flows through plasma between electrodes
- Plasma emits UV radiation AND visible light directly

# Why Gas Discharge Lamps?

---




## Advantages

- Lower total cost of ownership
- Higher efficacy (Lumens/watt)
- Broad-spectrum, high CRI (HID)
- Long lifetime (15k hours)
- Dimmable (fluorescent)


## Disadvantages

- Higher initial cost
- Requires ballast for operation
- Narrow spectrum, lower CRI (most fluorescent)
- Long warmup time (HID)
- Disposal/recycling issues


# Fluorescent Lamp Operating Modes

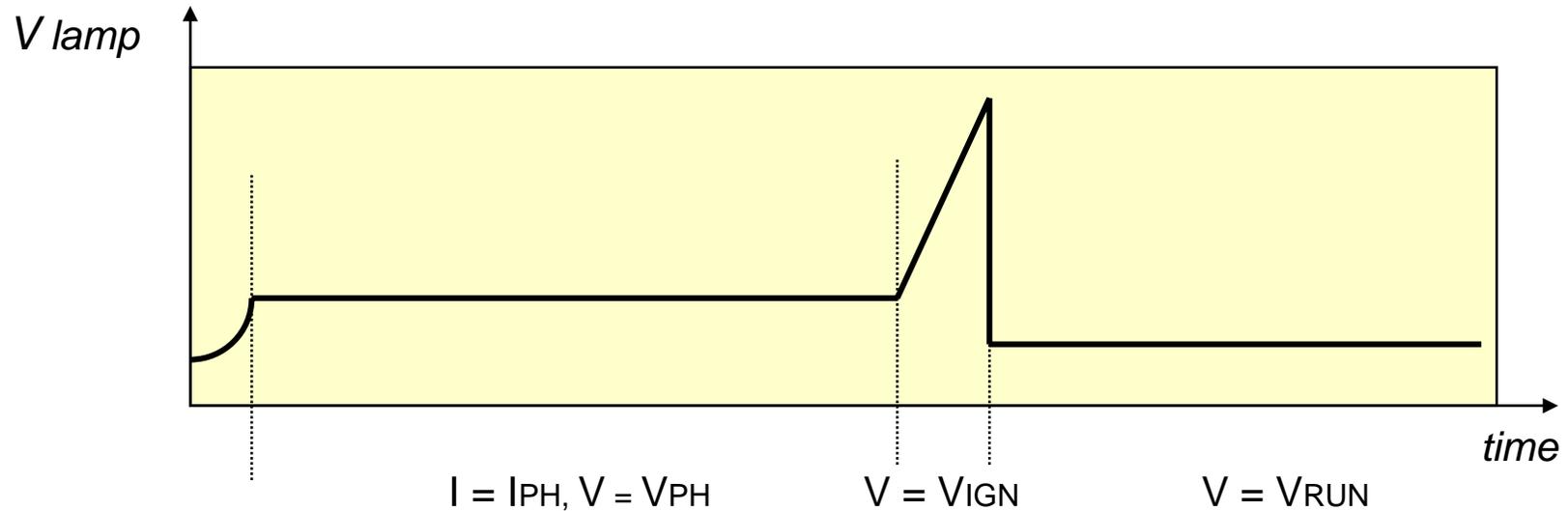


Start

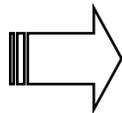





PH

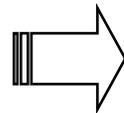


IGN

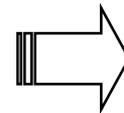


RUN

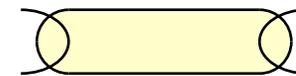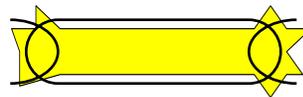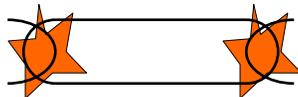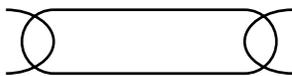



# Simple Ballast Block Diagram

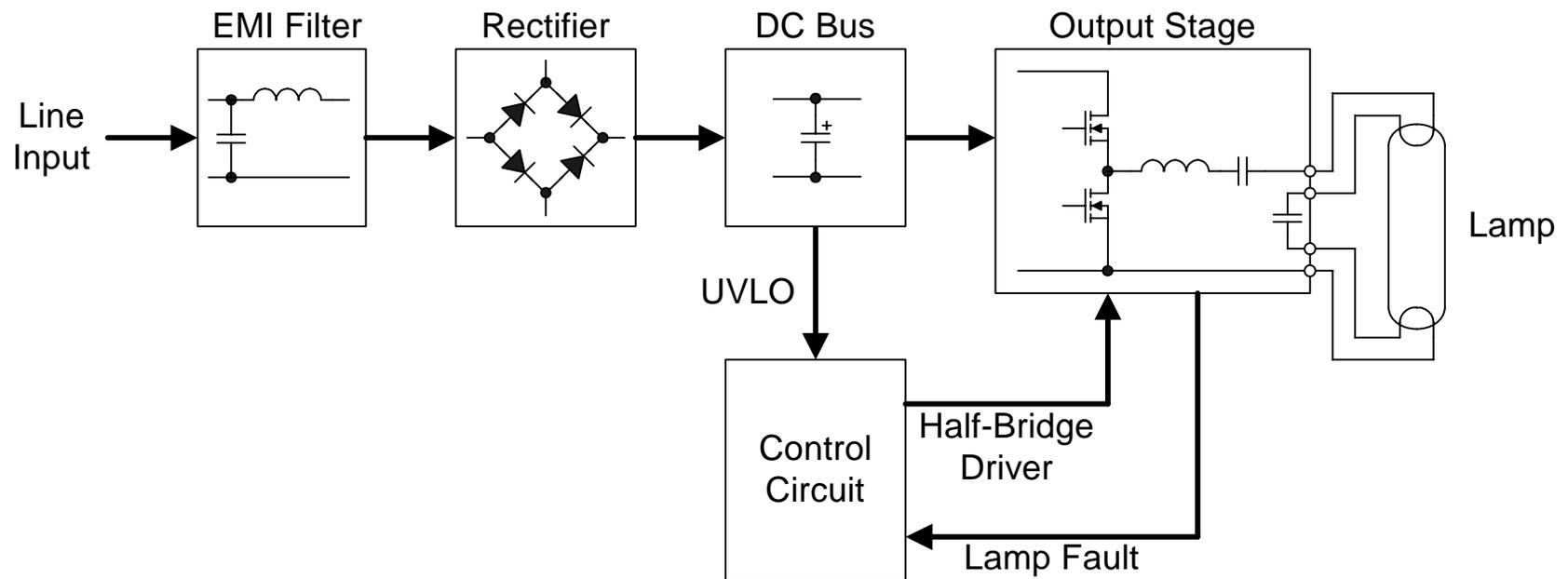


# Power stage - resonant LC Circuit

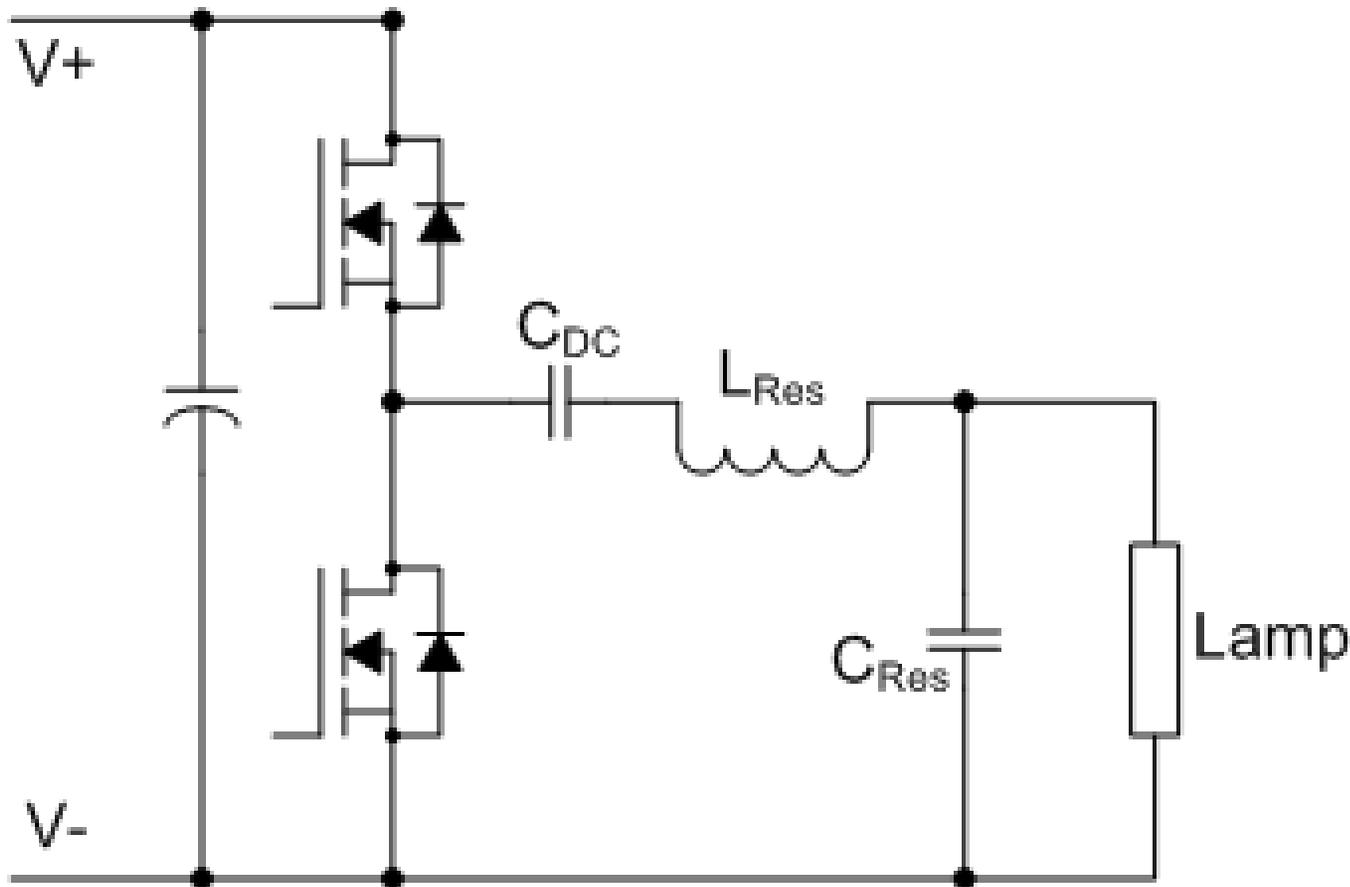

# Parallel Resonant, Above Resonance

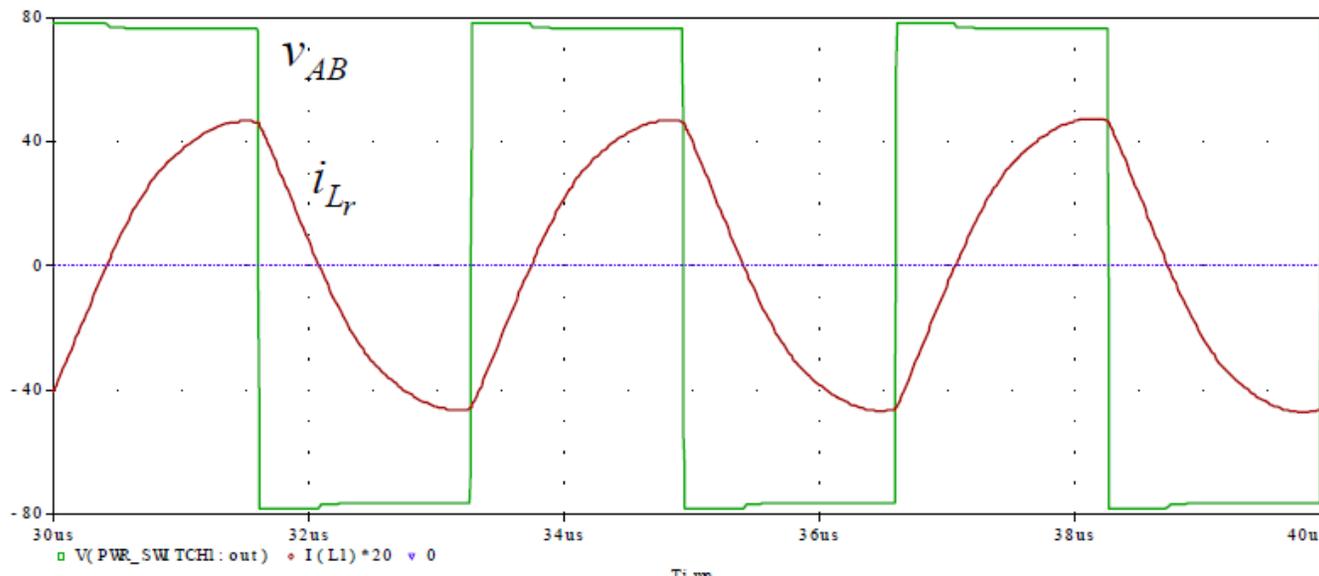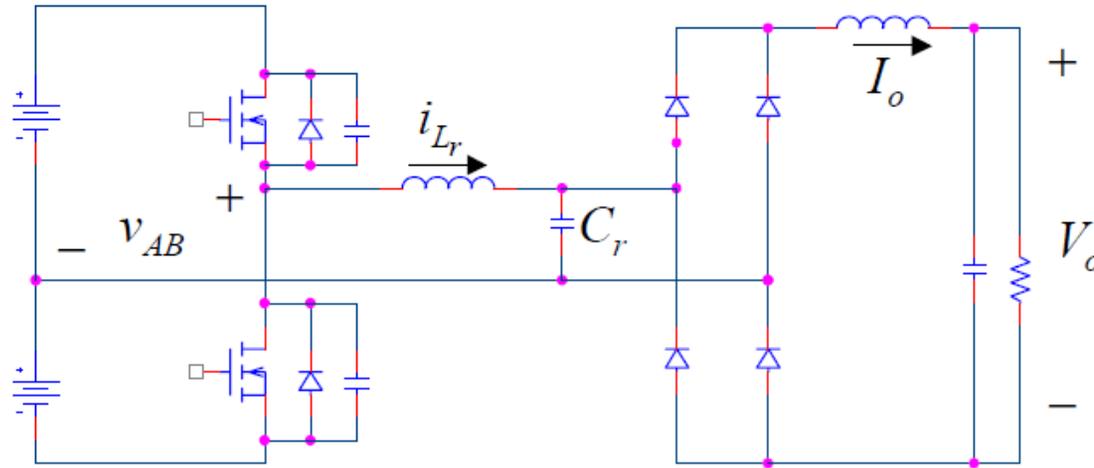


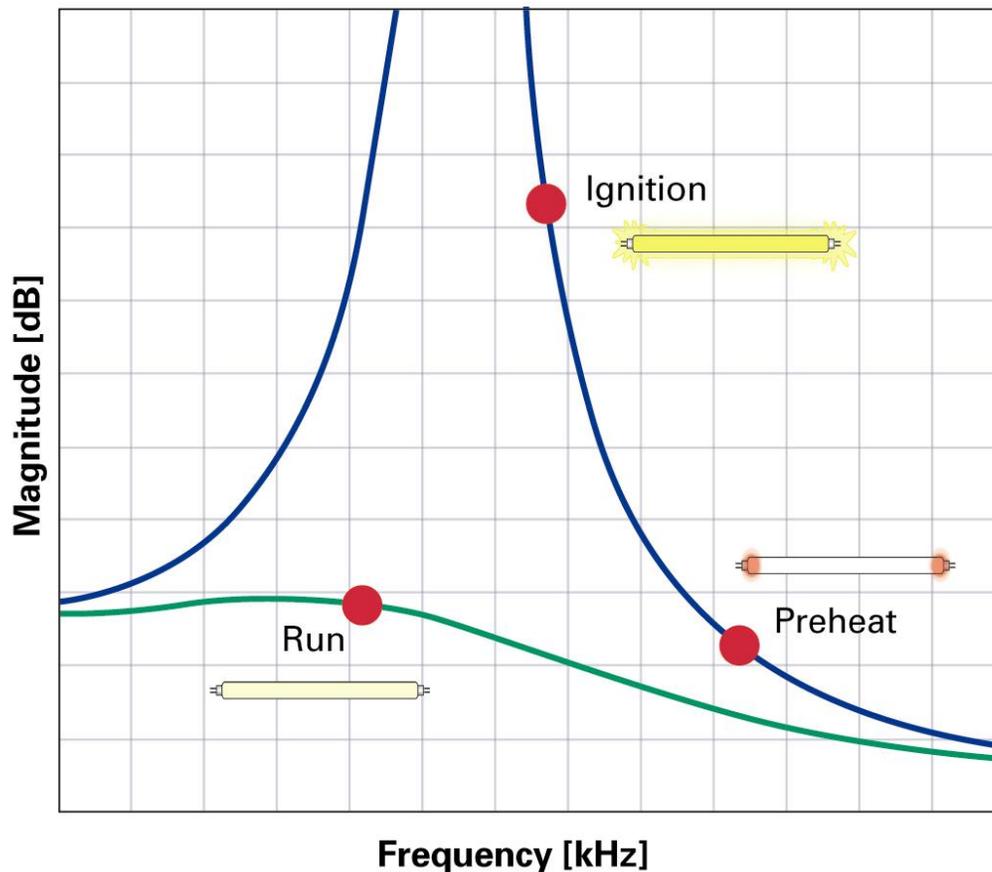

## Design Constraints

- $f_{RUN} \geq 42KH_z$  (infrared)
- $f_{PH} - f_{IGN} \geq 10KH_z$  (tolerances)
- $V_{PH} \leq V_{PH_{MAX}}$  (ignition during preheat)
- $I_{IGN} \leq I_{MAX}$  (component ratings)


# CFL Ballast Typical Schematic

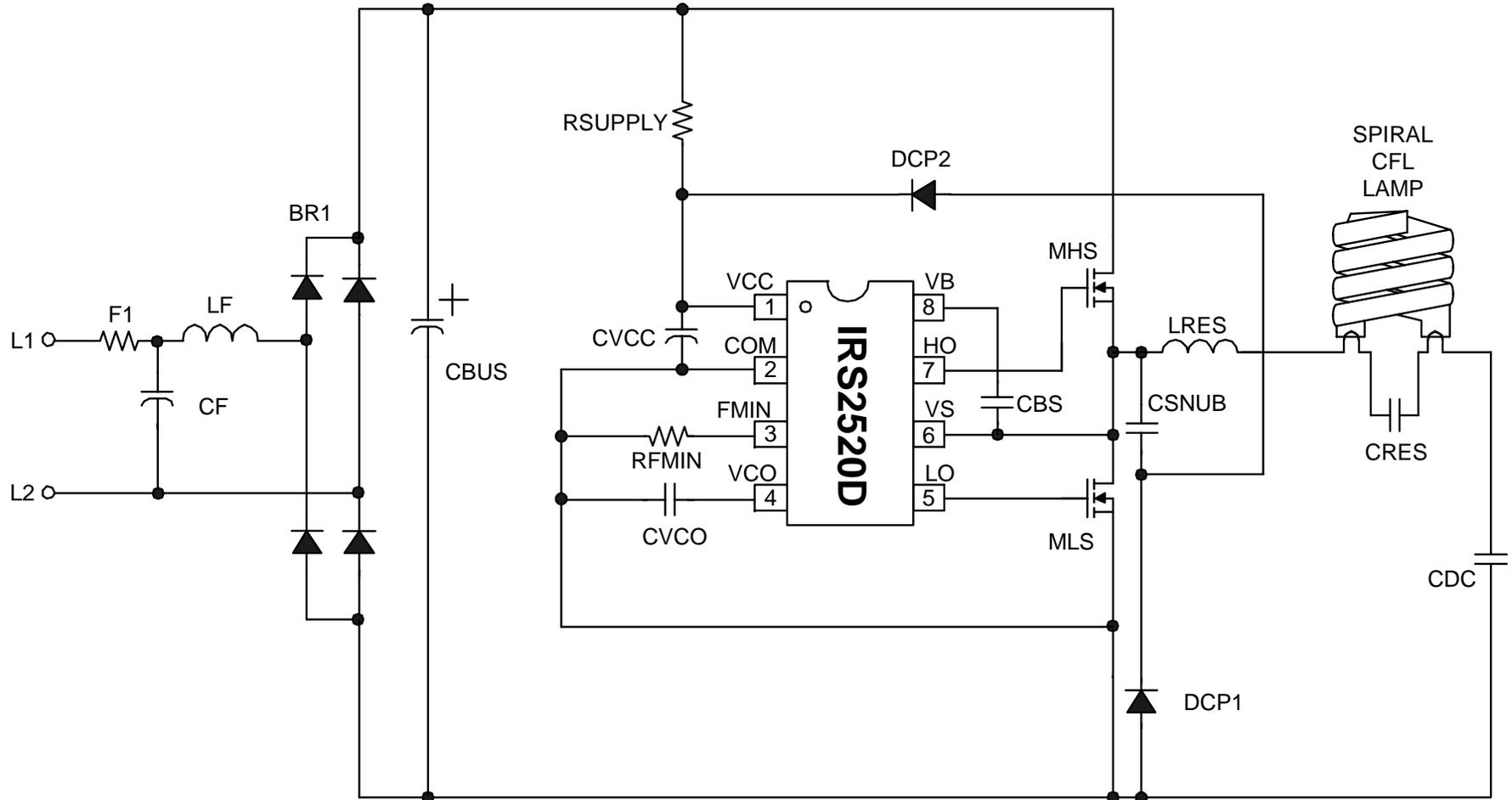

# Typical Design Procedure for Ballast




Begin with lamp requirements

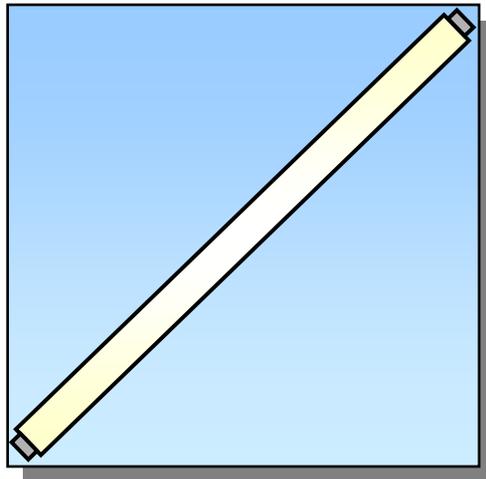

Lamp Type: 36W/T8

- Preheat Current: 0.6 [A]
- Preheat Time: 2 [sec]
- Max Preheat Voltage: 600 [Vpp]
- Ignition Voltage: 1500 [Vpp]
- Running Lamp Power: 34 [W]
- Running Lamp Voltage: 141 [Vpk]

# Select Resonant L and C

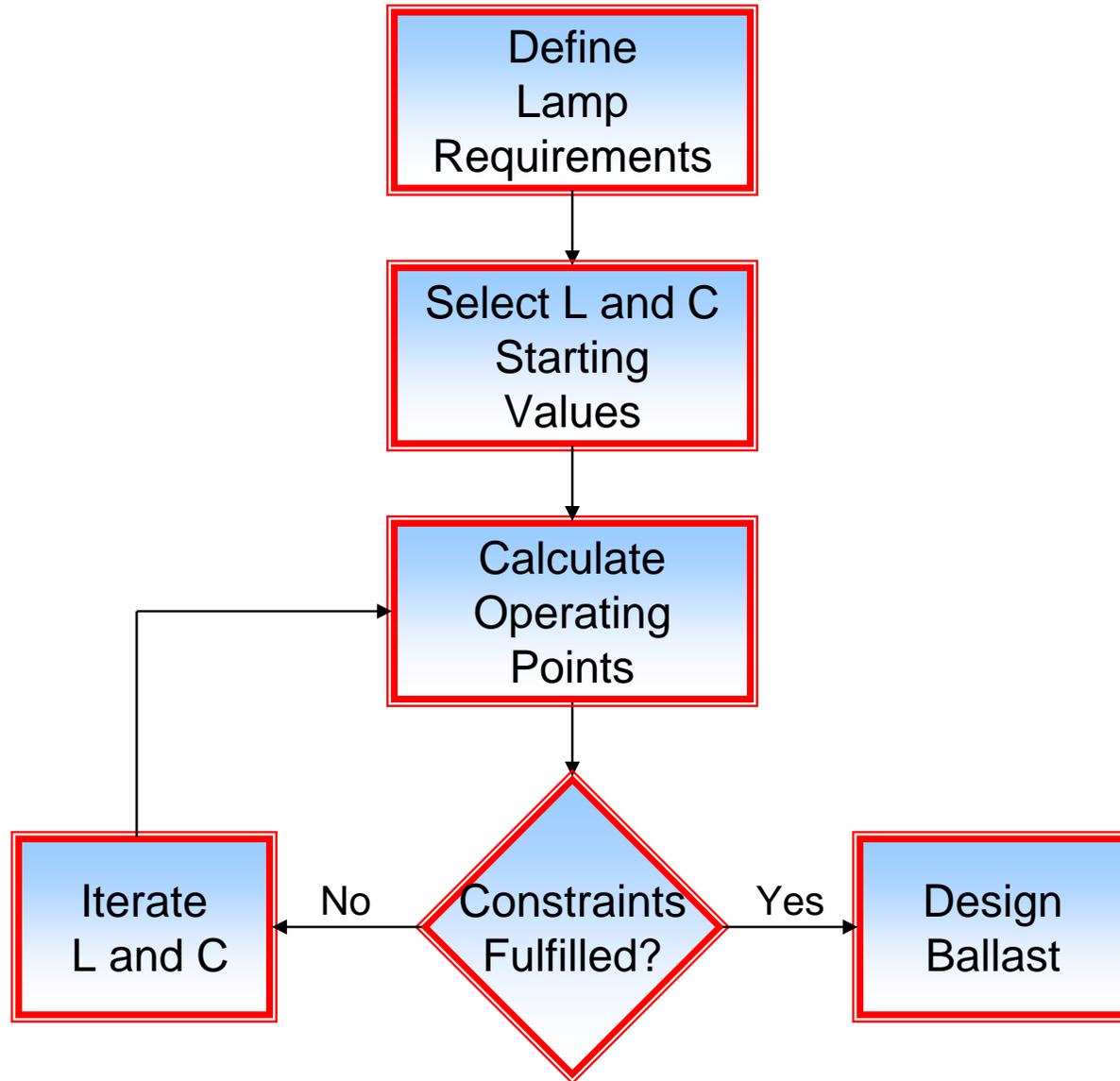

# Spreadsheet Method




L and C selection example for linear lamp:


Lamp Type = T8/36W,  $P_{RUN} = 32W$ ,  $V_{RUN} = 141 V_{pk}$ ,  $V_{PHMAX} = 300 V_{pk}$ ,  
 $I_{PH} = 0.6 Arms$ , and  $V_{IGN} = 600 V_{pk}$ .

Inputs		Outputs				
L (H)	C (F)	$I_{IGN}$ (Apk)	$f_{PH}$ (KHz)	$f_{IGN}$ (KHz)	$f_{RUN}$ (KHz)	$V_{PH}$ (Vpk)
0.002	3.3E -9	0.9	75	74	43	545
0.002	6.8E -9	1.3	57	52	45	350
0.002	1.0E -8	1.6	49	42	43	273
0.002	1.5E -8	2.0	43	35	39	208



# Ballast Design Assistant Software

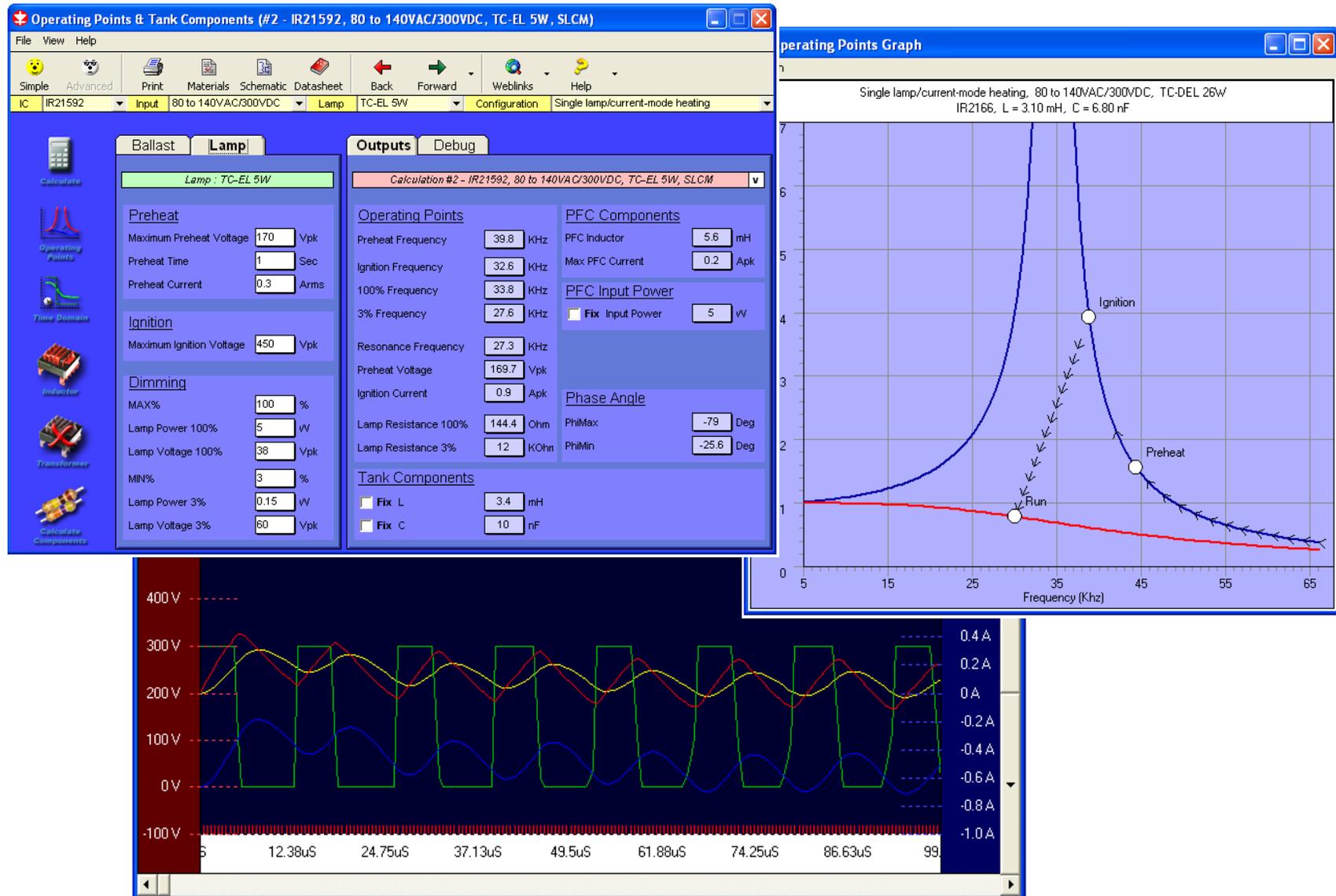


# Adding Power Factor Correction

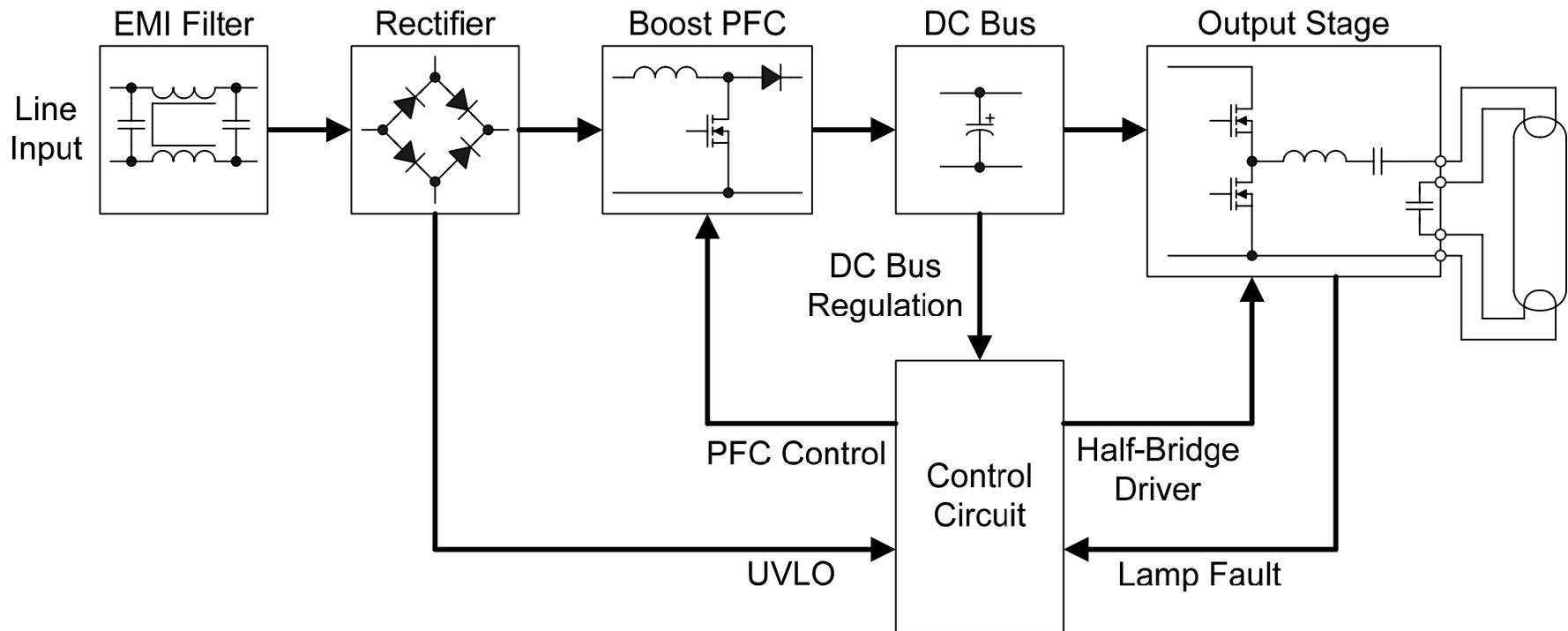

# CrCM boost-mode PFC commonly used

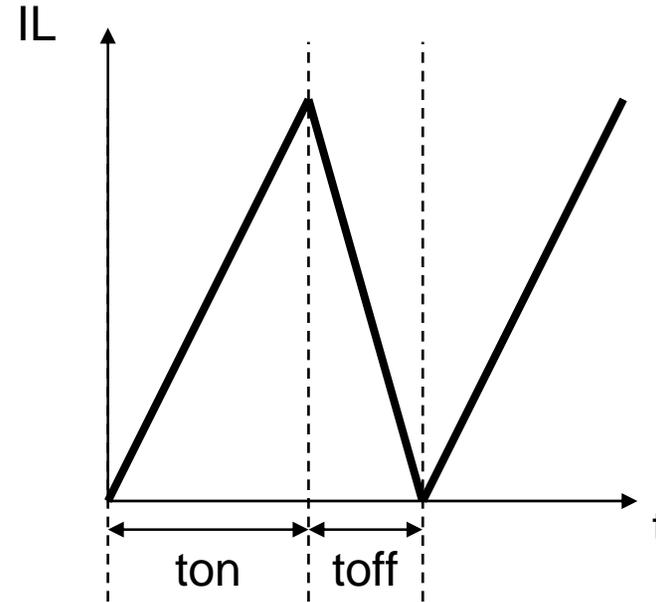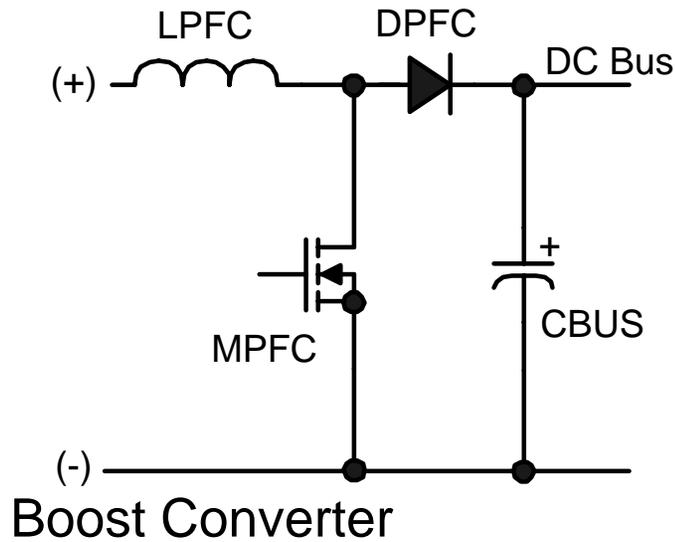


Critical-conduction Mode (CrCM)

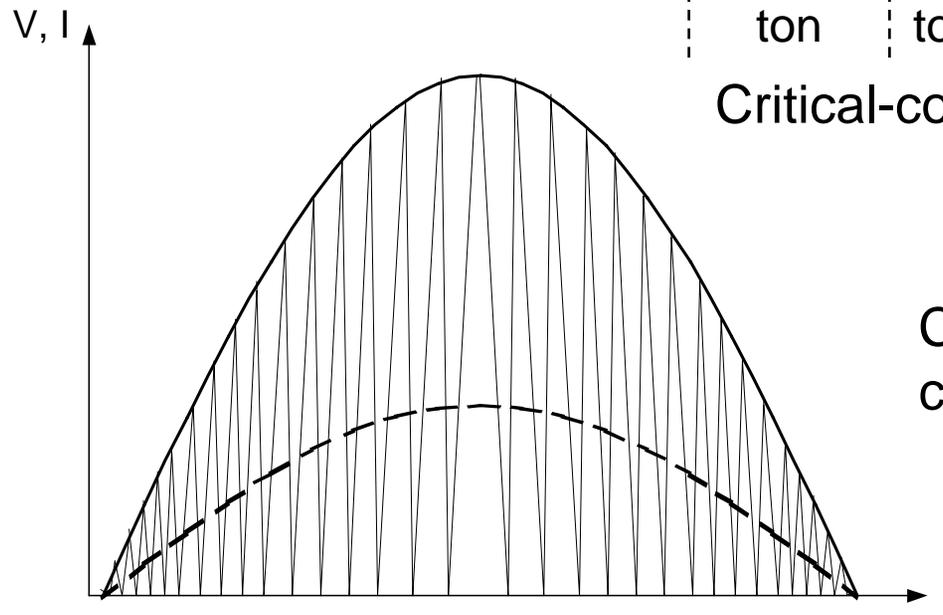


Constant on-time control


# Advanced protection – lamp out circuit

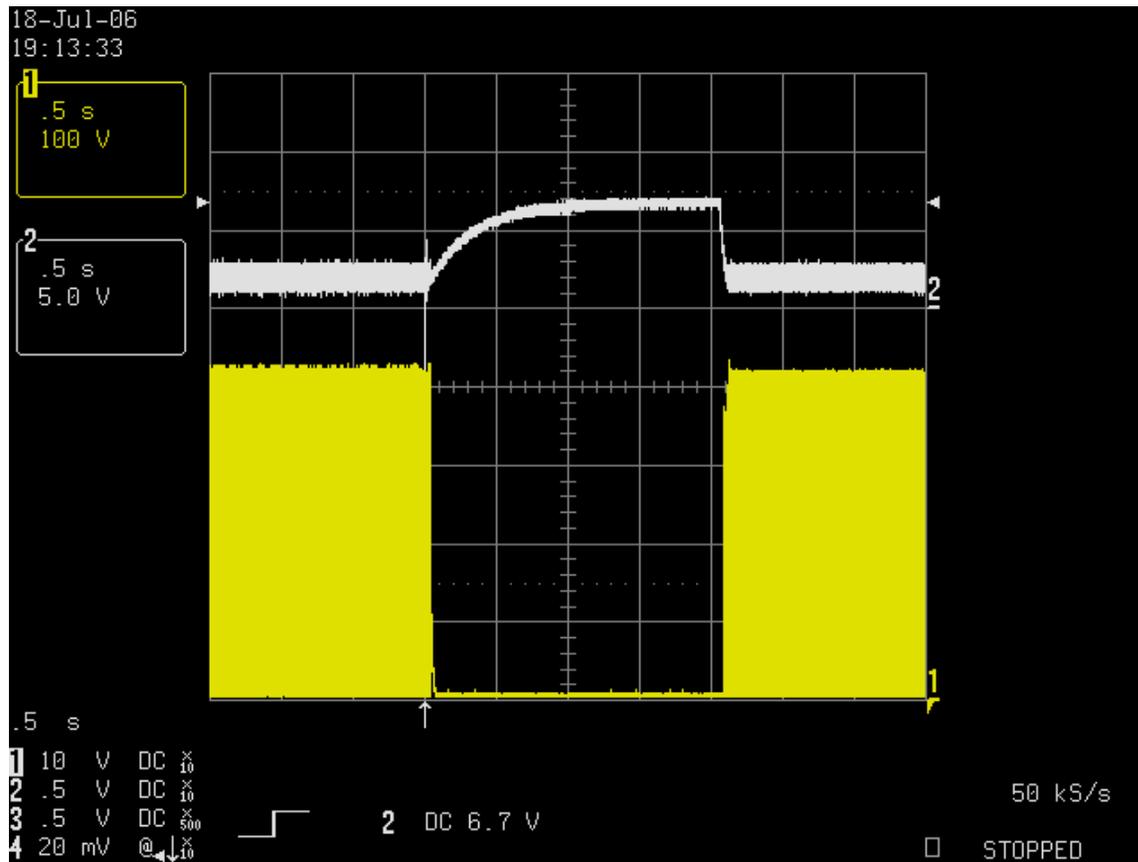

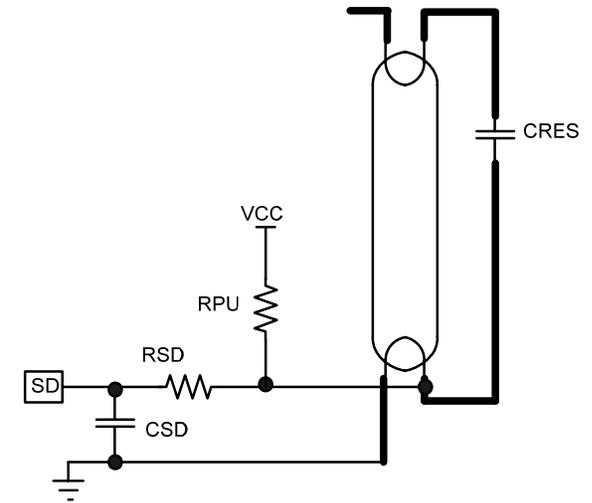
SD pin (upper) and half-bridge voltage (lower) during lamp out/re-insert condition



# End-of-life detection - protection

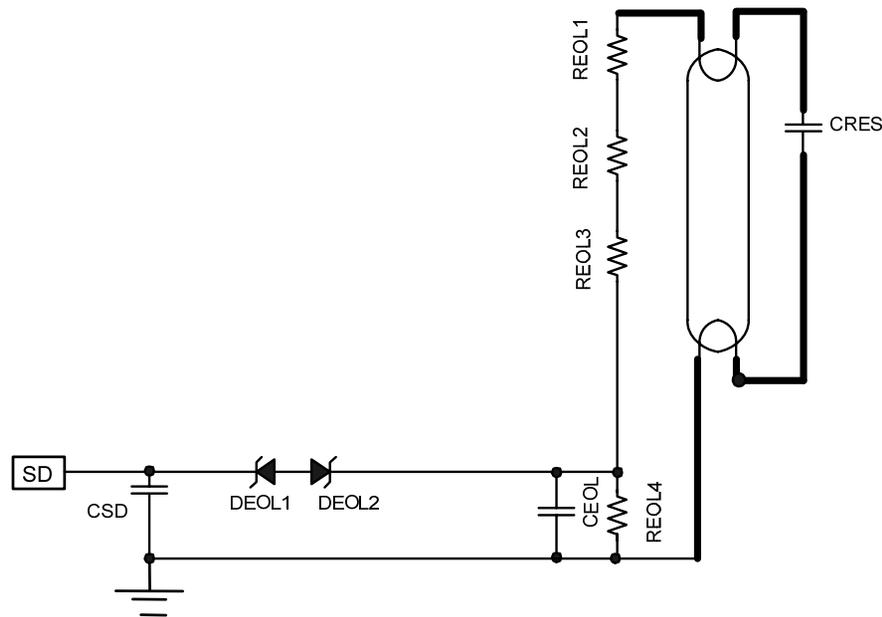


## Lamp Voltage

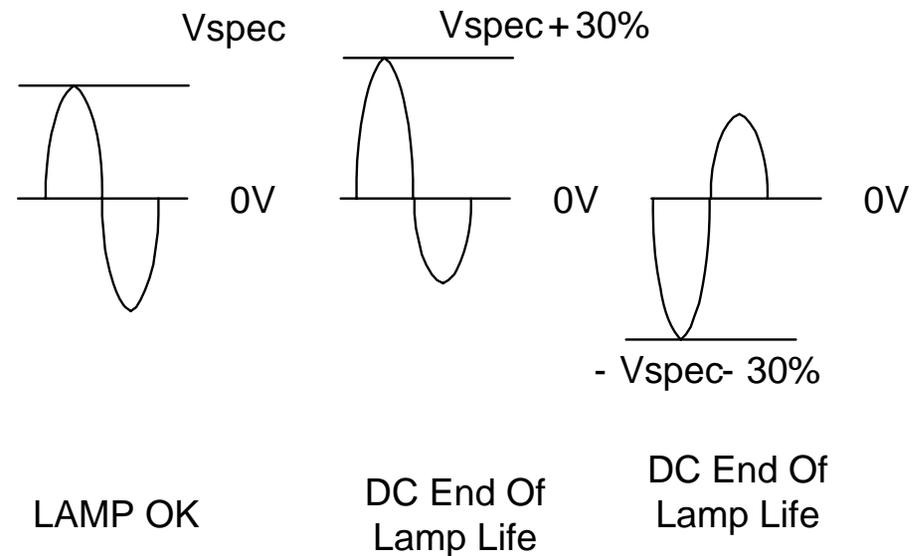

$V_{spec} = V_{pK}$  in the spec of the lamp

The SD pin is internally biased at 2V. During end of life the lamp voltage will increase asymmetrically (DC end of life). The voltage offset sensed at the top of REOL4 will increase and one of the Zeners will turn on, therefore triggering the shutdown.

# Example Ballasts

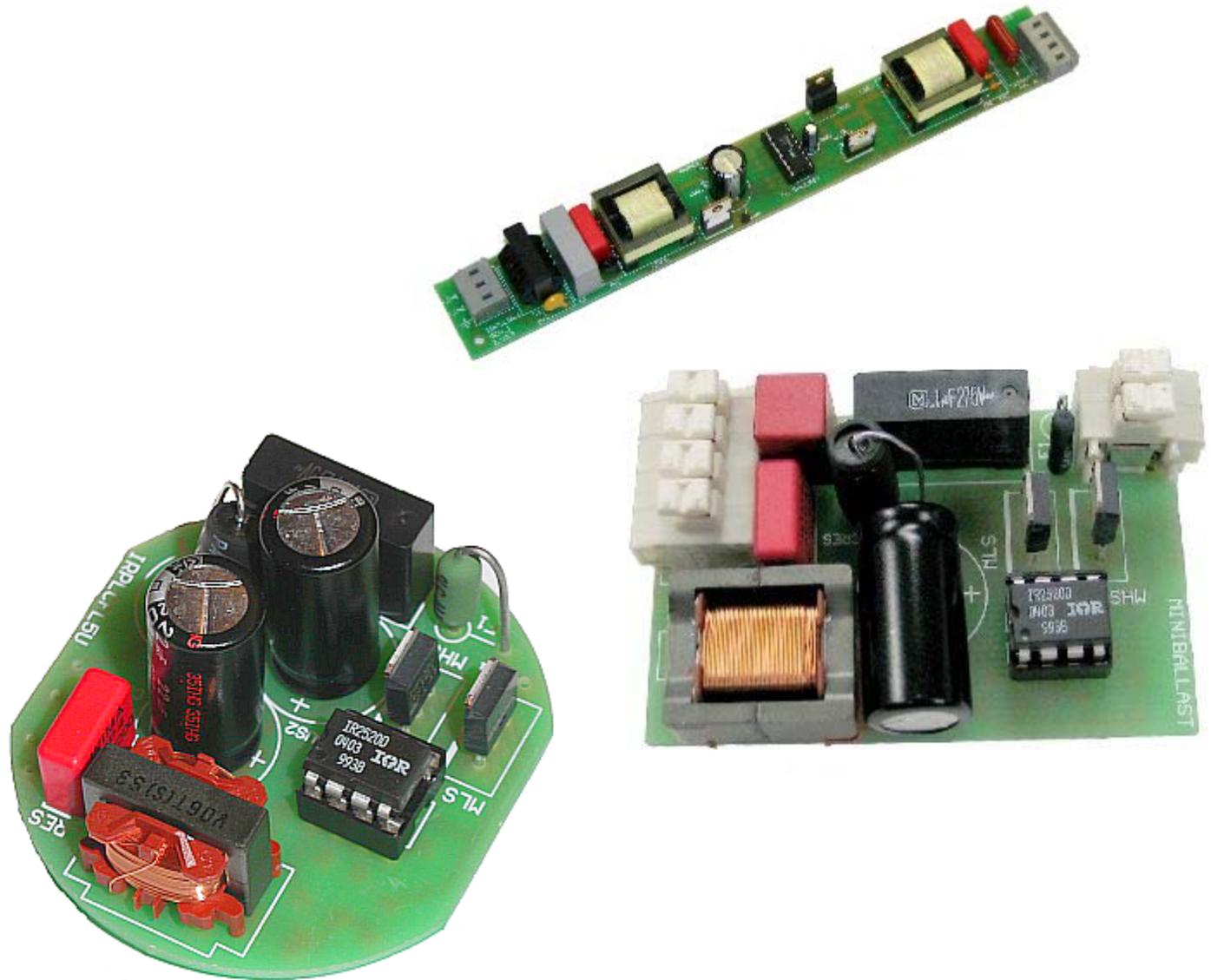

# Summary

---

- Gas-discharge (Fluorescent) lamps offer:
  - Improved efficacy (lumens/watt)
  - Lower total operating cost
  - Better CRI lowers light output
- Ballast is necessary to operate lamp
- Ballast operates ZVS to minimize switching loss
- Ballast controls frequency to adjust lamp current
- Ballast self protects by shutdown when lamp misbehaves